

RYERSON UNIVERSITY

Department of Electrical & Computer Engineering

MID-TERM Examination

Course Name: Electronic Circuits

Course Number: ELE 404

Examiners: Prof. D. Androutsos
Prof. A. Kabbani

DATE: Wednesday February 28, 2007

DURATION: 110 Minutes

TOTAL MARKS: 100

EXAMINATION INSTRUCTIONS:

1. This is a closed-book examination. No aids other than basic calculators are permitted.
2. The examination paper contains 9 pages and is comprised of FOUR questions worth 100 marks, *and are not equally weighted.*
3. No questions are allowed during the examination time. *If in doubt, state your assumptions.*

INFORMATION:


- (a) OP-AMPS are assumed to be ideal, unless stated otherwise. The maximum output voltage of any OP-AMP is limited by its power-supply voltages, $\pm V_{CC}$.
- (b) Note:- Symbols "V" or "v" stand for Volts; "k" stands for kilo-Ohms; and "mA" stands for milli-Amps.
- (c) The diode current (I_D) in the forward-bias mode is given as: $I_D = I_S \exp(V_D/nV_T)$, and the voltage difference between two operating points for a forward-bias diode can be expressed as:
 $V_{D2} - V_{D1} = 2.3nV_T \log(I_{D2}/I_{D1})$.

NAME: SOLUTION **NUMBER:** _____

SECTION #: _____

Q1	Q2	Q3	Q4	TOTAL
/25	/28	/20	/27	/100

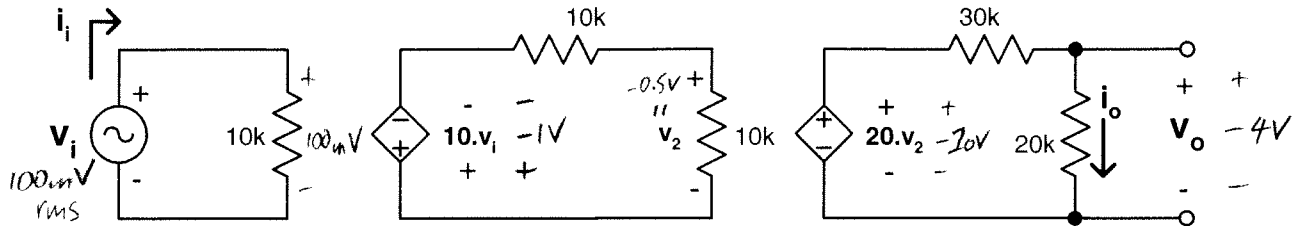Q1(a). [15 marks] An amplifier has the small-signal a.c. equivalent circuit as shown below. (i) Find the voltage gain A_v , (v_o/v_i) and current gain A_i , (i_o/i_i) of the amplifier; and (ii) if this amplifier draws 1mA from a single 10V d.c. supply when $v_i = 100\text{mV}$ r.m.s., determine the signal input power, P_{in} , signal output power, P_{out} , and the power efficiency, η , of the amplifier.



$$\frac{V_o}{V_i} = \frac{-4V}{100mV} = -40V/V$$

$$i_o = \frac{-4V}{20k} = -0.2mA \text{ rms}$$

$$\frac{i_o}{i_i} = \frac{-0.2mA}{0.01mA} = -20A/A$$

$$i_i = \frac{100mV}{10k} = 0.01mA \text{ rms}$$

$$P_{in} = (0.01mA)(100mV) = 0.001mW$$


$$P_{dc} = (1mA)(10V) = 10mW$$

$$P_{out} = (0.2mA)(4V) = 0.8mW$$

$$\eta = \frac{P_{out}}{P_{in} + P_{dc}} \times 100\% = \frac{0.8mW}{0.001mW + 10mW} = 0.079998 \times 100\% = 8\%$$


A_v	A_i	P_{in}	P_{out}	η
$-40V/V$	$-20A/A$	$0.001mW$	$0.8mW$	8%

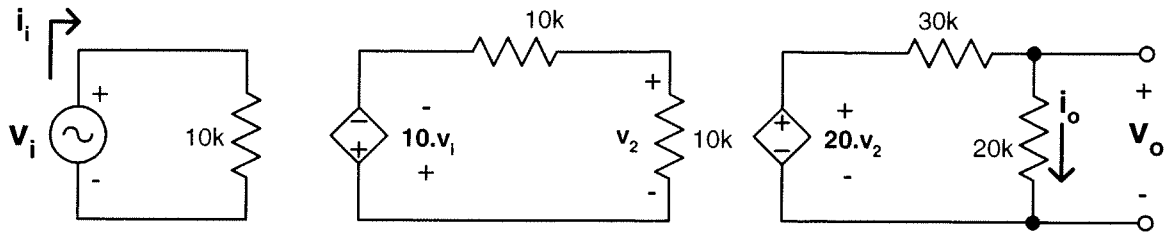Q1(a). [15 marks] An amplifier has the small-signal a.c. equivalent circuit as shown below. (i) Find the voltage gain A_v , (v_o/v_i) and current gain A_i , (i_o/i_i) of the amplifier; and (ii) if this amplifier draws 1mA from a single 10V d.c. supply when $v_i = 100\text{mV}$ r.m.s., determine the signal input power, P_{in} , signal output power, P_{out} , and the power efficiency, η , of the amplifier.



η	P_{out}	P_{in}	A_i	A_v
8%	0.8mW	0.001mW	-20 A/A	-40 V/V

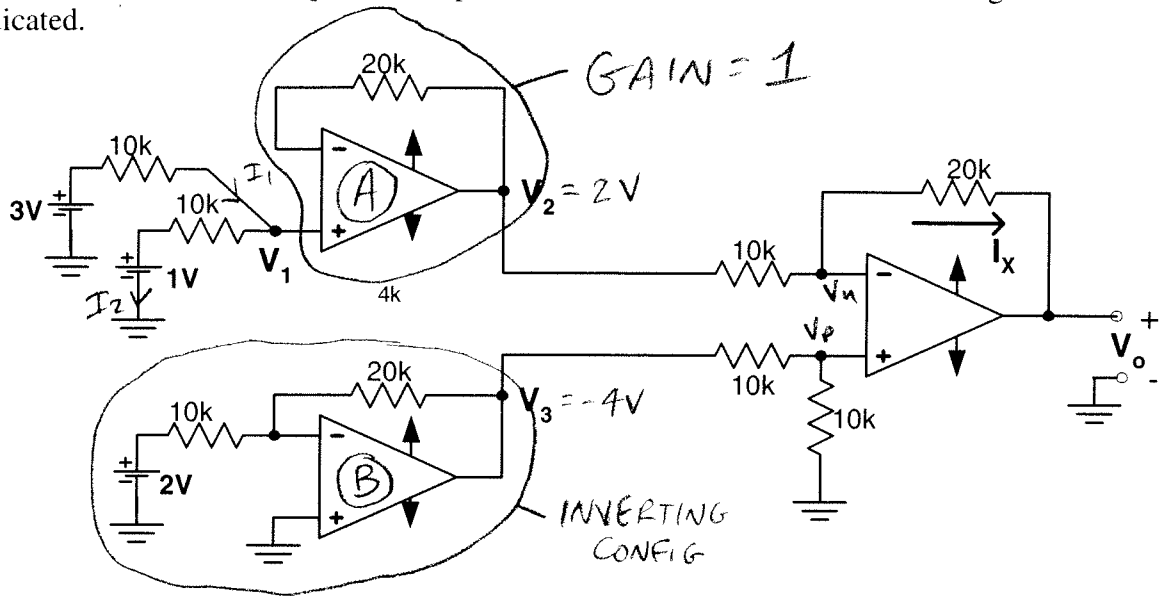Q1(b). [10 marks] For Op-AMP amplifier circuit shown, determine the voltages and current as indicated.



$$I_1 = I_2$$

$$V_3 = 2V \left(-\frac{20k}{10k} \right) = -4V$$


$$\frac{3 - V_1}{10k} = \frac{V_1 - 1}{10k}$$

$$V_1 = 2V$$

Since op-amp (A) has gain = 1

$$V_2 = V_1 = 2V$$

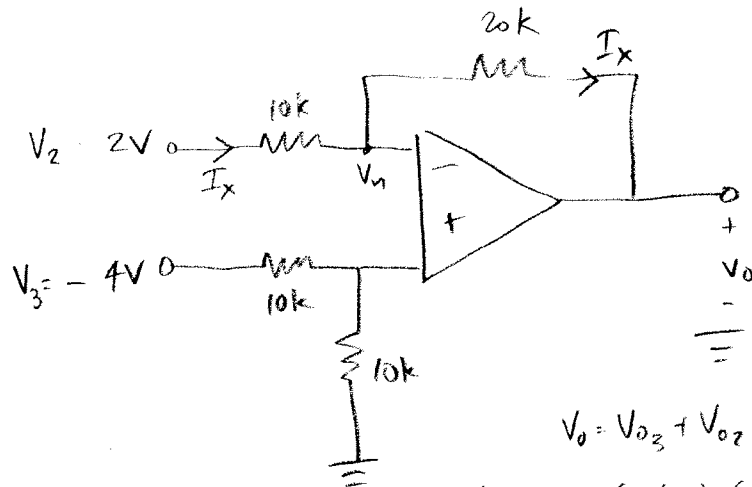Can now solve the following using superposition:



$$V_0 = V_{03} + V_{02}$$

$$V_{03} = (-4) \left(\frac{10k}{10k + 10k} \right) \left(1 + \frac{20k}{10k} \right) = -6V$$

$$V_{02} = (2) \left(-\frac{20k}{10k} \right) = -4V$$

$$\therefore V_0 = -10V$$

$$\frac{V_2 - V_n}{10k} = \frac{V_n - V_0}{20k}$$


$$\frac{2 - V_n}{10k} = \frac{V_n + 10}{20k}$$

$$V_n = -2$$

$$I_x = (V_n - V_0) / 20k = 0.4mA$$


V_1	V_2	V_3	I_x	V_0
2V	2V	-4V	0.4mA	-10V

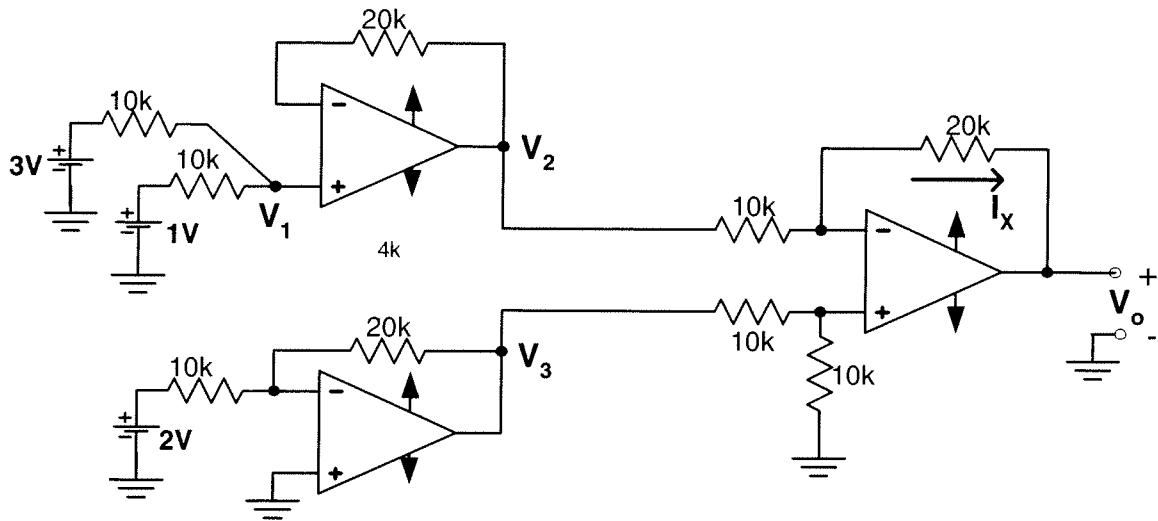Q1(b). [10 marks] For Op-AMP amplifier circuit shown, determine the voltages and current as indicated.




V_o	I_x	V_3	V_2	V_1
-10V	0.4mA	-4V	2V	2V

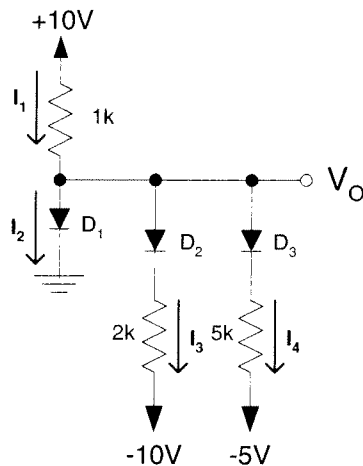Q2(a). [13 marks] Assume all diodes exhibit a constant 0.7 volt drop in forward bias mode. Find I_1 , I_2 , I_3 , I_4 & V_o as indicated and the state of the diodes.



ALL DIODES ARE ON.

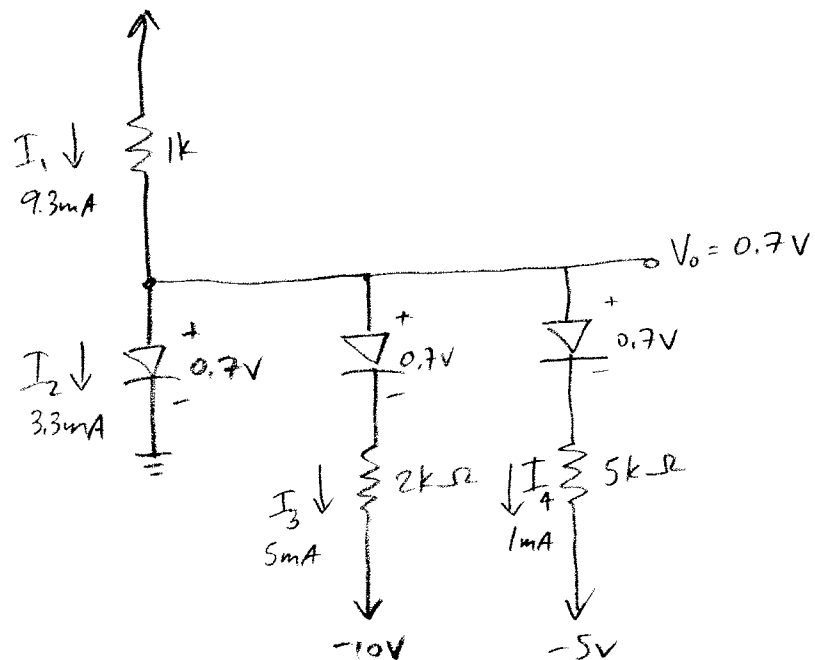

$$I_1 = \frac{10 - 0.7}{1k} = 9.3mA$$

$$I_3 = \frac{0.7 - 0.7 - (-10)}{2k} = 5mA$$

$$I_4 = \frac{0.7 - 0.7 - (-5)}{5k} = 1mA$$


$$I_1 = I_2 + I_3 + I_4$$

$$\therefore I_2 = 3.3mA$$

All diodes are forward biased and all currents are flowing into the anodes of all diodes.


I_1	I_2	I_3	I_4	D1	D2	D3	V_o
9.3mA	3.3mA	5mA	1mA	On Off	On Off	On Off	0.7V

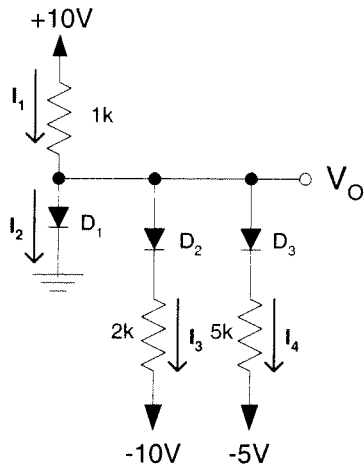Q2(a). [13 marks] Assume all diodes exhibit a *constant 0.7 volt drop in forward bias mode*. Find I_1 , I_2 , I_3 , I_4 & V_o as indicated and the state of the diodes.



V_o	D3	D2	D1	I_4	I_3	I_2	I_1
0.7V	On Off	On Off	On Off	1mA	5mA	3.3mA	9.3mA

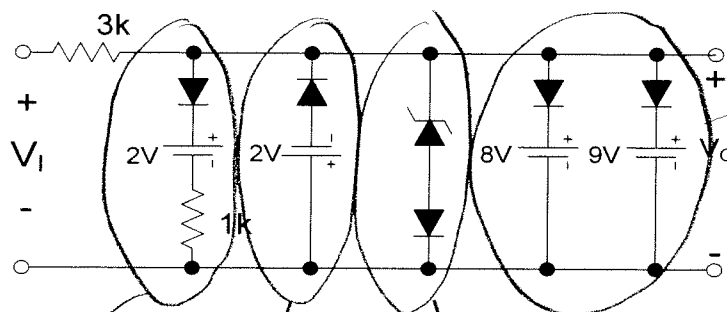
Q2(b). [15 marks] For the circuit shown, assume all diodes to be *ideal*. The Zener diode has a reverse breakdown voltage, $V_z = 4V$, and acts as an ideal diode in forward bias. Determine, and neatly sketch on the graph provided, the transfer characteristic (V_O vs V_I) of the circuit. Label all the *breakpoints* on both axes and *slopes* of the transfer characteristic.




both have
NO
EFFECT

limits
@ -2V

limits @ 4V

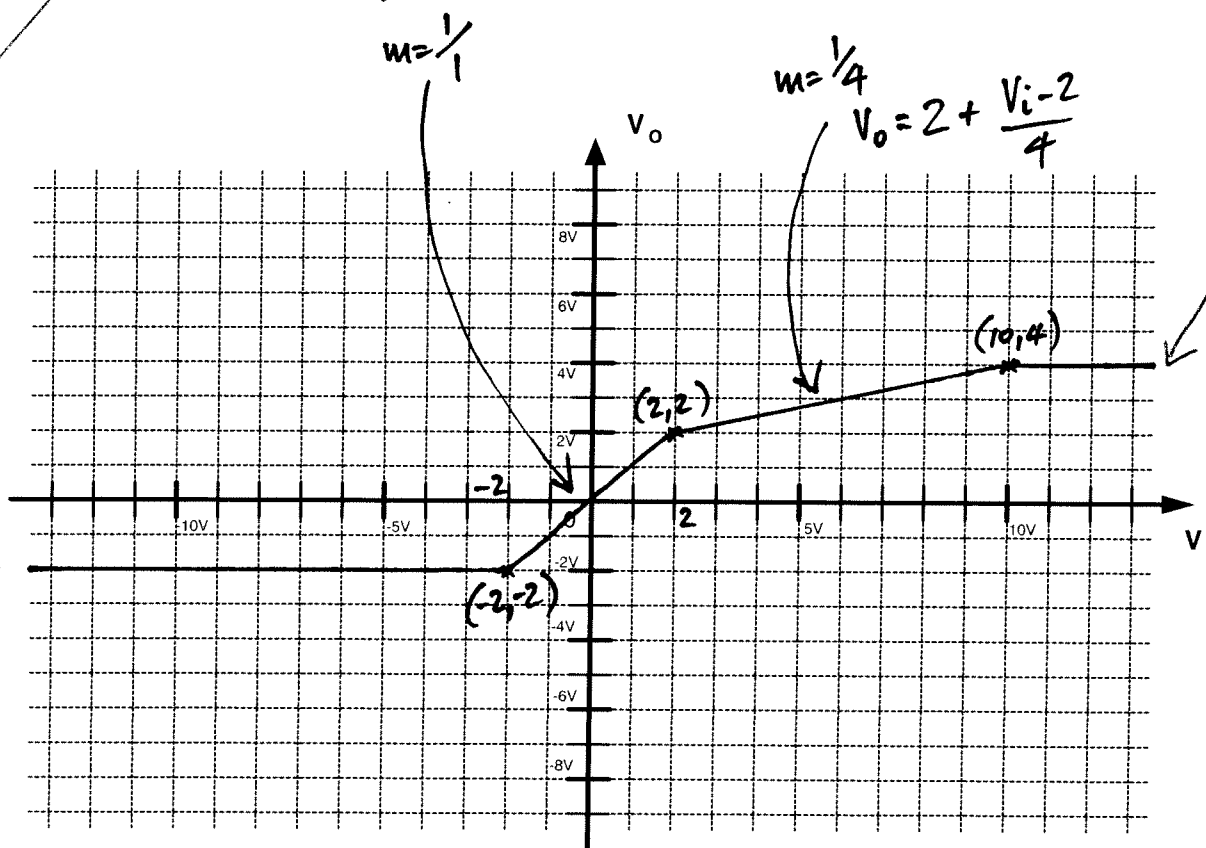

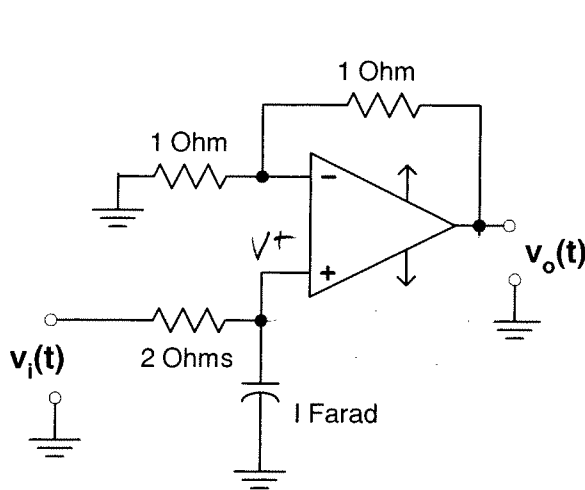Q3(a). [8 marks] For the circuit shown below, assume the Op-AMP and all components to be ideal. Develop the expression for the transfer function, $T(j\omega)$ $[= v_o(j\omega)/v_i(j\omega)]$. What function does this circuit perform?



$$V^+ = V_i(j\omega) \left(\frac{\frac{1}{j\omega}}{2 + \frac{1}{j\omega}} \right)$$


$$V_o = V^+ \left(1 + \frac{1\Omega}{1\Omega} \right) = 2V^+$$

$$V_o(j\omega) = 2 \left(V_i(j\omega) \left(\frac{\frac{1}{j\omega}}{2 + \frac{1}{j\omega}} \right) \right)$$

$$\therefore \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{2}{2j\omega + 1}$$

This circuit is a LOW-PASS filter

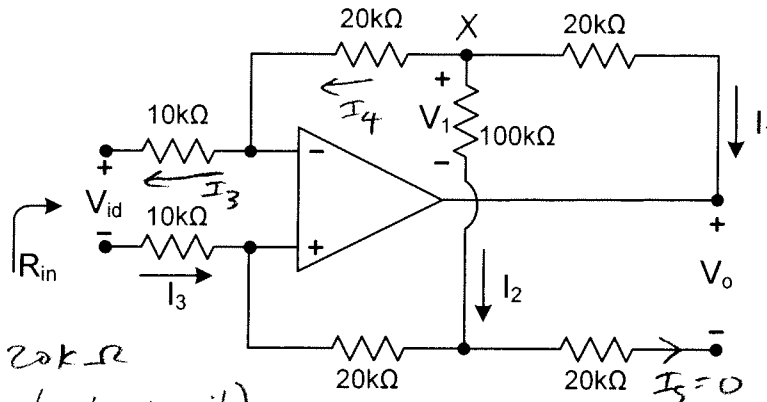Q3(b). [12 marks] For the circuit shown below, assume the Op-AMP and all components to be ideal. (i) Find the differential gain $A_{id} = V_o/V_{id}$, (ii) Find the labeled currents and voltages, V_1 , I_1 , I_2 and I_3 , if $V_{id}=6V$ (iii) Find R_{in} .



$$R_{in} = 10k\Omega + 10k\Omega = 20k\Omega$$

(due to virtual short circuit)

$$I_3 = -\frac{V_{id}}{20k} = -I_2 \quad (\text{since } I_5 = 0)$$

$$\text{Thus, } I_2 = \frac{V_{id}}{20k} = \frac{6V}{20k} = 0.3mA$$

$$I_3 = -0.3mA$$

$$\text{Also, } I_4 = I_3$$

KCL @ X gives:

$$I_1 + I_2 + I_4 = 0$$

$$I_1 = -(I_2 + I_4)$$

$$\text{but } I_4 = I_3 = -I_2$$

$$\text{So, } I_1 = -(I_2 - I_4)$$

$$I_1 = 0$$

$$\text{Since } I_5 = I_1 = 0,$$

$$V_o = V_1$$


$$V_1 = I_2 (100k\Omega) = (0.3mA)(100k)$$

$$V_1 = 30V = V_o$$

$$A_{id} = \frac{V_o}{V_{id}} = \frac{30V}{6V} = 5 V/V$$


R_{in}	I_3	I_2	I_1	V_1	A_{id}
$20k\Omega$	$-0.3mA$	$0.3mA$	0	$30V$	$5 V/V$

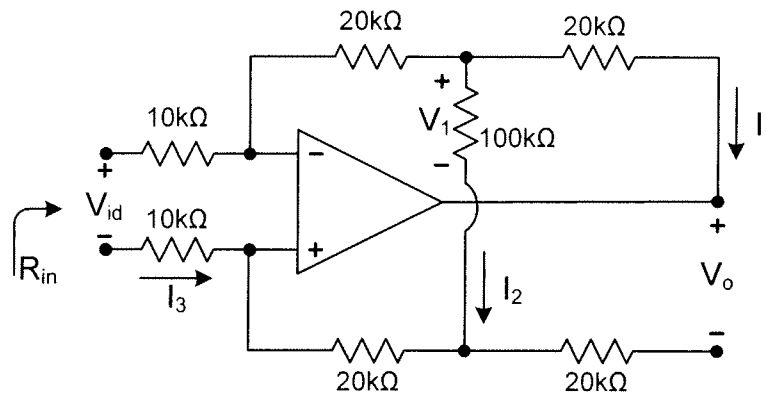Q3(b). [12 marks] For the circuit shown below, assume the Op-AMP and all components to be ideal. (i) Find the differential gain $A_{id} = V_o/V_{id}$, (ii) Find the labeled currents and voltages, V_1 , I_1 , I_2 and I_3 , if $V_{id}=6V$ (iii) Find R_{in} .



A_{id}	V_1	I_1	I_2	I_3	R_{in}
$5\sqrt{2}$	$30V$	0	$0.3mA$	$-0.3mA$	$20k\Omega$

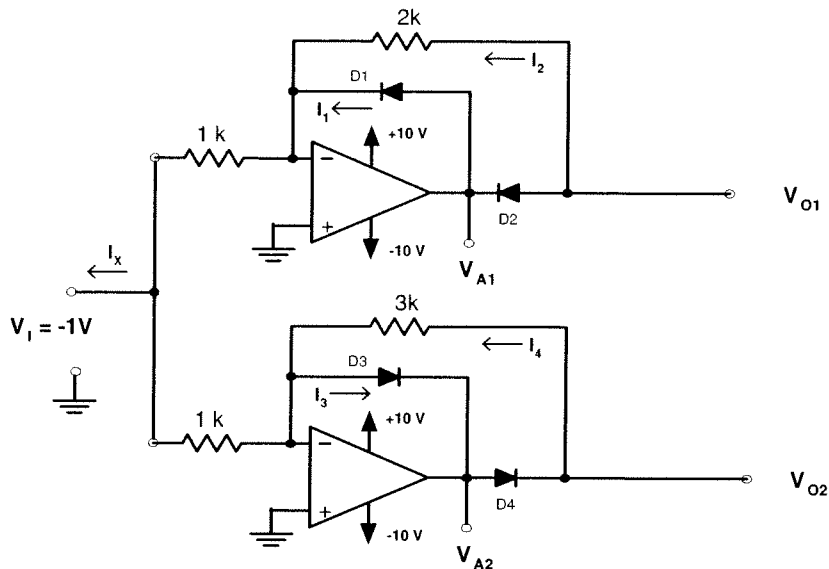Q4(a). [15 marks] For the circuit shown below, assume each diode exhibits a **0.7V** constant-voltage-drop in the forward-bias mode. For $V_I = -1V$, determine all voltages and currents as indicated, and the status of each diode (On or OFF).



$$D1 \text{ ON}, D2 \text{ OFF}, I_1 = \frac{0 - (-1)}{1k} = 1mA, I_2 = 0$$

$$V_{O1} = 0, V_{A1} = V_{D1} = 0.7V$$

$$D3 \text{ OFF}, D4 \text{ ON}, I_3 = 0, I_4 = \frac{0 - (-1)}{1k} = 1mA$$


$$V_{O2} = -1 \left(-\frac{3}{1} \right) = 3V$$

$$V_{O2} = V_{O2} + V_D = 3.7V$$

$$I_x = 2 \left(\frac{1}{1k} \right) = 2mA$$

V_I	I_x	I_1	I_2	V_{A1}	V_{O1}	I_3	I_4	V_{A2}	V_{O2}	D_1	D_2	D_3	D_4
-1V	2mA	1mA	0	0.7V	0	0	1mA	3.7V	3V	On	On	On	On
										Off	Off	Off	Off

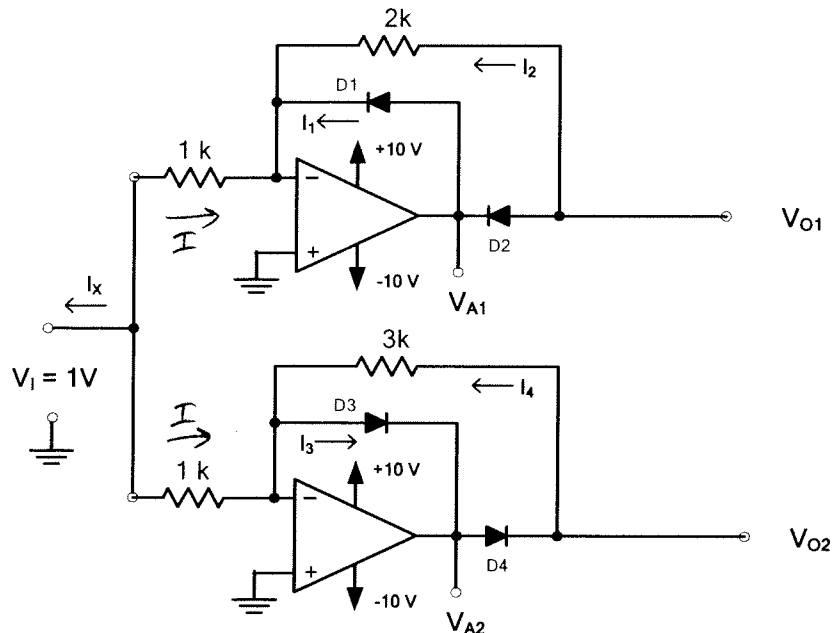Q4(a). [15 marks] For the circuit shown below, assume each diode exhibits a **0.7V** constant-voltage-drop in the forward-bias mode. For $V_I = +1V$, determine all voltages and currents as indicated, and the status of each diode (On or OFF).



$$D1 \text{ OFF}, D2 \text{ ON}, \quad I_2 = -\frac{1}{1k} = -1mA$$

$$V_{O1} = V_i \left(-\frac{R_2}{R_1} \right) = -2V$$

$$V_{A1} + V_{D2} - (I_2)2 = 0 \Rightarrow V_{A1} = -0.7 - (1)(2) = -2.7V$$


$$D3 \text{ ON}, D4 \text{ OFF}, \Rightarrow V_{O2} = 0, \quad V_{A2} = -V_{D3} = -0.7V$$

$$I_4 = 0, \quad I_3 = I = \frac{1}{1k} = 1mA$$

$$I_x = -(2I) = -2mA$$

V_I	D_4	D_3	D_2	D_1	V_{O2}	V_{A2}	I_4	I_3	V_{O1}	V_{A1}	I_2	I_1	I_x
1V	On (Off)	(On) Off	(On) Off	On (Off)	0	-0.7V	0	1mA	-2V	-2.7V	-1mA	0	-2mA

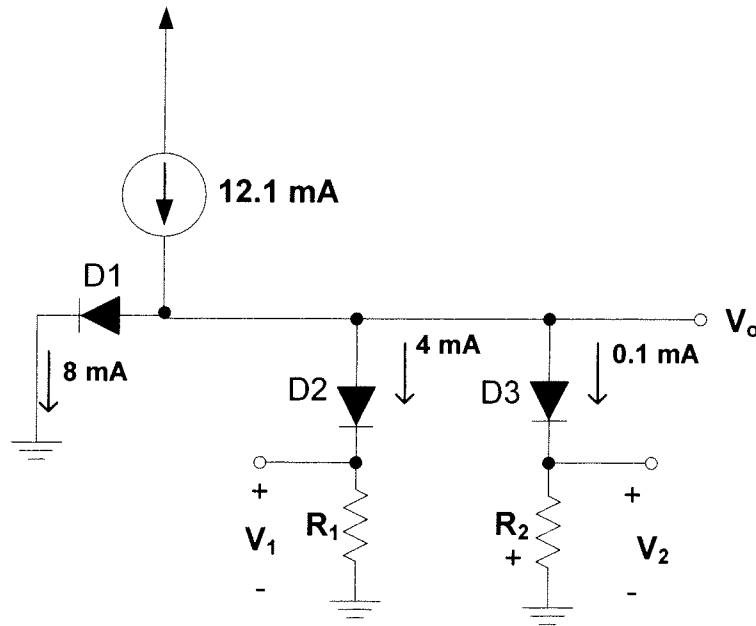Q4(b). [12 marks] For the circuit shown below, assume the diodes to be *identical*. The diode characteristic is such that it has a forward-bias voltage of **0.7V** at **1mA** current and its voltage changes by **0.1V** per decade change in current (note: $2.3nV_T = 0.1V$). Find the voltages as indicated.



$$V_0 = V_{D1} = 0.7 + 0.1 \log \frac{8}{1} = 0.79V$$

$$V_1 = V_0 - V_{D2}, \Rightarrow V_{D2} = 0.7 + 0.1 \log \frac{4}{1} = 0.76V$$

So,

$$V_1 = 0.79 - 0.76 = 0.03V$$


$$V_2 = V_0 - V_{D3} \Rightarrow V_{D3} = 0.7 + 0.1 \log \frac{0.1}{1} = 0.6V$$

So

$$V_2 = 0.79 - 0.6 = 0.19V$$

V_0	V_2	V_1
0.79V	0.19V	0.03V

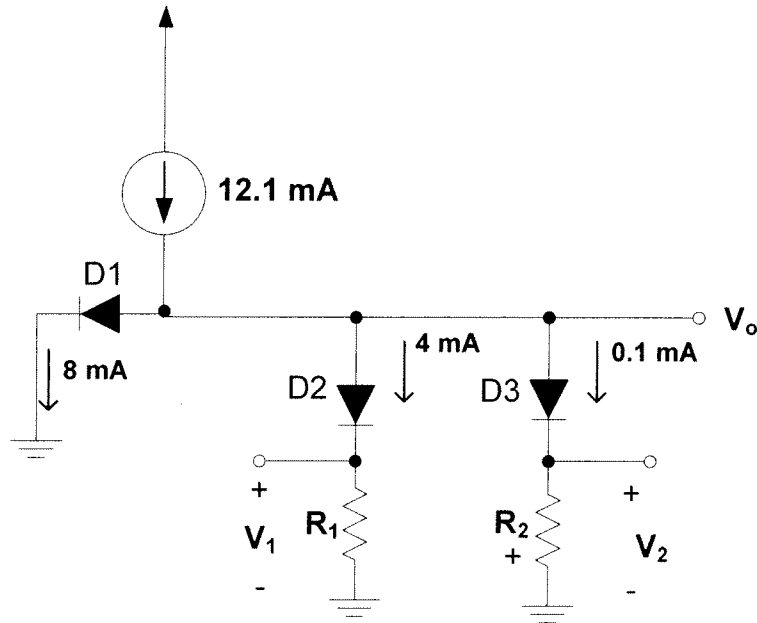Q4(b). [12 marks] For the circuit shown below, assume the diodes to be *identical*. The diode characteristic is such that it has a forward-bias voltage of **0.7V** at **1mA** current and its voltage changes by **0.1V per decade** change in current (note: $2.3nV_T = 0.1V$). Find the voltages as indicated.



V_1	V_2	V_0
0.03V	0.19V	0.79V

BLANK PAGE