

# SOLUTIONS, Midterm, F08

Department of Electrical and Computer Engineering

Ryerson University

ELE302: Electric Networks

## **Midterm Examination**

Duration: 1.5 hours

October 14, 2008

**Student's Name:** .....

**Student Number:** .....

**Section:** .....

Dr.Karim


Dr.Venkatesh

**Note:**

1. Please check your professor's name above.
2. **Answer all questions**

Questions	Marks	Marks obtained
Q1	20	
Q2	15	
Q3	15	
Q4	20	
Total	70	

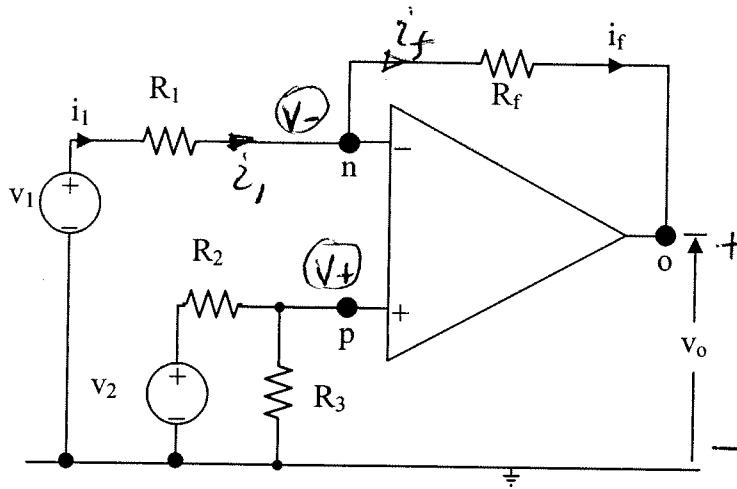Q1. Derive an expression for  $v_o$  in terms of  $v_1$  and  $v_2$ .



Given:

$$R_1 = 10 \text{ k}\Omega$$

$$R_2 = 10 \text{ k}\Omega$$

$$R_3 = 10 \text{ k}\Omega$$

$$R_f = 100 \text{ k}\Omega$$

Solution: By voltage division principle,  $V_+ = \frac{R_3}{(R_2 + R_3)} \cdot V_2$

(5) For the ideal opamp  $V^- = V^+ = \frac{R_3}{(R_2 + R_3)} \cdot V_2$

By KCL:  $i_1 = i_f$

$$\frac{V_1 - V^-}{R_1} = \frac{V^- - V_o}{R_f}$$

(5)

$$R_f(V_1 - V^-) = R_1(V^- - V_o) = R_1 V^- - R_1 V_o$$

$$\therefore V_o = \frac{1}{R_1} (R_f + R_1) V^- - \left( \frac{R_f}{R_1} \right) V_1$$

$$V_o = \frac{1}{R_1} (R_f + R_1) \cdot \frac{R_3}{(R_2 + R_3)} V_2 - \left( \frac{R_f}{R_1} \right) V_1$$

$$V_o = \frac{R_3}{R_1} \cdot \frac{(R_f + R_1)}{(R_2 + R_3)} V_2 - \left( \frac{R_f}{R_1} \right) V_1$$

$$V_o = \frac{10}{10} \cdot \frac{(100 + 10)}{(10 + 10)} V_2 - \left( \frac{100}{10} \right) V_1$$

(10)

$$V_o = 5.5 V_2 - 10 V_1$$

Q2. Draw Bode Plots (both Amplitude and Phase plots) for the following transfer function:

$$H(j\omega) = \frac{1000 \cdot (j\omega)}{(5 + j\omega) \cdot (20 + j\omega)}$$

Use to semi-log sheet for your sketch

Solution:

$$H(j\omega) = \frac{1000 \cdot j\omega}{5(1 + j\frac{\omega}{5}) 20(1 + j\frac{\omega}{20})} = \frac{10 \cancel{000} \cdot j\omega}{\cancel{1000} (1 + j\frac{\omega}{5}) (1 + j\frac{\omega}{20})}$$


(5)

$$H(j\omega) = \frac{10 \cdot j\omega}{(1 + j\frac{\omega}{5}) (1 + j\frac{\omega}{20})}$$

$$10 \Rightarrow 20 \log_{10} 10 = 20 \text{ dB}$$


Q2  
(contd)

(5)

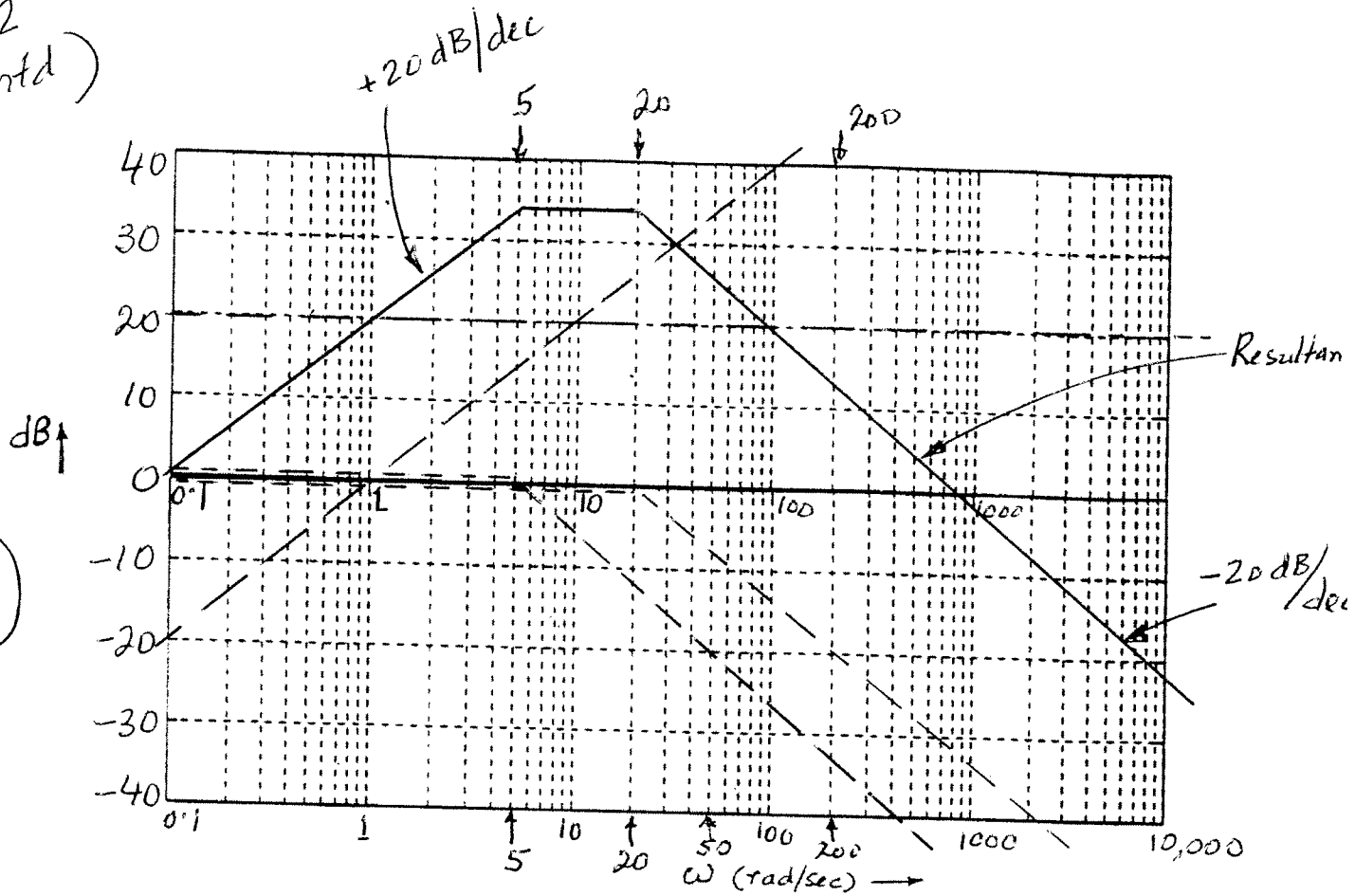


(5)

$\theta$   
(deg)

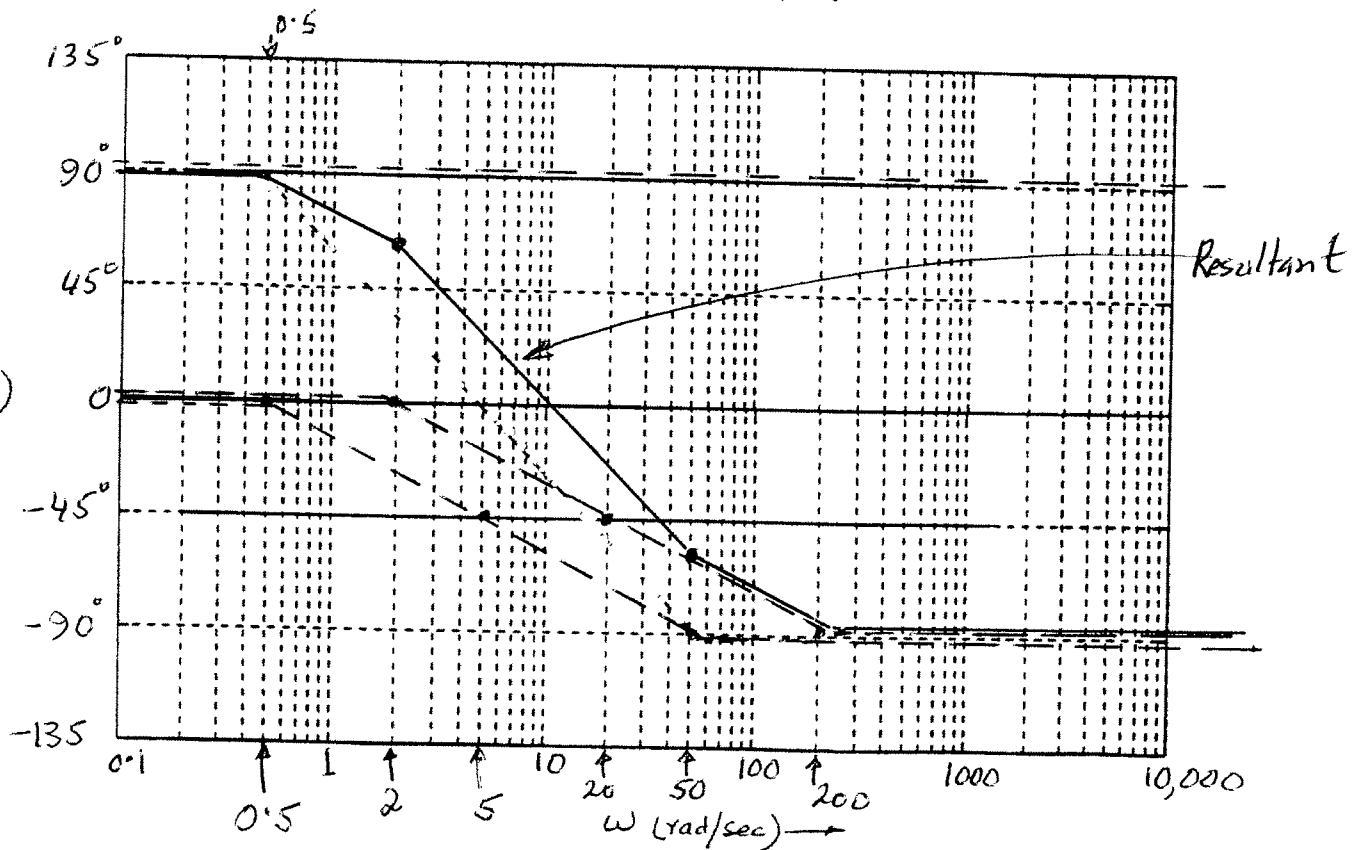

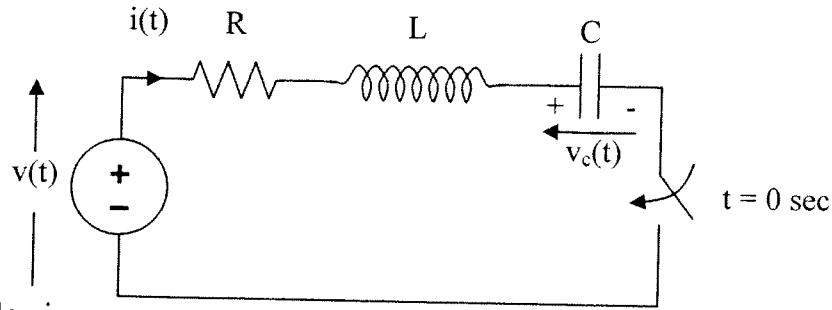Q3.  $R = 200 \Omega$ ;  $L = 10 \text{ H}$ ,  $C = 10 \mu\text{F}$  and  $v(t) = 10\text{V}$ . For the circuit shown above, it is given that  $v_c(0^-) = 5\text{V}$ .



Answer the following:

a) write a differential equation of  $i(t)$ .

$$V = Ri' + L \frac{di'}{dt} + v_c(0) + \frac{1}{C} \int_0^t i' dt$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} = \frac{1}{L} \frac{dV}{dt} \quad (5)$$

$$R/L = 20, \quad \frac{1}{LC} = 10^4, \quad \frac{1}{L} = 0.1$$

b) Write characteristic equation and its natural solution.

$$s^2 + 20s + 10^4 = 0 \quad \alpha = 10, \omega_0 = 100$$

$$s_1, s_2 = -10 \pm \sqrt{10^2 - 10^4}$$

$$= -10 \pm j\sqrt{9900}$$

$$i_N = A e^{-10t} \cos(\sqrt{9900}t + \phi)$$

c) determine initial conditions and

$$i_L(0) = 0, \quad V_C(0) = 5V \quad (1)$$

$$10 = R \cdot i_L(0) + L \frac{di_L}{dt} + V_C(0)$$

$$10 - 5 = 10 \cdot \frac{di_L}{dt} \quad \therefore \frac{di_L}{dt} = 0.5 A/s \quad (1)$$

d) find  $i(t), t \geq 0$

$$i = i_n + i_f = A \cdot e^{-10t} \cos(\omega t + \phi)$$

$$i(0) = \cancel{-10} A \cos \phi = 0 \quad (1)$$

$$\frac{di}{dt} = -A \cdot 10 \cos(\phi) - A \cdot \sin(\phi) \cdot \omega = 0.5 \quad (1)$$

$$\phi = 90^\circ$$


$$-A \sin \phi \cdot \omega = 0.5$$

$$\therefore A = \frac{-0.5}{\sqrt{9900}} \quad (1)$$

$$i = \frac{-0.5}{\sqrt{9900}} e^{-10t} \cos(\sqrt{9900} t + 90^\circ)$$

$$= (0.5 / \sqrt{9900}) e^{-10t} \sin(\sqrt{9900} t)$$

Q4. For the circuit shown below

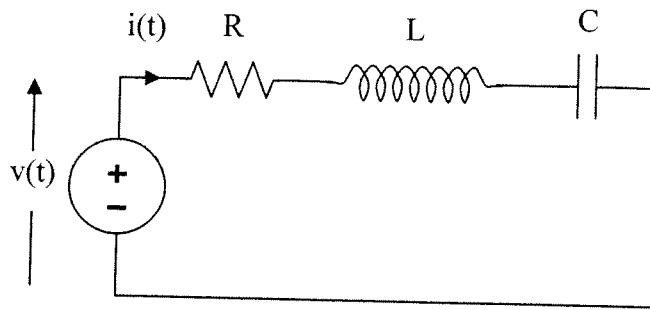

Given:  $R = 10\Omega$ ,  $L = 0.01$ ;  $C = 0.01$  F

Answer the following:

a) Find resonant frequency ( $\omega_0$ )

$$\omega_0 = \frac{1}{\sqrt{LC}} = 100 \text{ rad/sec.}$$

(4)

b) Find two half power frequencies ( $\omega_1, \omega_2$ )

$$\omega_1, \omega_2 = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 + 1/LC}$$

(2)

$$= 9.9020, 1009.9 \text{ rad/sec}$$

c) Find quality factor (Q)

$$= \omega_0 / (R/L)$$

$$= 0.1$$

(4)

d) Find band width (B)

$$= \omega_2 - \omega_1 = 1000 \text{ rad/sec}$$

(4)