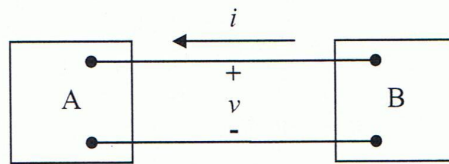


Q1(i):

Two electric circuits represented by boxes A and B are connected as shown in the following figure. For each of the following sets of numerical values, calculate the power in the interconnection and state whether the power is flowing from A to B or vice versa (3 marks each).

- (a) $i = 10 \text{ A}$, $v = 125 \text{ V}$
- (b) $i = 5 \text{ A}$, $v = -240 \text{ V}$
- (c) $i = -12 \text{ A}$, $v = 480 \text{ V}$
- (d) $i = -25 \text{ A}$, $v = -660 \text{ V}$



- (a) $10 \times 125 = 1250 \text{ watts}$
- (b) ~~1250~~
 $5 \times (-240) = -1200 \text{ watts}$
- (c) $-12 \times 480 = -5760 \text{ watts}$
- (d) $-25 \times (-660) = 16500 \text{ watts}$

(a) 1250 W B → A



(b) 1200 W A → B

(c) 5760 W A → B

(d) 16500 W B → A

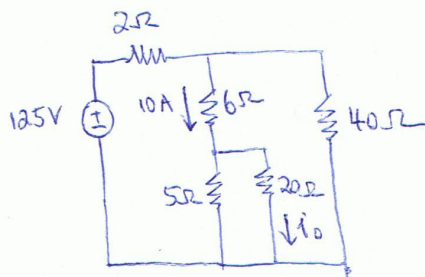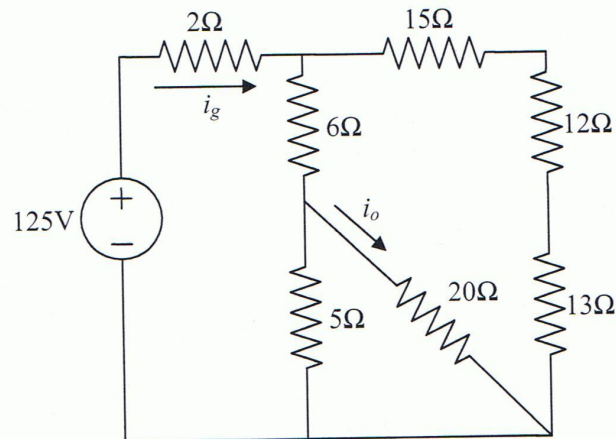Q1(ii):




Find i_o and i_g in the following circuits (6.5 marks for each current).



$$i_g = \frac{125V}{10\Omega} = 12.5A$$

$$i_1 = 12.5 \times \frac{40}{10+40} = 10A$$

$$i_o = 10 \times \frac{20}{5+20} = 8A$$

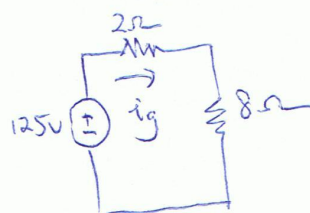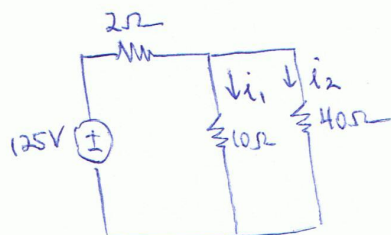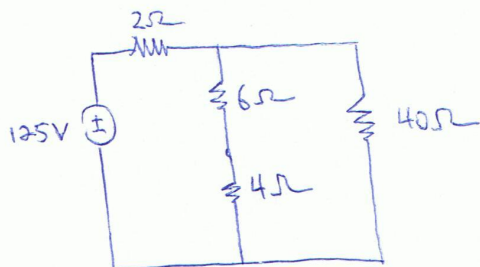


$$i_g = 12.5A$$


$$i_o = 8A$$

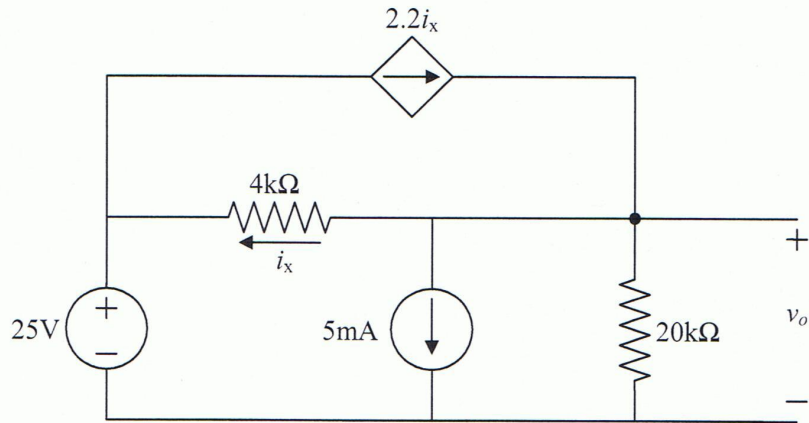Q2:

Using superposition to find v_o in the following circuit.



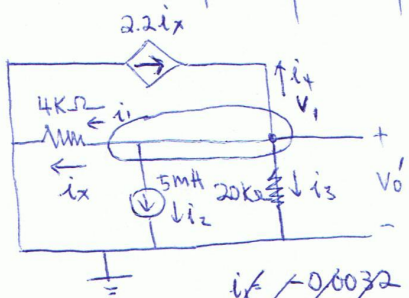Disable 25V \Rightarrow $\begin{matrix} + \\ - \end{matrix} 0 \Rightarrow$



$$\begin{aligned} i_1 &= -0.0032 \\ i_2 &= 0.005 \\ i_3 &= -0.00064 \\ i_4 &= i_1 \end{aligned}$$

$$i_1 + i_2 + i_3 + i_4 = 0$$

$$\frac{V_1}{4000} + 5\text{mA} + \frac{V_1}{20000} - 2.2 \cdot \frac{V_1}{4000} = 0$$

$$i_x = \frac{V_1}{4000}$$

$$\frac{V_1}{4000} + 0.005 + \frac{V_1}{20000} - \frac{2.2V_1}{4000} = 0$$

$$5V_1 + 0.005 \times 20000 + V_1 - 5 \cdot 2.2V_1 = 0$$

$$5V_1 + 100 + V_1 - 11V_1 = 0$$

$$\cancel{(5+1-11)V_1 = -100}$$

$$\cancel{5.2V_1 = -100}$$

$$V_1 = \frac{-100}{5.2} = -19.23 \text{ volts}$$

$$(5+1-5 \times 2.2)V_1 + 100 = 0$$

$$-(6-11)V_1 = 100$$

$$V_1 = \frac{100}{5}$$

$$= 20 \text{ volts}$$

$$i_1 = \frac{20}{4000} = 0.005$$

$$i_2 = 0.005$$

$$i_3 = \frac{20}{20000} = 0.001$$

$$i_4 = -0.005 \times 2.2$$

$$= -0.011$$

$$i_1 + i_2 + i_3 + i_4 = 0.005 + 0.005 + 0.001 - 0.011$$



$$= 0.010 + 0.001 - 0.011$$

$$= 0$$

$$V_o' = V_1 = 20 \text{ volts}$$

$$v_o = V_o' + V_o'' = 20 + 30 \text{ volts} = 50 \text{ volts}$$

Blank page

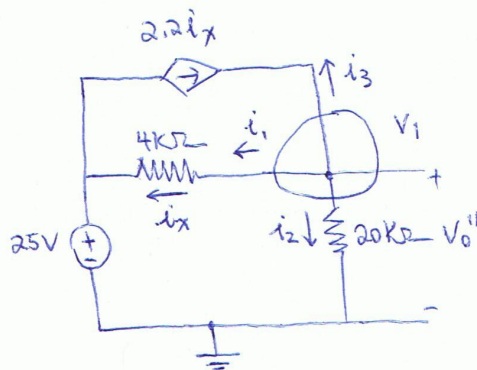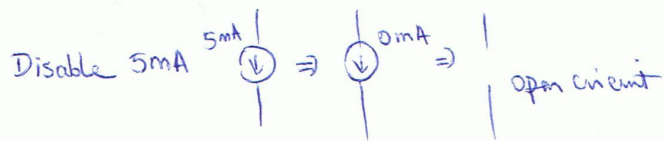

$$i_1 + i_2 + i_3 = 0$$

$$V_0'' = V_1 = 30 \text{ volts}$$

$$\left\{ \begin{aligned} \frac{V_1 - 25}{4000} + \frac{V_1}{20000} - 2.2 \cdot i_x &= 0 \end{aligned} \right.$$

$$i_x = i_1 = \frac{V_1 - 25}{4000}$$

$$\downarrow \quad \frac{V_1 - 25}{4000} + \frac{V_1}{20000} - \frac{2.2(V_1 - 25)}{4000} = 0$$

$$5V_1 - 125 + V_1 - 11V_1 + 275 = 0$$

$$(5 + 1 - 11)V_1 + 150 = 0$$

$$-5V_1 + 150 = 0$$

$$V_1 = 30 \text{ volts}$$


$$i_1 = \frac{30 - 25}{4000} = 0.00125 \text{ A}$$

$$i_2 = \frac{30}{20000} = 0.0015 \text{ A}$$

$$i_3 = -2.2 \cdot 0.00125 = -0.00275$$

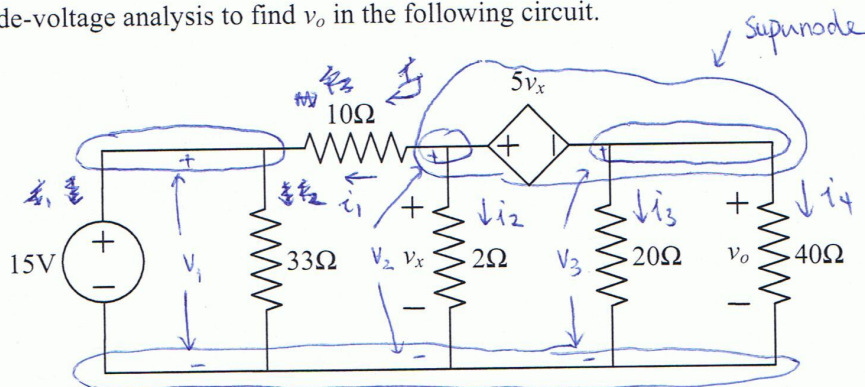Q3:

Use node-voltage analysis to find v_o in the following circuit.



$$i_1 + i_2 + i_3 + i_4 = 0$$

$$V_1 = 15$$

$$i_1 + i_2 + i_3 + i_4 = 0$$

$$\frac{V_2 - 15}{10} + \frac{V_2}{2} + \frac{V_3}{20} + \frac{V_3}{40} = 0$$

$$4V_2 - 60 + 20V_2 + 2V_3 + V_3 = 0$$

$$24V_2 + 3V_3 = 60$$

$$8V_2 + V_3 = 20 \quad (1)$$

Sub(3) into (1)

$$8V_2 + (-4V_2) = 20$$

$$4V_2 = 20$$

$$V_2 = 5 \text{ volts (4)}$$

Sub(4) into (3)

$$V_3 = -4 \times 5$$

$$V_3 = -20 \text{ volts}$$

$$V_3 + 5V_x = V_2$$

$$V_2 = V_x$$

$$V_3 + 5V_2 = V_2$$

$$V_3 + 4V_2 = 0$$

$$4V_2 + V_3 = 0 \quad (2)$$

$$-4V_2 = V_3 \quad (3)$$

$$i_1 = \frac{5 - 15}{10} = -1 \text{ A}$$

$$i_2 = \frac{5}{2} = 2.5 \text{ A}$$

$$i_3 = \frac{-20}{20} = -1 \text{ A}$$



$$i_4 = \frac{-20}{40} = -0.5 \text{ A}$$

$$-1 + 2.5 - 1 - 0.5 = 0 \text{ check.}$$

$$V_o = V_3 = -20 \text{ volts.}$$

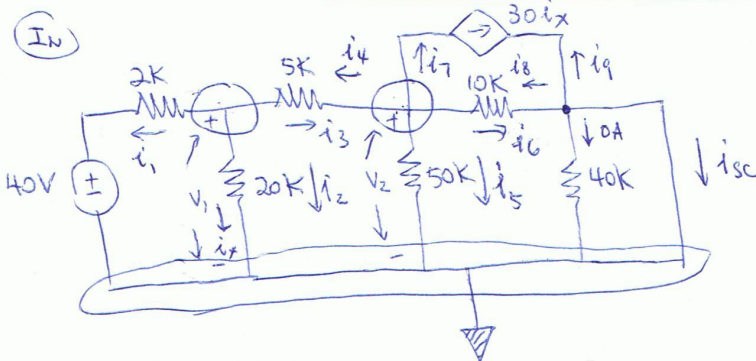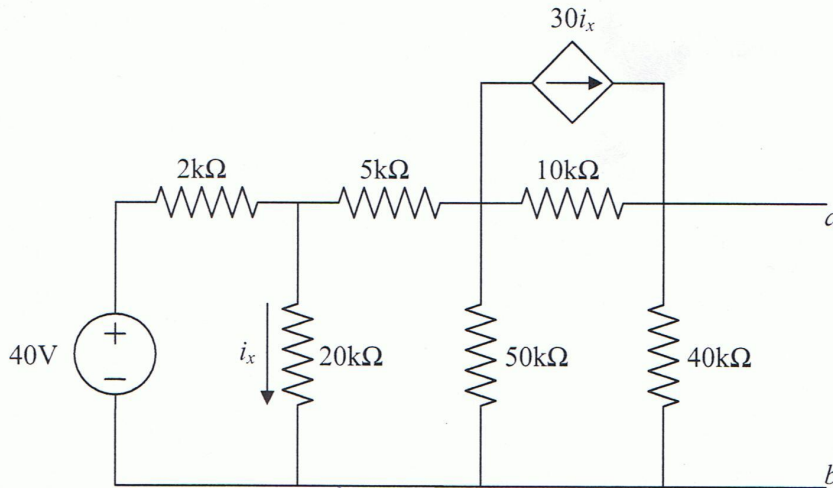Q4:

Find the Norton equivalent between terminals $a-b$ of the following circuit:



$$i_{sc} + i_8 + i_9 = 0$$

$$i_{sc} + \frac{0 + 52}{10000} - 30 \cdot i_x = 0 \quad \rightarrow 0.0192A$$

$$i_{sc} + \frac{52}{10000} - 30 \cdot \frac{12.8}{20000} = 0$$

$$+0.0052 \quad i_{sc} = \frac{-0.0244 \text{ Amps}}{0.014 \text{ Amps}}$$

$$\frac{V_1 - 40}{2000}$$

$$i_1 + i_2 + i_3 = 0$$

$$\frac{V_1 - 40}{2000} + \frac{V_1}{20000} + \frac{V_1 - V_2}{5000} = 0$$

$$10V_1 - 400 + V_1 + 4V_1 - 4V_2 = 0$$

$$15V_1 - 4V_2 = 400 \quad (1)$$

$$V_1 = 12.8 \text{ volts}$$

$$V_2 = -52 \text{ volts}$$

$$i_4 + i_5 + i_6 + i_7 = 0$$

$$\frac{V_2 - V_1}{5000} + \frac{V_2}{50000} + \frac{V_2}{10000} + 30i_x = 0$$

$$i_x = \frac{V_1}{20000}$$

$$\frac{V_2 - V_1}{5000} + \frac{V_2}{50000} + \frac{V_2}{10000} + 30 \frac{V_1}{20000} = 0$$

$$20V_2 - 20V_1 + 2V_2 + 10V_2 + 150V_1 = 0$$

$$130V_1 + 32V_2 = 0 \quad (2)$$


$$i_4 = \frac{-52 - 12.8}{5000} = -0.01296A$$

$$i_5 = \frac{-52}{50000} = -0.00104A$$

$$i_6 = \frac{-52}{10000} = -0.0052A$$

$$i_7 = 30 \cdot \frac{12.8}{20000} = 0.0192A$$
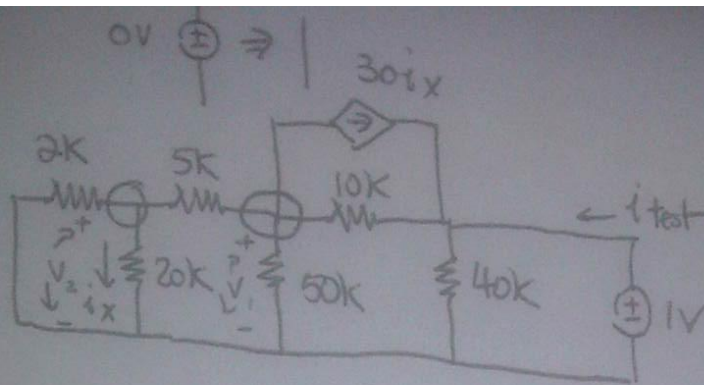
$$\left. \begin{aligned} i_1 &= \frac{12.8 - 40}{2000} = -0.0136 \\ i_2 &= \frac{12.8}{20000} = 0.00064 \\ i_3 &= \frac{12.8 + 52}{5000} = 0.01296 \end{aligned} \right\} \checkmark$$



$$\frac{V_1 - V_2}{5} + \frac{V_1 - 1}{10} + 30i_x + \frac{V_1}{50} = 0$$

$$\frac{V_1 - V_2}{5000} + \frac{V_1 - 1}{10000} + 30i_x + \frac{V_1}{50000} = 0$$

$$50000 \left(\frac{V_1 - V_2}{5000} + \frac{V_1 - 1}{10000} + 30i_x + \frac{V_1}{50000} \right) = 0$$

$$10(V_1 - V_2) + 5(V_1 - 1) + 50000 \cdot 30i_x + V_1 = 0$$

$$\underline{10V_1 - 10V_2 + 5V_1 - 5 + 1500000i_x + V_1 = 0}$$

$$16V_1 - 10V_2 + 1500000i_x = 5 \quad (1)$$

$$\frac{V_2}{2000} + \frac{V_2}{20000} + \frac{V_2 - V_1}{5000} = 0$$

$$\frac{V_2}{2} + \frac{V_2}{20} + \frac{V_2 - V_1}{5} = 0$$

$$20 \left(\frac{V_2}{2} + \frac{V_2}{20} + \frac{V_2 - V_1}{5} \right) = 0$$

$$\underline{10V_2 + V_2 + 4V_2 - 4V_1 = 0}$$

$$4V_1 = 15V_2$$

$$\frac{4}{15} V_1 = V_2 \quad (2)$$

$$i_x = \frac{V_2}{20000}$$

$$i_x = \frac{4}{15} \frac{V_1}{20000} \quad (3)$$

Sub (2) & (3) into (1)

$$16V_1 - 10 \left(\frac{4}{15} V_1 \right) + \frac{100 \cdot 5}{500,000} \cdot \frac{4}{15} \cdot \frac{1}{20,000} \cdot V_1 = 5$$

$$16V_1 - \frac{40}{15} V_1 + 20V_1 = 5$$


$$16V_1 - \frac{8}{3} V_1 + 20V_1 = 5$$

$$48V_1 - 8V_1 + 60V_1 = 15$$

$$100V_1 = 15$$

$$V_1 = 0.15$$
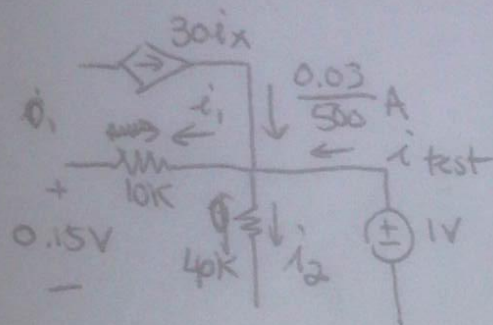
$$\Rightarrow i_x = \frac{4}{15} \frac{0.15}{20,000} = \frac{4 \cdot 0.01}{20,000} = \frac{0.01}{5,000} \text{ A}$$



$$30i_x = 30 \cdot \frac{0.01}{5,000} = \frac{0.03}{500} \text{ A}$$

$$i_1 = \frac{1 - 0.15}{10K} = \frac{0.85}{10K}$$

$$i_2 = \frac{1}{40K}$$

$$\frac{40000}{500} = 80$$

$$\frac{0.03}{500} + i_{test} = \frac{0.85}{10K} + \frac{1}{40K}$$

$$40000 \left(\frac{0.03}{500} + i_{test} \right) = 40000 \left(\frac{0.85}{10000} + \frac{1}{40000} \right)$$

$$80 \cdot 0.03 + 40,000 i_{test} = 4 \cdot 0.85 + 1$$

$$2.4 + 40,000 i_{test} = 4.4$$

$$40,000 i_{test} = 4.4 - 2.4$$

$$i_{test} = \frac{2}{40,000}$$

$$R_{th} = \frac{1}{i_{test}} = \frac{40,000}{2} = 20,000 = 20K$$

Answer $R_{th} = 20K$