

Final Answers Only

Ryerson University
Department of Electrical and Computer Engineering

ELE404 (Electronic Circuits I)

Makeup Midterm Examination (W2014)

March 2014

Duration: 100 minutes

Examiner: Prof. A. Yazdani

Name:.....
[Print Last Name] [Print First Name]

Student No:..... Section:....

NOTES

1. This is a closed-book examination. No aids other than basic calculators are permitted.
2. The examination paper is comprised of **FIVE QUESTIONS**, each question is worth as indicated in the following Table. The entire examination is worth 100 marks.

Question #	Maximum Mark	Mark Earned
1	30	
2	15	
3	20	
4	15	
5	20	
Total	100	

3. Answer all questions in the booklet, within the blank spaces provided under each question in this booklet. Use the reverse if needed.
4. **No Questions to be asked during the examination.** If in doubt about any question, clearly state your assumptions in answering the question.
5. Part marks for an answer will only be given if the *correct methodology* is clearly shown.
6. **DO NOT DETACH** any pages from this booklet.

Q1: In the diode circuit of **Fig. 1**, D_1 is a regular diode whose forward voltage drop is assumed to be 0.7 V , whereas D_2 is an LED that starts to glow when its forward voltage drop reaches about 2.2 V . Further, $V_{CC} = 10\text{ V}$, $R_1 = 1.0\text{ k}\Omega$, $R_2 = 2.0\text{ k}\Omega$, and $I_x = 4.0\text{ mA}$. It is assumed that neither diode enters the breakdown region.

1a) If the voltage V_x is so negative that the LED is ^{off}~~dim~~, determine the conduction state ("on" or "off") of D_1 , and calculate the voltages V_3 and V_4 . Summarize your findings in **Table 1a**.

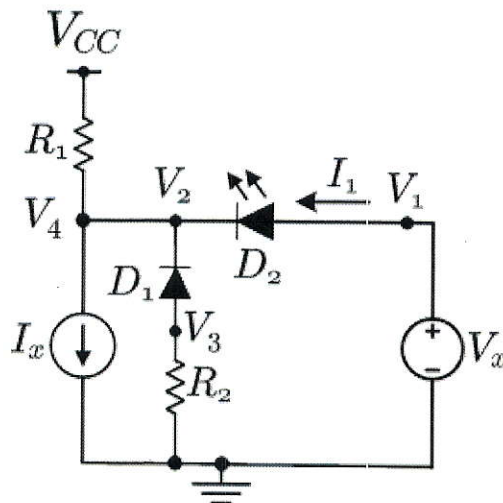


Fig. 1: Diode circuit of Q1.

Table 1a: Results of the diode circuit of Q1.

State of D_1	V_3 [V]	V_4 [V]
OFF	0	6

- 1b) V_x is then raised to 10.2 V and the LED glows. For this operating condition, calculate I_1 , V_2 , and V_3 . Complete **Table 1b**.

Table 1b: voltage values corresponding to $V_x = 10.2$ V.

I_1 [mA]	V_2 [V]	V_3 [V]
2.0	8.0	0

Q2: In the circuit of **Fig. 2**, $V_{CC} = 15\text{ V}$, $I = 1.5\text{ mA}$, and $R = 3.3\text{ k}\Omega$. If $V_O = 5.7\text{ V}$ at a temperature of 20°C , what will V_O be the 40°C ? At 0°C ? At 80°C ? Explain why and/or show the calculations. Summarize your results in **Table 2**. [*Hint*: the voltage drop across the resistor is proportional to the current of the diode].

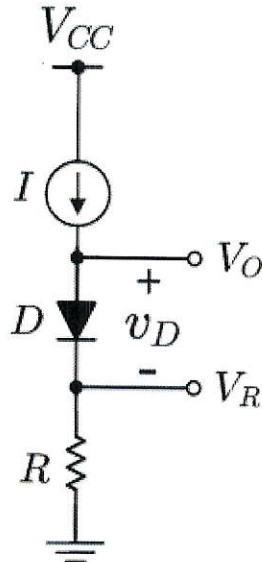


Fig. 2: Diode circuit of Q2.

Table 2: Results of the diode circuit of Q2.

$T [^\circ\text{C}]$	20	40	0	80
$V_O [\text{V}]$	5.7	5.66	5.74	5.58

Q3: Fig. 3 shows a full-wave rectifier with smoothing capacitor. A gross manufacturing error has resulted in the connection of a grounded load to the anode (as opposed to the cathode) of D_1 . The source voltage v_I is a 5-Vrms sinusoid, $C = 680 \mu F$, and $R_L = 1.2 k\Omega$. The diodes may be assumed ideal.

Assuming that the circuit has reached a steady state, determine the reading of a dc voltmeter of the voltages v_O and v_L . Show all the work. **Box your answers.**

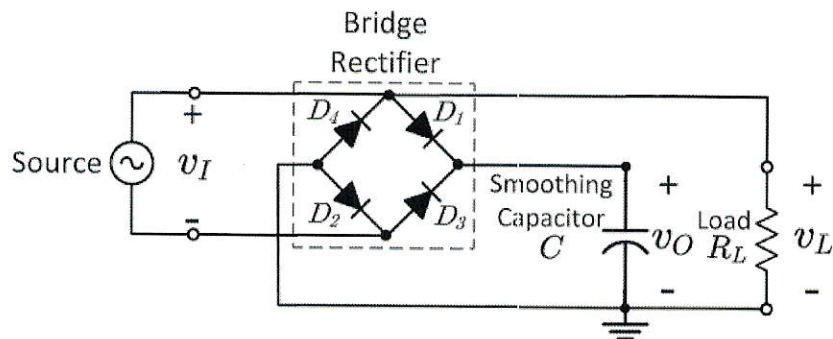


Fig. 3: Full-wave rectifier of Q3.

$$\overline{v_O} = 7.0 V$$

$$\overline{v_L} = 2.23 V$$

Q4: In the shunt voltage regulator of **Fig. 4**, $R = 330\ \Omega$, and the unregulated voltage v_{rec} is the output of a full-wave rectifier and, therefore, has an almost triangular waveform. According to the manufacturer, the Zener diode gives a voltage of $v_Z = V_{ZT} = 5.6\text{ V}$ at a test current of $i_Z = I_{ZT} = 25\text{ mA}$, and the diode can tolerate a maximum current of $I_{Zmax} = 100\text{ mA}$. Further, $r_Z = 15\ \Omega$ and $I_{ZK} = 1.5\text{ mA}$.

If the reading of a dc voltmeter of v_O is 5.9 V , and if v_O has a peak-to-peak ripple of 100 mV , determine the minimum and maximum values of v_{rec} .

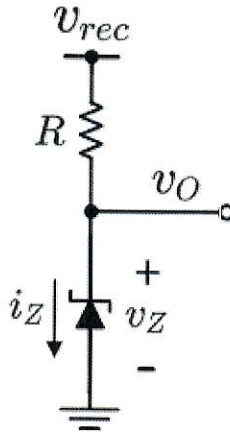


Fig. 4: Shunt regulator of Q4.

$$v_{rec, \min} = 19.6\text{ V}$$

$$v_{rec, \max} = 21.9\text{ V}$$

Q5: In the transistor circuit of **Fig. 5**, determine the mode of operation of the transistor and the node voltages, if $V_{EE} = 5\text{ V}$, $-V_{CC} = -V_{BB} = -10\text{ V}$, $R_1 = R_4 = 1.0\text{ k}\Omega$, $R_2 = 3.3\text{ k}\Omega$, and $R_3 = 1.5\text{ M}\Omega$. Assume that $V_{EBon} = 0.7\text{ V}$, $V_{ECsat} = 0.3\text{ V}$, and $\beta = 100$.

Show all the work, and complete **Table 5**.

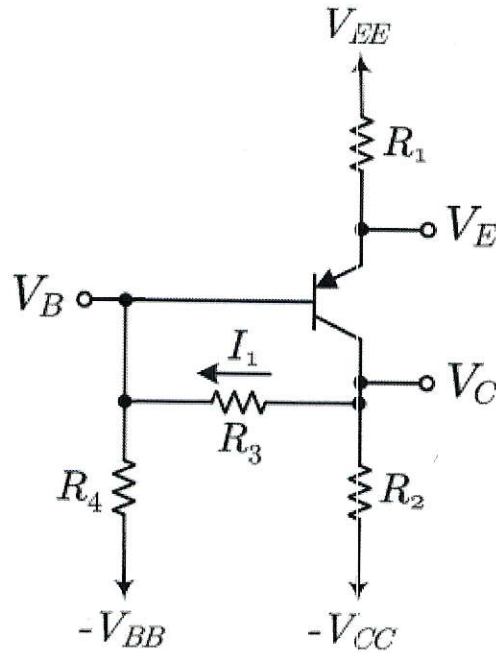


Fig. 5: Transistor circuit of Q5.

Table 5: transistor's mode of operation and the node voltages in the circuit of Q5.

Mode of Q1	$v_B[\text{V}]$	$v_C[\text{V}]$	$v_E[\text{V}]$
Saturation	-3.85	-3.45	-3.15