

# Solution & Grading

**Ryerson University**  
Department of Electrical and Computer Engineering  
**ELE404 (Electronic Circuits I)**  
**Midterm Examination (W2014)**  
**February 2014**  
**Duration: 100 minutes**  
Examiner: Prof. A. Yazdani

Name:.....  
[Print Last Name] [Print First Name]

Student No:..... Section:....

## **NOTES**

1. This is a closed-book examination. No aids other than basic calculators are permitted.
2. The examination paper is comprised of **FIVE QUESTIONS**, each question is worth as indicated in the following Table. The entire examination is worth 100 marks.

Question #	Maximum Mark	Mark Earned
1	30	
2	15	
3	20	
4	15	
5	20	
Total	100	

3. Answer all questions in the booklet, within the blank spaces provided under each question in this booklet. Use the reverse if needed.
4. **No Questions to be asked during the examination.** If in doubt about any question, clearly state your assumptions in answering the question.
5. Part marks for an answer will only be given if the *correct methodology* is clearly shown.
6. **DO NOT DETACH** any pages from this booklet.

Q1: In the diode circuit of **Fig. 1**,  $D_1$  is a regular diode whose forward voltage drop is assumed to be  $0.7\text{ V}$ , whereas  $D_2$  is an LED that starts to glow when its forward voltage drop reaches about  $2.2\text{ V}$ . Further,  $R_1 = 1.0\text{ k}\Omega$ ,  $R_2 = 2.0\text{ k}\Omega$ , and  $I_x = 4.0\text{ mA}$ . It is assumed that neither diode enters the breakdown region.

1a) If the voltage  $V_x$  is so negative that the LED is <sup>dark</sup>~~on~~, determine the conduction state ("on" or "off") of  $D_1$ , and calculate the voltages  $V_3$  and  $V_4$ . Summarize your findings in **Table 1a**.

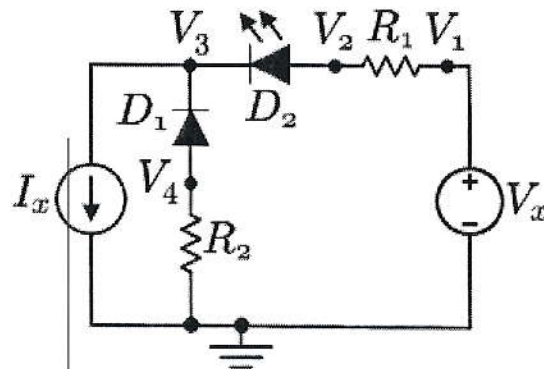



Fig. 1: Diode circuit of Q1.

Table 1a: Results of the diode circuit of Q1.

State of $D_1$	$V_3$ [V]	$V_4$ [V]
ON	-8.7	-8

Each item (5) marks

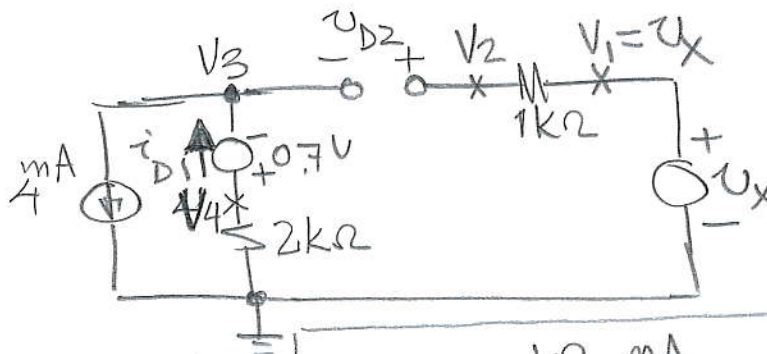$D_2$ : OFF  $\Rightarrow D_1$ : ON Since  $D_1$  is the only remaining path for the current  $I_x$  which is impressed.



$$i_{D1} = I_x = 4\text{ mA} \checkmark$$

$$V_4 = 0 - 2 \times 4 = -8\text{ V}$$

$$V_3 = V_4 - 0.7 = -8 - 0.7 = -8.7\text{ V}$$

**Blank Page**


- 1b) Starting from a very negative voltage, as in Part (a),  $V_x$  is gradually raised until  $D_2$  starts to glow. For this operating condition, calculate  $V_x$ ,  $V_1$ , and  $V_2$ . Complete **Table 1b**.

**Table 1b:** voltage values corresponding to state transition of  $D_2$  from "dim" to "glowing".

$V_x$ [V]	$V_1$ [V]	$V_2$ [V]
-6.5	-6.5	-6.5

5 marks each

The same circuit applies here:

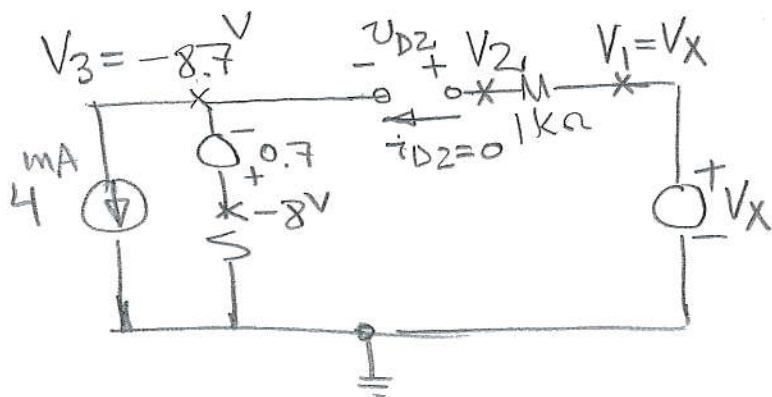

$$i_{D2}=0 \Rightarrow V_2 = V_1 = V_x$$

$$v_{D2} = V_2 - V_3 = V_x - (-8.7)$$

The LED turns on when  $v_{D2}$  reaches  $2.2^V$

$$\Rightarrow 2.2 = V_x + 8.7 \Rightarrow \boxed{V_x = -6.5^V}$$

$$\Rightarrow \boxed{V_1 = -6.5^V}$$

$$\Rightarrow \boxed{V_2 = -6.5^V}$$

Q2: In the circuit of Fig. 2,  $V_s = -9\text{ V}$ . If  $V_o = -8\text{ V}$  is at a temperature of  $20^\circ\text{C}$ , what will  $V_o$  be the  $40^\circ\text{C}$ ? At  $0^\circ\text{C}$ ? At  $80^\circ\text{C}$ ? Explain why and/or show the calculations. Summarize your results in Table 2. [Hint: the voltage drop across the resistor is proportional to the reverse current of the diode].


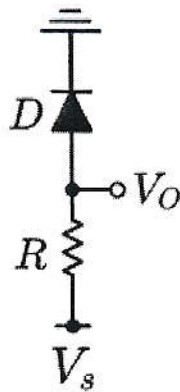


Fig. 2: Diode circuit of Q2.

Table 2: Results of the diode circuit of Q2.

$T [^\circ\text{C}]$	20	40	0	80
$V_o [\text{V}]$	-8	-5	-8.75	0

} (5) marks each

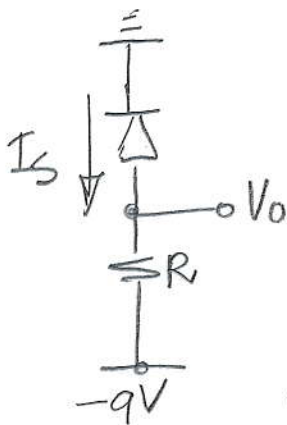

The diode is reverse-biased. Therefore, its current, the reverse current, flows down and results in a proportional voltage drop across the resistor:

$$V_o - (-9) \propto I_s \Rightarrow V_o + 9 \propto I_s$$

On the other hand,  $I_s$  doubles for every  $10^\circ\text{C}$  temperature rise.

$$\theta = 40^\circ\text{C} \Rightarrow \frac{V_o + 9}{-8 + 9} = 2^{\left(\frac{40 - 20}{10}\right)} = 4 \Rightarrow \boxed{V_o = -5\text{ V}}$$

$$\theta = 0^\circ\text{C} \Rightarrow \frac{V_o + 9}{-8 + 9} = 2^{\left(\frac{0 - 20}{10}\right)} = \frac{1}{4} \Rightarrow \boxed{V_o = -8.75\text{ V}}$$

$$\theta = 80^\circ\text{C} \Rightarrow \frac{V_o + 9}{-8 + 9} = 2^{\left(\frac{80 - 20}{10}\right)} = 64 \Rightarrow V_o = 55\text{ V} \times \text{impossible}$$

$V_o$  cannot exceed zero, as, otherwise, the diode starts to conduct and current would flow from the negative source to the ground, which is impossible  $\Rightarrow \boxed{V_o \approx 0}$

**Blank Page**



Q3: In the bridge rectifier of Fig. 3, the diodes are assumed to be ideal, and the source voltage  $v_I$  is a 60-Hz, 20-Vrms sinusoid. Determine the **reading of a DC voltmeter** of the output voltage  $v_O$ , under each of the following conditions:

- (3a) Only the load  $R_L$  is connected (the smoothing capacitor  $C$  has been removed);
- (3b) Only  $C$  is connected ( $R_L$  has been removed);
- (3c)  $R_L = 1.0 \text{ k}\Omega$  and  $C = 150 \mu\text{F}$ ; and
- (3d)  $R_L = 1.0 \text{ k}\Omega$  and  $C = \infty$ .

Support your answers by calculations and/or explanations. Complete Table 3.

Table 3: results of the circuit of Q3.

Answer to (3a)	Answer to (3b)	Answer to (3c)	Answer to (3d)
18	28.3	27.5	28.3

} 5 marks each

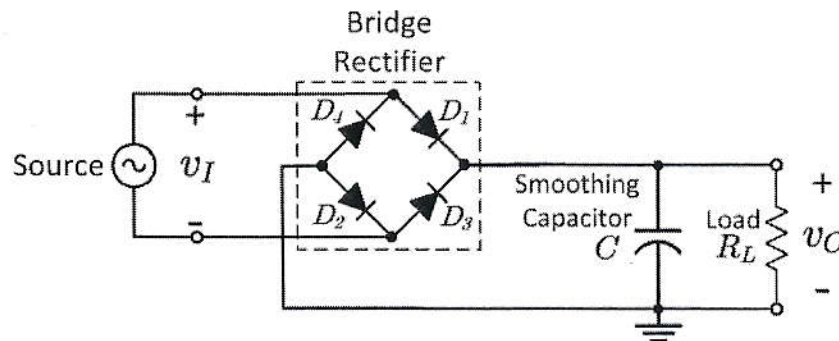


Fig. 3: Bridge rectifier of Q3.

3a)

Full-wave rectifier




$$V_m = 20 \times \sqrt{2} = 28.3 \text{ V}$$

$$\overline{V}_O = \frac{2V_m}{\pi} = \frac{2 \times 28.3}{\pi} = 18 \text{ V}$$

3b)


Peak Detector

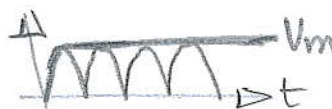


$$\overline{V}_O = V_m = 28.3 \text{ V}$$

3c)

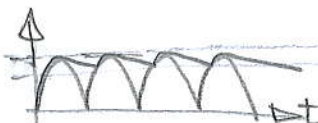Full-wave rectifier with output capacitor


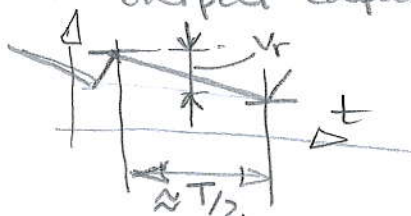
$$\overline{V}_O = V_m - \frac{1}{2} V_r$$




$$V_r \approx \frac{I \Delta t}{C} = \frac{(V_m/R) T/2}{C} = \frac{(28.3/1000) \times 8.3 \times 10^{-3}}{150 \times 10^{-6}} = 1.56 \text{ V}$$

Page 7 of 14

$$\overline{V}_O = V_m - \frac{1}{2} V_r = 28.3 - \frac{1}{2} \times 1.56 = 27.5 \text{ V}$$

See also the back

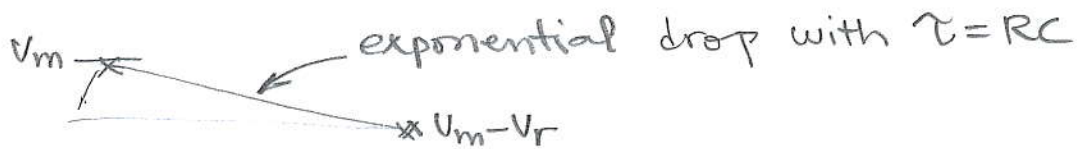Alternative solution to (3c)

$$v_o(t) = v_o(\infty) + [v_o(0) - v_o(\infty)]e^{-t/\tau}$$

$$v_o(t) = 0 + [V_m - 0]e^{-t/\tau}$$

$$\tau = RC = 1000 \times 150 \times 10^{-6} = 0.15 \text{ s}$$

$$t = T/2 = \frac{1}{2f} = \frac{1}{2 \times 60} = 8.3 \times 10^{-3} \text{ s}$$

$$v_o(t = T/2) = V_m - V_r$$

$$\Rightarrow V_m - V_r = V_m e^{-\frac{8.3 \times 10^{-3}}{0.15}} \Rightarrow V_r = \left[1 - e^{-\frac{8.3 \times 10^{-3}}{0.15}}\right] \times 28.3$$

$$\Rightarrow V_r = 1.5 \text{ V}$$

$$\boxed{\bar{V}_o = V_m - \frac{1}{2} V_r = 28.3 - \frac{1}{2} \times 1.5 = 27.5 \text{ V}}$$

3d)

Very large capacitor results in very small ripple,  $V_r$ . Therefore

$$\bar{V}_o \approx V_m \quad (\text{since } V_r \approx 0)$$

$$\Rightarrow \boxed{\bar{V}_o = 28.3 \text{ V}}$$



**Blank Page**

Q4: In the shunt voltage regulator of Fig. 4,  $R_L = 1.0 \text{ k}\Omega$  and  $R = 820 \Omega$ . According to the manufacturer, the Zener diode gives a voltage of  $v_Z = V_{ZT} = 5.1 \text{ V}$  at a test current of  $i_Z = I_{ZT} = 20 \text{ mA}$ . Further,  $r_Z = 10 \Omega$  and  $I_{ZK} = 1.5 \text{ mA}$ .


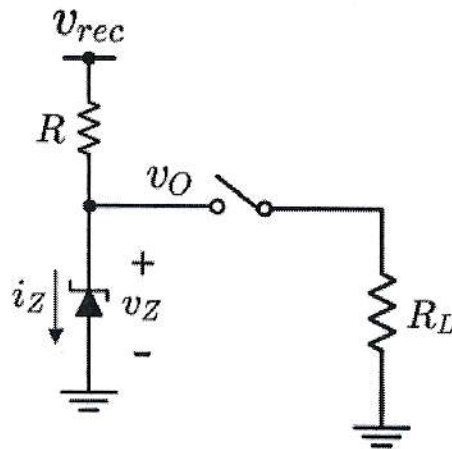


Fig. 4: Shunt regulator of Q4.

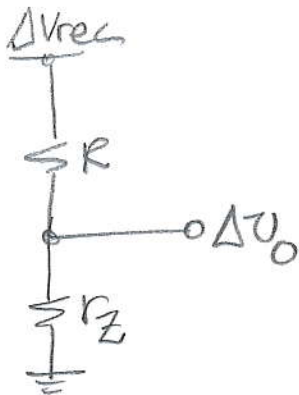(4a) Assuming that the switch is open, determine the peak-to-peak ripple of the output voltage  $v_O$  if the unregulated voltage  $v_{rec}$  has a peak-to-peak ripple of  $2.0 \text{ V}$ . Show all the work.




$$\Delta v_O = \frac{\Delta v_{rec}}{R + r_Z} \times r_Z$$

$$\Rightarrow \Delta v_O = \frac{2}{820 + 10} \times 10 = 0.024 \text{ V}$$

or 24 mV

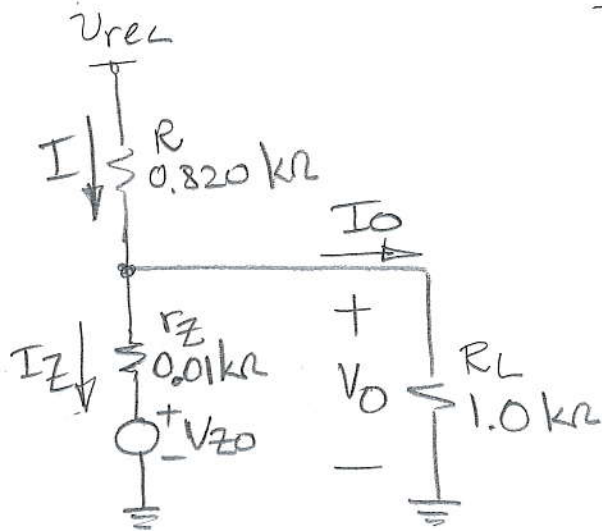(5) marks

- (4b) Assuming that the switch is closed, calculate the minimum permissible value of the unregulated voltage  $v_{rec}$ . Show all the work.



The minimum value of  $v_{rec}$  should be such that  $i_Z$  does not fall below  $I_{ZK}$ . The boundary condition, therefore, is when  $i_Z = I_{ZK}$  while the load is also connected.

First calculate  $V_{Z0}$  using test data:

$$V_Z = V_{Z0} + r_Z i_Z$$

$$\underbrace{5.1}_{\text{given}} = \underbrace{V_{Z0}}_{\text{given}} + \underbrace{0.01 \times 20}_{\text{given}} \Rightarrow \underline{V_{Z0} = 4.9V}$$

Then,

$$I_Z = I_{ZK} = 1.5 \text{ mA} \Rightarrow V_Z = 4.9 + 0.01 \times 1.5 = 4.915V$$

$$V_O = V_Z = 4.915V \Rightarrow I_O = \frac{V_O}{R_L} = \frac{4.915}{1.0} = 4.915 \text{ mA}$$


$$I = I_O + I_Z = 4.915 + 1.5 = 6.415 \text{ mA}$$

$$v_{rec} = V_Z + RI = 4.915 + 0.820 \times 6.415 \approx 10.2V$$

$$\boxed{v_{rec} = 10.2V} \quad (10) \text{ marks}$$

Q5: In the transistor circuit of **Fig. 5**, determine the mode of operation of the transistor and the node voltages, if  $V_{CC} = 10\text{ V}$ ,  $R_1 = R_2 = 1.0\text{ k}\Omega$ ,  $R_C = 100\text{ }\Omega$ , and  $R_E = 220\text{ }\Omega$ . Assume that  $V_{BEon} = 0.7\text{ V}$ ,  $V_{CEsat} = 0.3\text{ V}$ , and  $\beta = 100$ .

Show all the work, and complete **Table 5**.

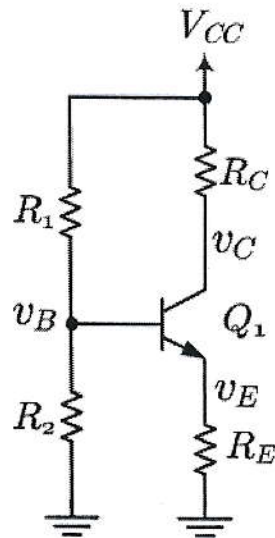


**Fig. 5:** Transistor circuit of Q5.

**Table 5:** transistor's mode of operation and the node voltages in the circuit of Q5.


Mode of Q1	$v_B[V]$	$v_C[V]$	$v_E[V]$
active	4.9	8.1	4.2

5 marks each

Blank Page

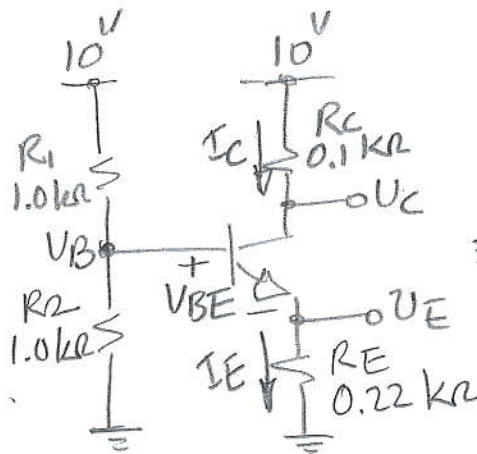

≡

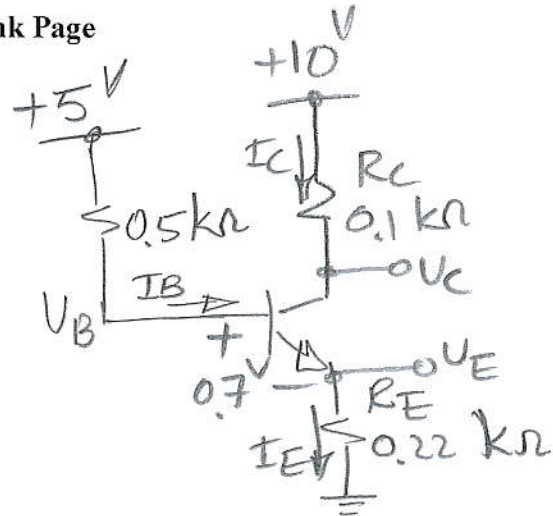

$$\text{KVL: } 5 - 0.5I_B - 0.7 - 0.22I_E = 0$$

$$\text{Assuming active mode: } I_B = \frac{1}{\beta} I_C, I_E = \frac{\beta + 1}{\beta} I_C$$

$$\Rightarrow 5 - \frac{0.5}{100} I_C - 0.7 - 0.22 \times \frac{101}{100} I_C = 0$$

$$\Rightarrow I_C = \frac{4.3 \times 100}{0.5 + 0.22 \times 101} = 18.9 \text{ mA}$$

$$\Rightarrow V_C = 10 - 0.1 \times 18.9 = 8.11 \text{ V}$$

$$I_E = \frac{\beta + 1}{\beta} I_C = \frac{101}{100} \times 18.9 = 19.1 \text{ mA}$$

$$\Rightarrow V_E = 0 + 0.22 \times 19.1 = 4.2 \text{ V}$$

$$\Rightarrow V_B = V_E + 0.7 = 4.2 + 0.7 = 4.9 \text{ V}$$

check to see whether the "active mode" assumption was right:

$$V_{CE} = V_C - V_E = 8.11 - 4.2 > 0.3 \text{ V} \checkmark$$



**Blank Page**