

Ryerson University
Department of Electrical and Computer Engineering
ELE202: Electric Circuits Analysis
Final Examination, July 2010
Duration: 3 hours

Student's Name:

Student's Number: **Section:**

NOTES:


1. This is a **Closed Book** examination. No aids other than the approved calculators are allowed.
2. All questions are of equal value.
3. **No questions are to be asked**. If doubt exists as to the interpretation of any question, the student is urged to submit with the answer paper, a clear statement of any assumptions made.

<i>Question No.</i>	<i>Mark of each question</i>	<i>Mark obtained</i>
Q1	20	
Q2	20	
Q3	20	
Q4	20	
Q5	20	
Total (100)		

Q1: In the circuit shown below, the current through the inductor, $i(t)$, is governed by the following equation:

$$i(t) = 3 + 2e^{-3t} \text{ A for } t \geq 0$$


Determine $v(t)$ for $t \geq 0$.

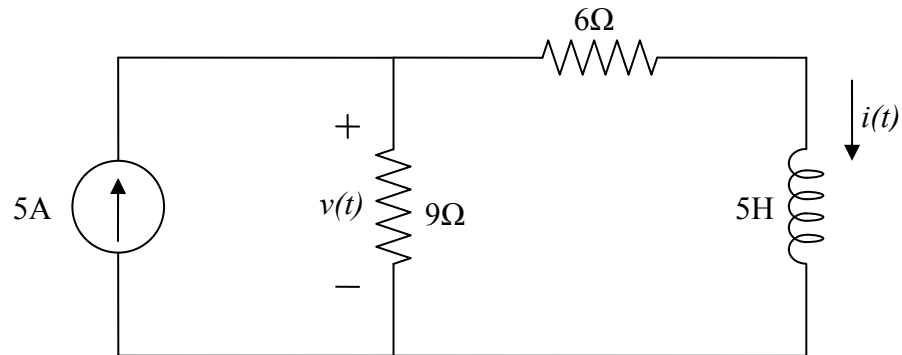

$v(t) =$

Black Page

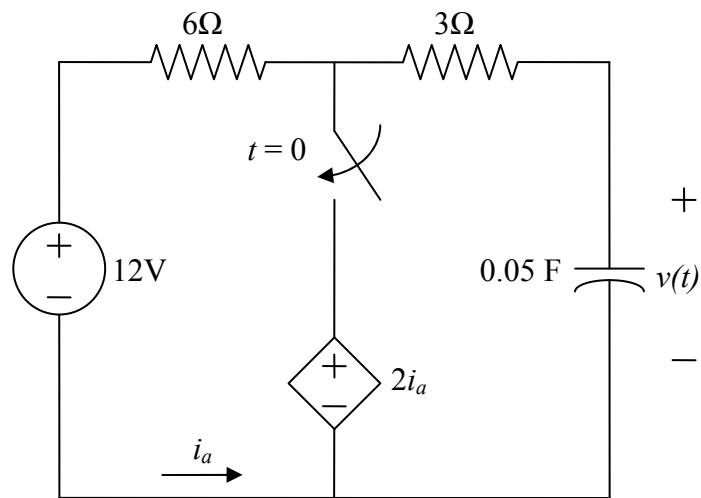Q2: The following circuit is at steady state before the switch closes at time $t=0$. Determine the capacitor voltage, $v(t)$, for $t \geq 0$.




$v(t) =$

Blank Page

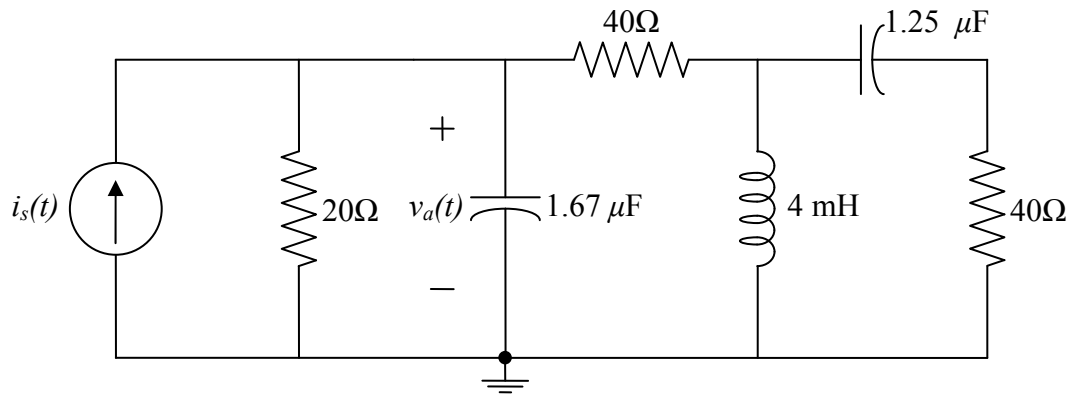Q3: Determine the voltage $v_a(t)$ for the following circuit when


$$i_s(t) = 20 \cos(\omega t + 53.13^\circ) \text{ A} \quad \text{and} \quad \omega = 10^4 \text{ rad/s.}$$



$v_a(t) =$

Blank Page

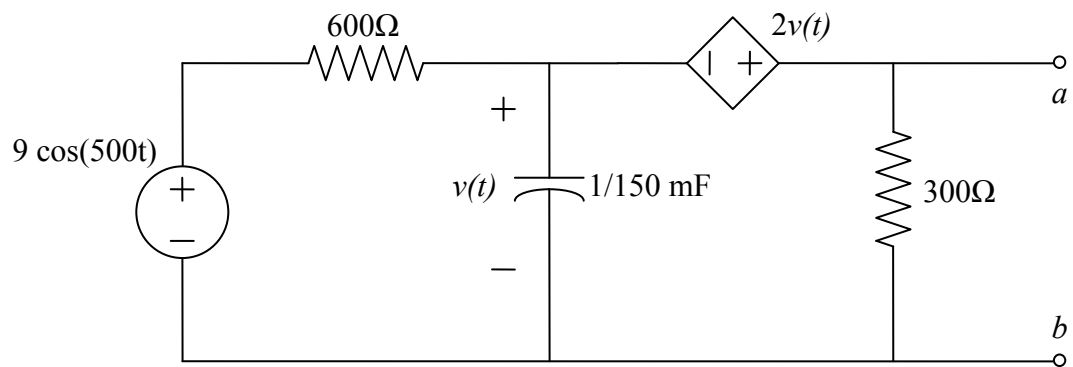Q4: Find the Thevenin equivalent circuit between point a and b for the following circuit:




$\mathbf{V_{th} =}$

$\mathbf{Z_{th} =}$

Blank Page

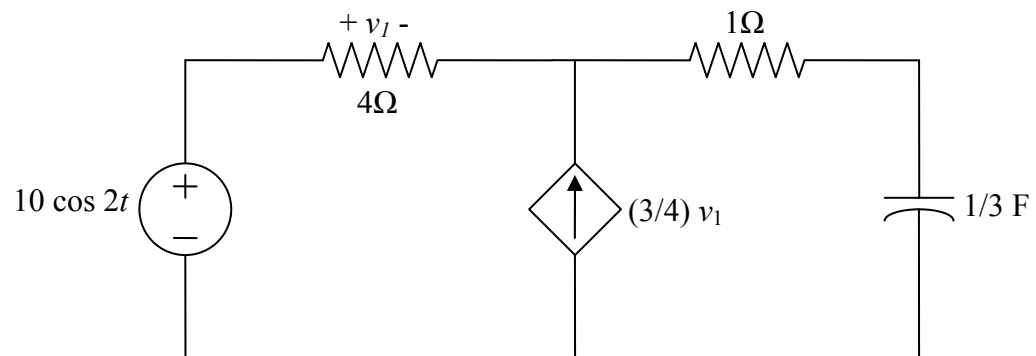Q5: Find the complex power delivered by the voltage source and the power factor seen by the voltage source for the following source:



S =

pf =

Blank Page