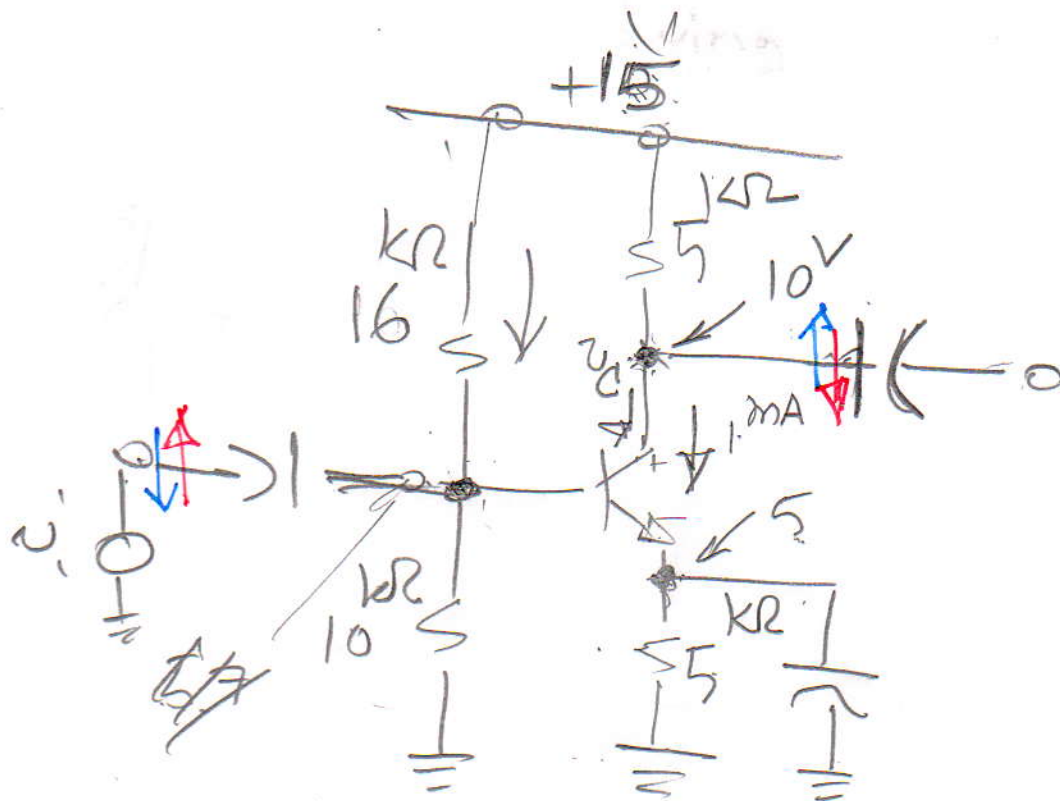


Voltage Swing Calculations


1

Example



$$\begin{aligned} V_A &= \infty \\ \beta &= 100 \\ V_{BE, on} &= 0.7V \\ V_{CE, sat} &= 0.3V \end{aligned}$$

$$V_E + V_{CE_{sat}} = 5.3V$$


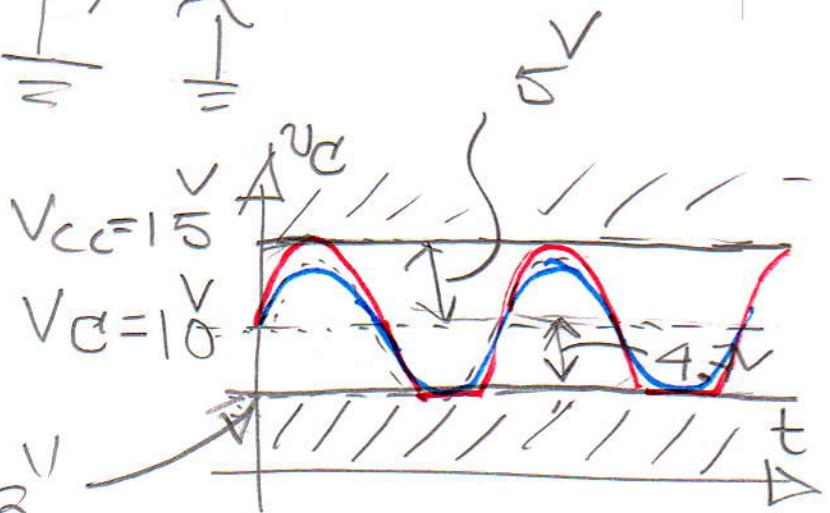


The maximum output voltage swing, then, is $2 \times 4.7 = 9.4V_{p-p}$.


The corresponding input voltage swing is $\frac{9.4V_{p-p}}{|A_{vol}|} = \frac{9.4V_{p-p}}{40 \times 50} = 0.0475V_{p-p}$ or $47.5mV_{p-p}$.

LOADED CASE.


2

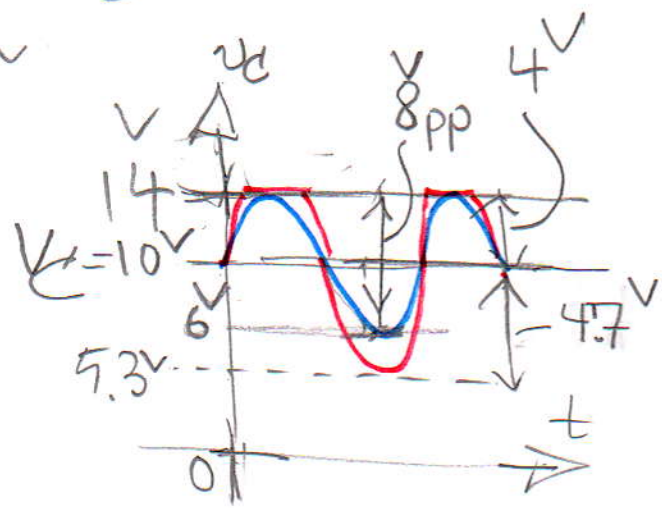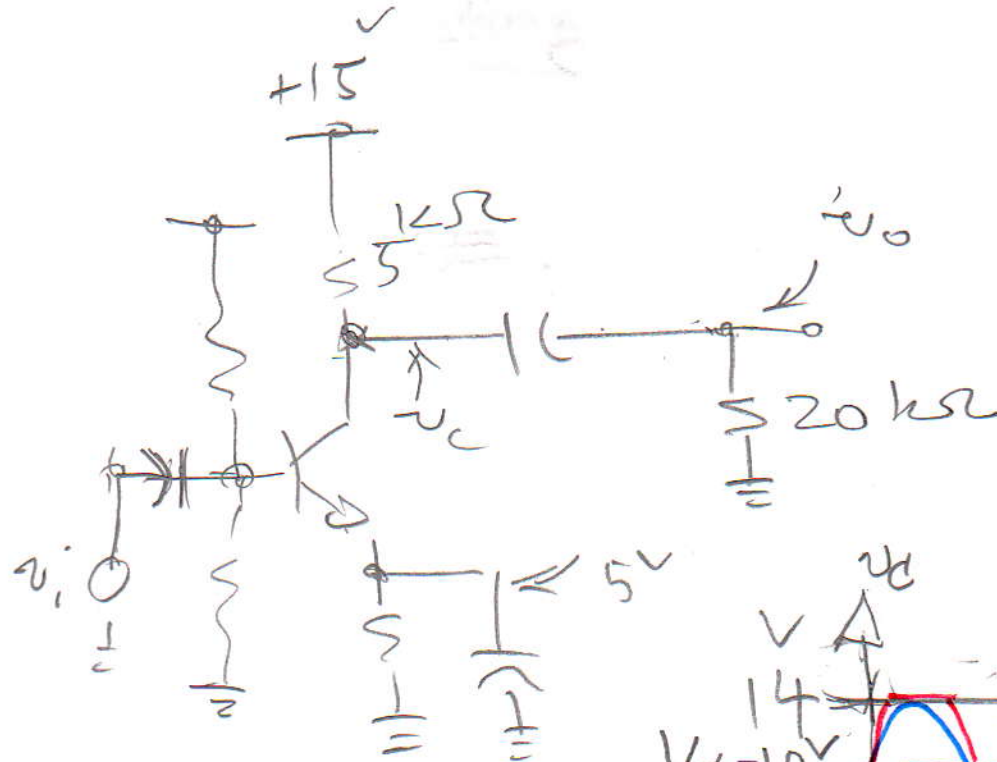

When "Saturated":

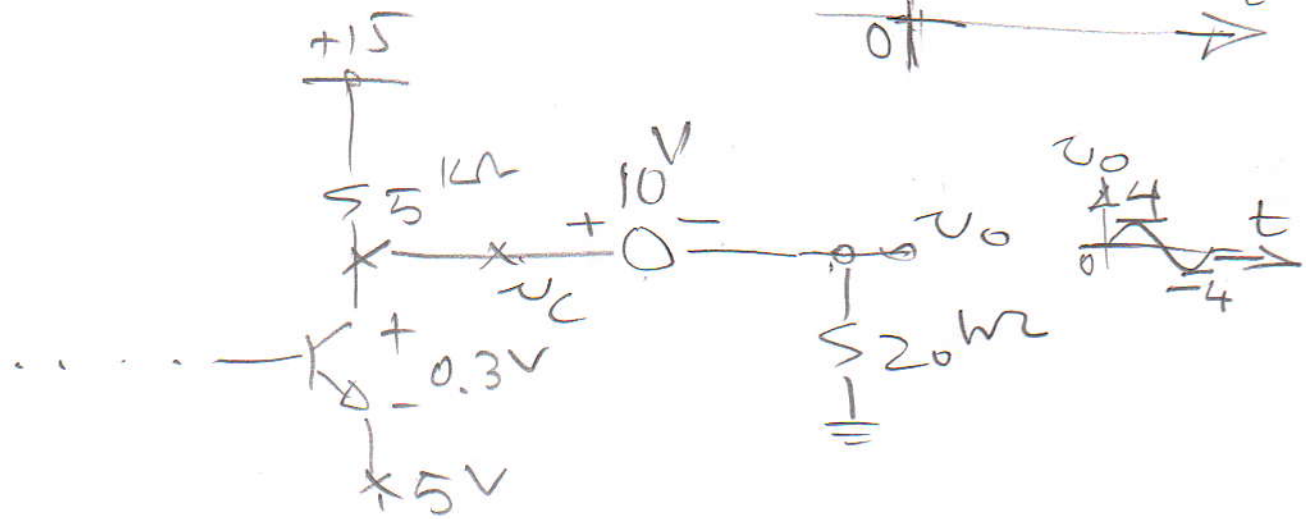

When "off"

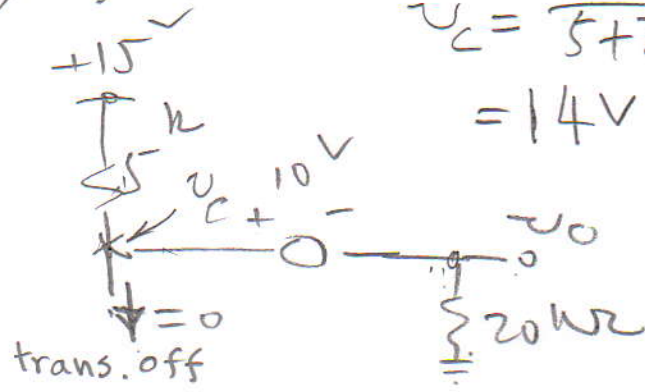


$$v_c = \frac{15-10}{5+20} \times 20 + 10 = 14V$$

Insertion of Emitter Deg.

3

let us need A_{v0} of -10 :

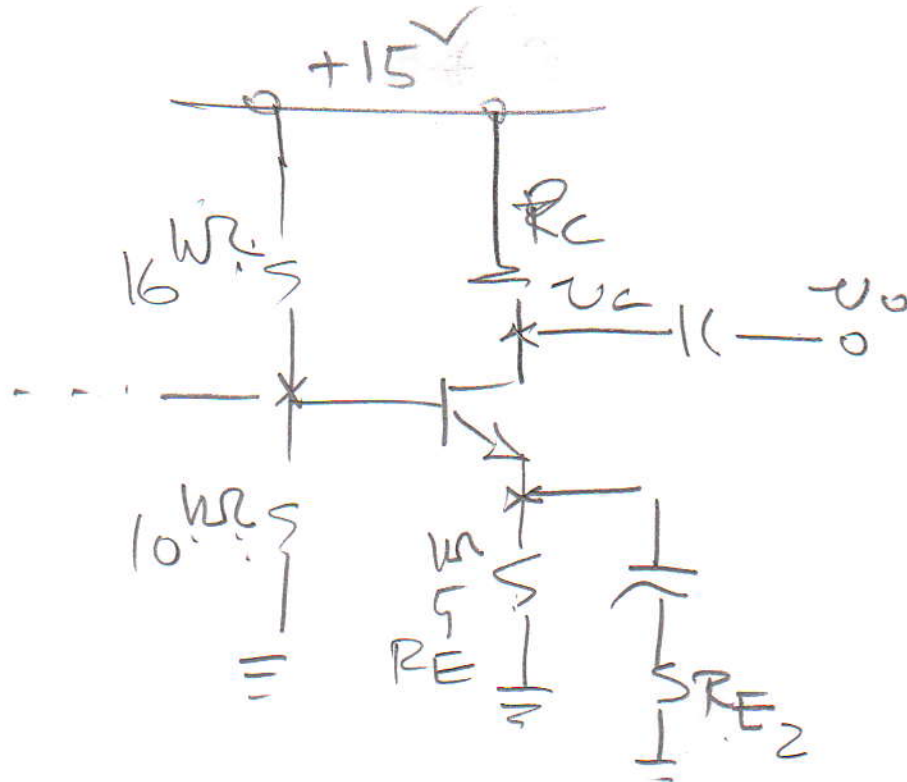

$$A_{v0} = \frac{-g_m R_C}{1 + g_m (R_E \parallel R_{E2})}$$

$\underbrace{R_E \parallel R_{E2}}_{\approx R_{E2}}$





$$-10 = \frac{-200}{1 + 40(R_E \parallel R_{E2})} \Rightarrow R_E \parallel R_{E2} \approx 0.475 \text{ k}\Omega$$

$$R_{E2} \approx 0.52 \text{ k}\Omega$$

Recalculate the Swing



4

No-load Case

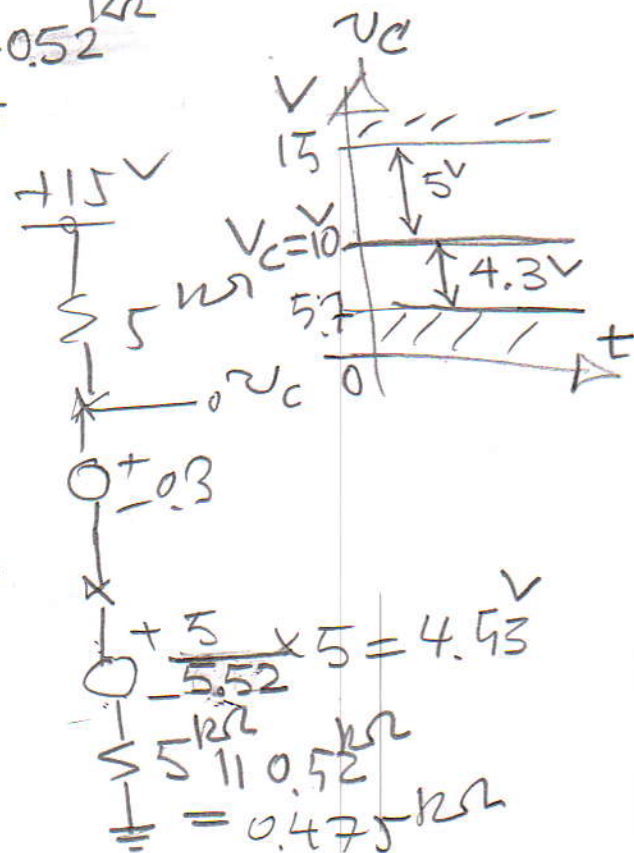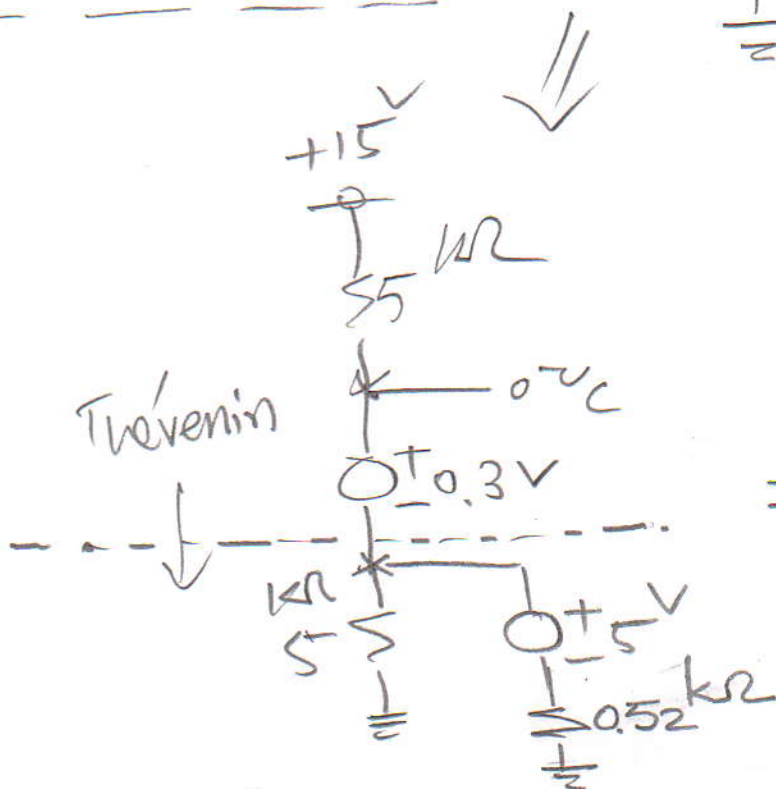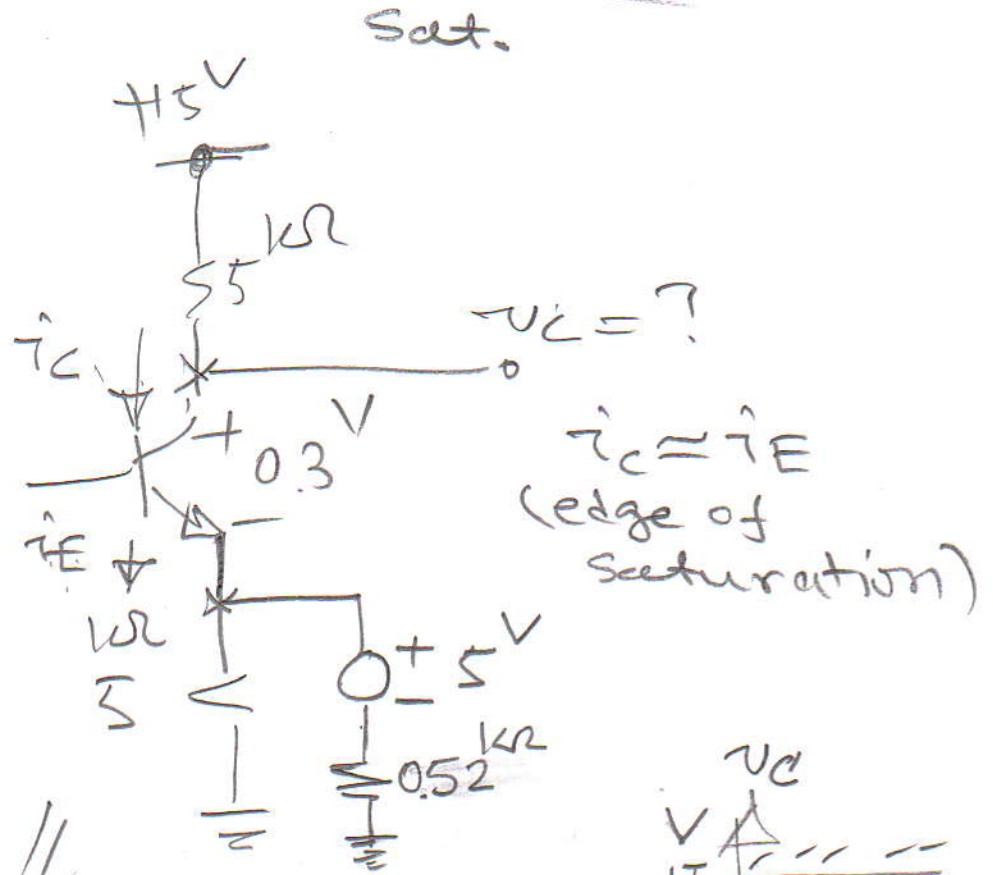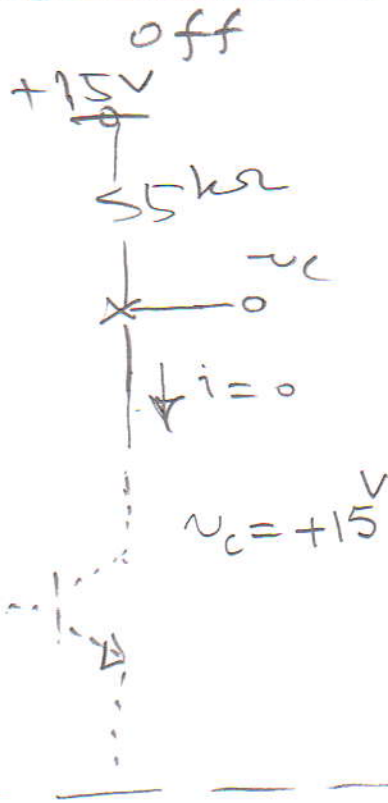

$$v_c = \frac{15 - (4.53 + 0.3)}{5 + 0.475} \times 0.475 + 4.53 + 0.3 = 5.7V$$


LOADED case

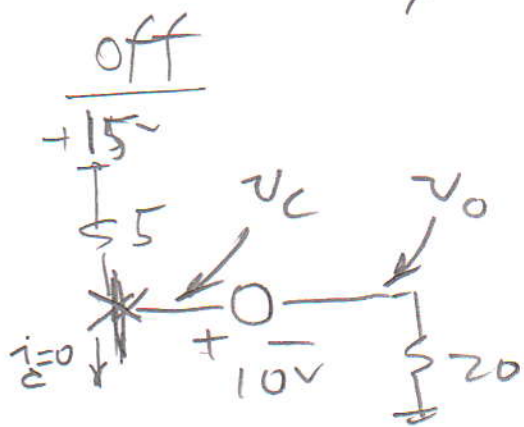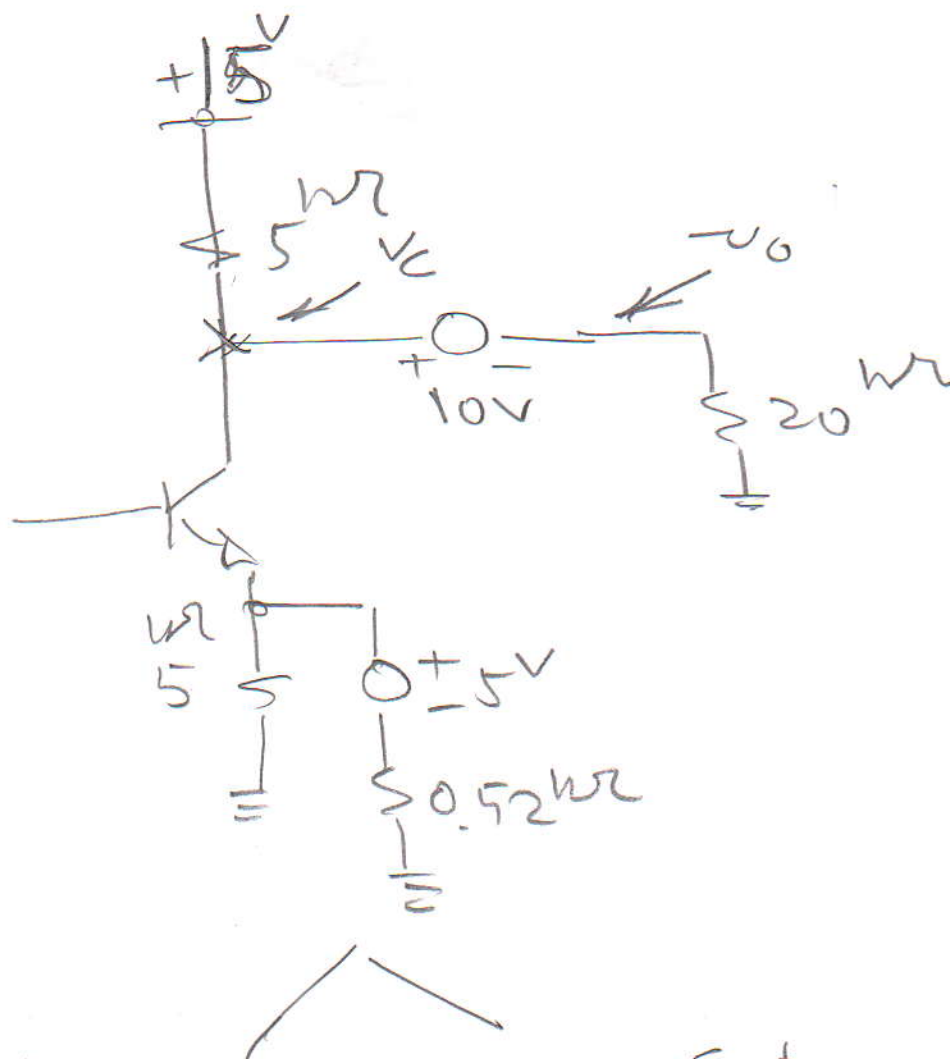

$$v_c = \frac{15 - 10}{25} \times 20 + 10$$


v_o

$$= 14V$$

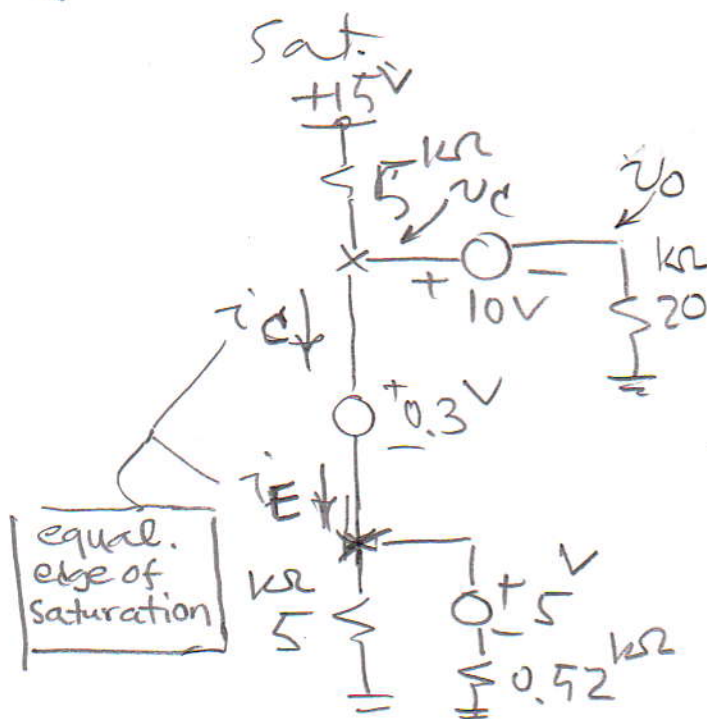


LOADED CASE (cont.)

6/

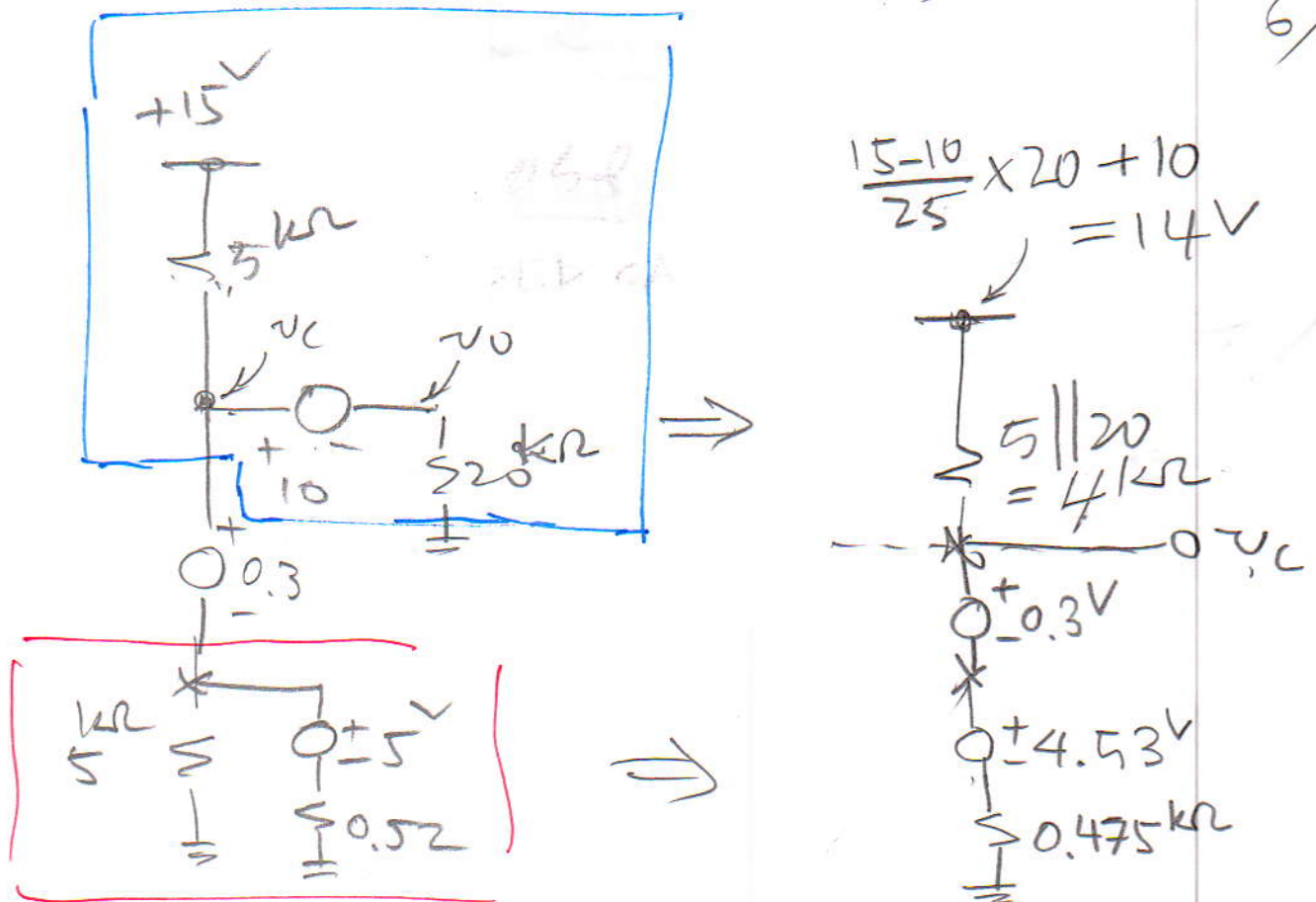

$$v_c = \frac{14 - (4.53 + 0.3)}{4 + 0.475} \times 0.475 + 4.53 + 0.3$$

$$\approx 5.8$$

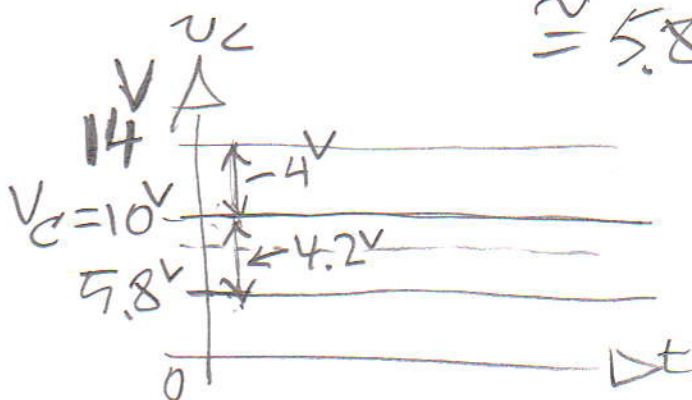

Max. output swing:
 $2 \times 4 = 8 \text{ V}_{pp}$

$$A_v = \frac{-40 \times (5 \parallel 20)}{1 + 40 \times (5 \parallel 0.52)} \approx -8 \text{ V/V}$$

$$\text{Max. input swing} = \frac{8 \text{ V}_{pp}}{|-8|} = 1 \text{ V}_{pp}$$