

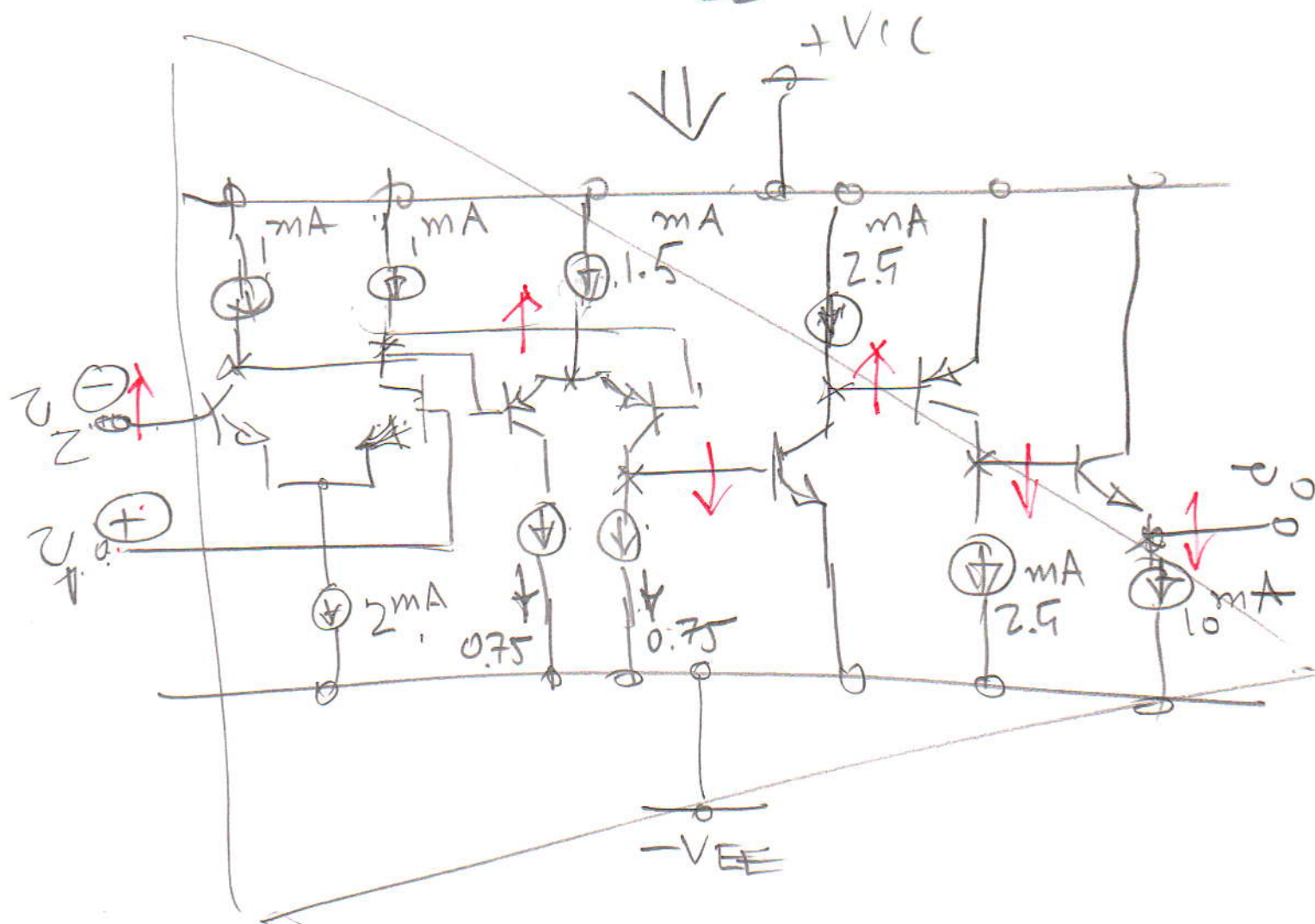
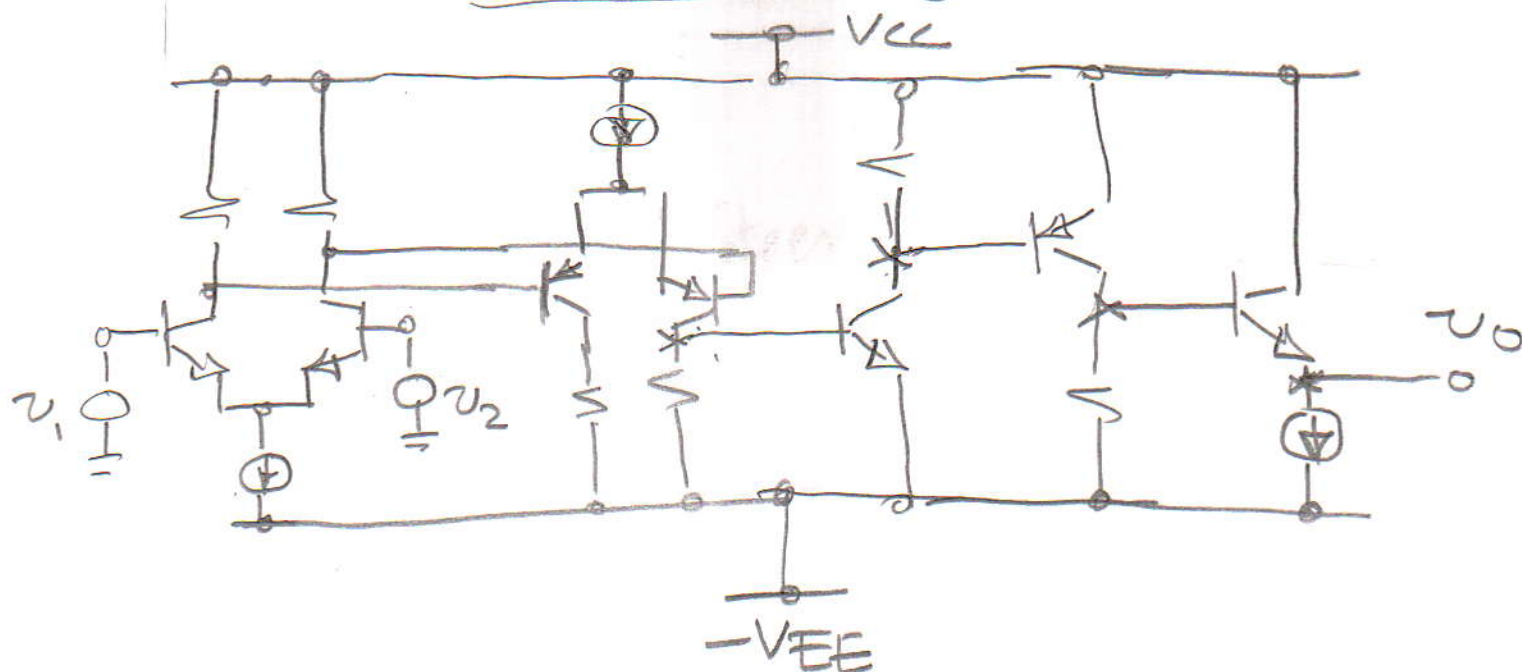




Current-Steering Circuits

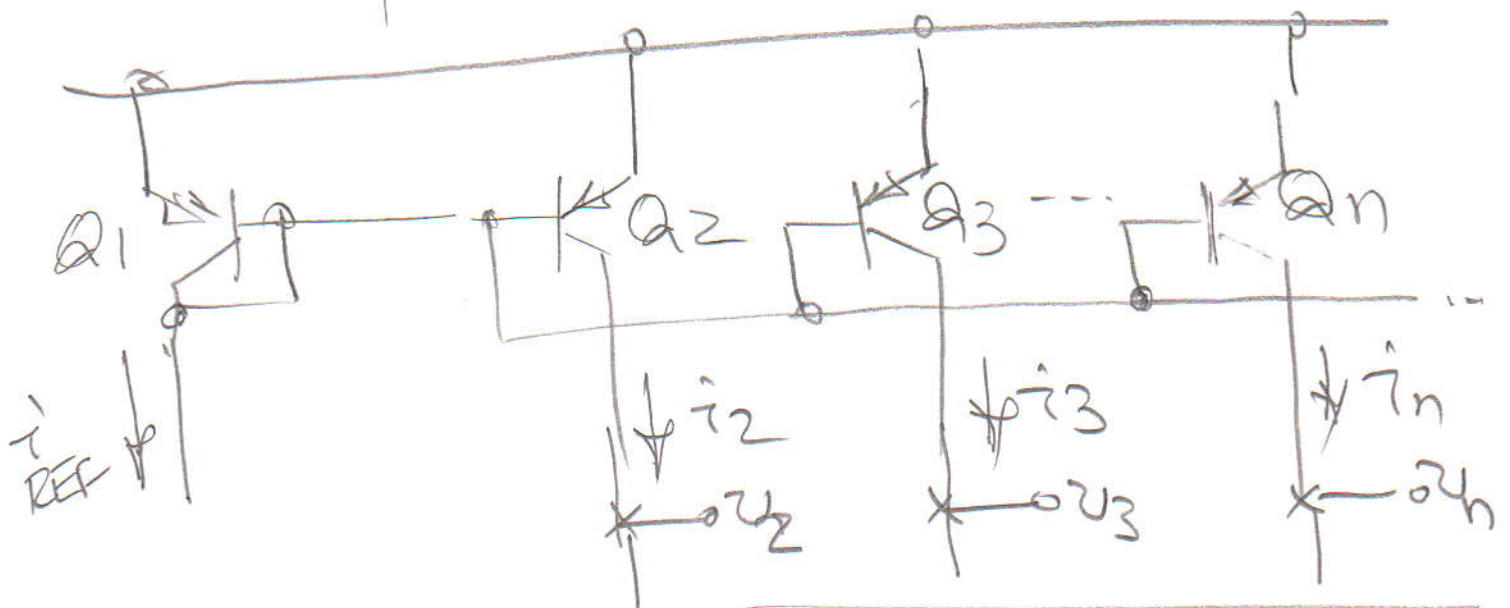

3/

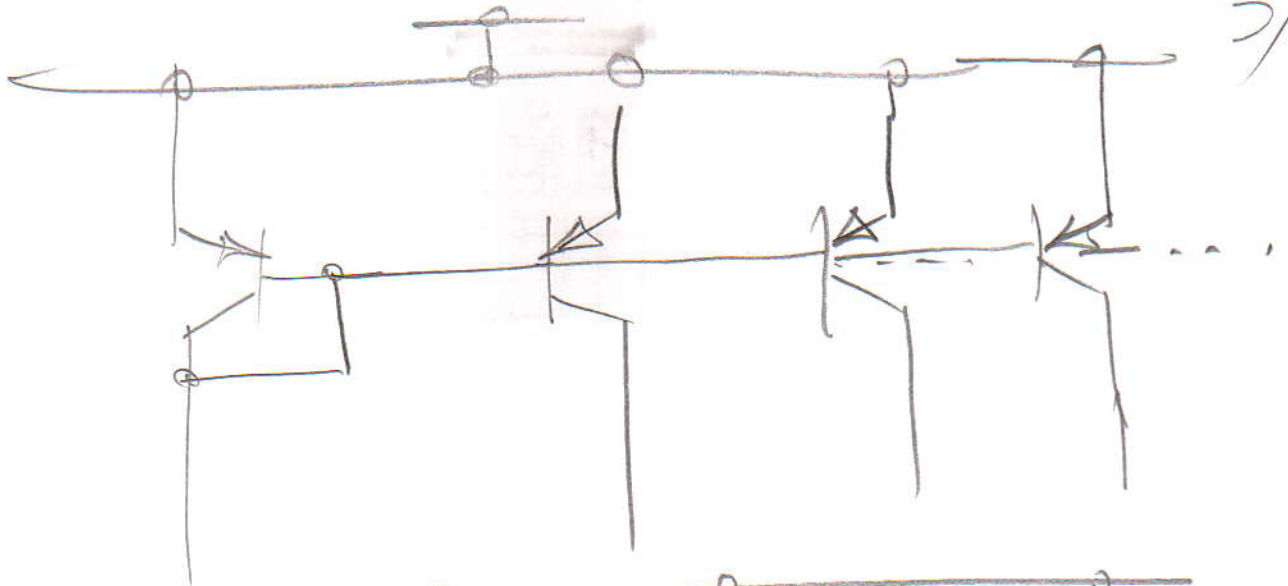

Special Case

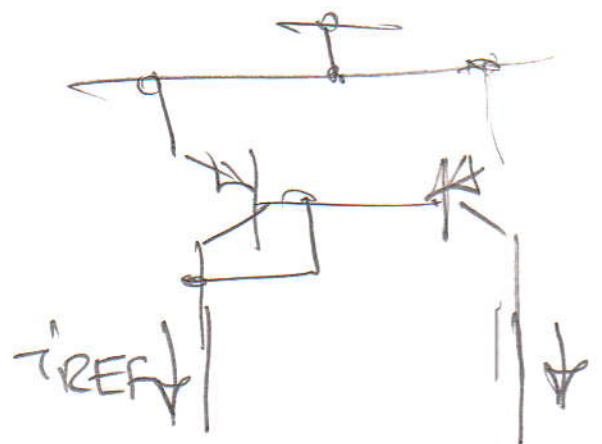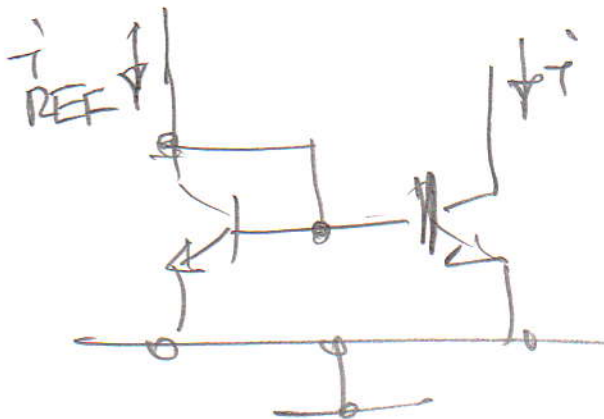


Called
"Current mirror"

$I_{S1} = I_{S2}$
matched pair


$$\Rightarrow i = i_{REF}$$

Documentation of an Experiment

4

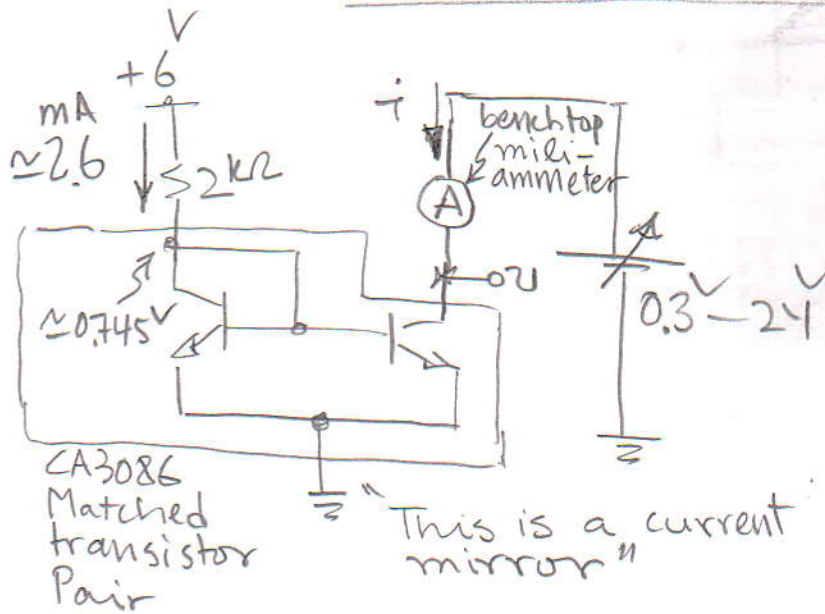


v	i
0.3V	2.46 mA
0.75V	2.56 mA
4.0V	2.72 mA
8.0V	2.90 mA
15.0V	3.27 mA
24.0V	4.15 mA
	$\Delta i / \Delta v \approx 71 \mu A/V$

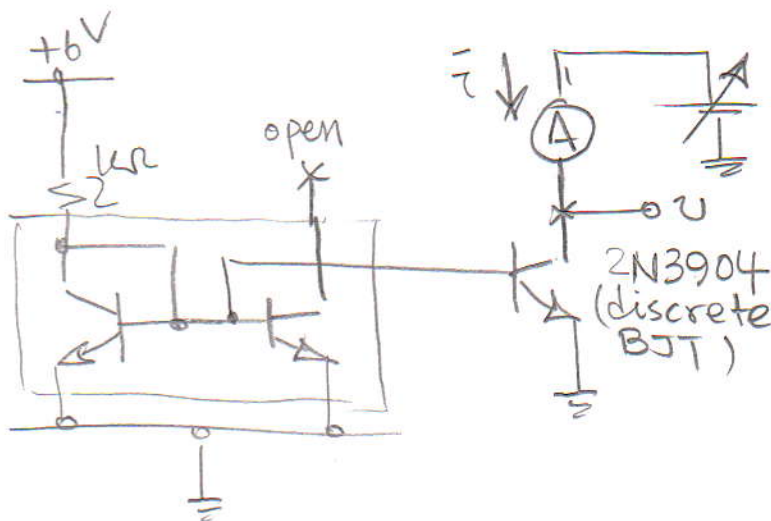

v	i
0.3V	14.7 mA
0.75V	19.6 mA
4.0V	starts at about 30 mA

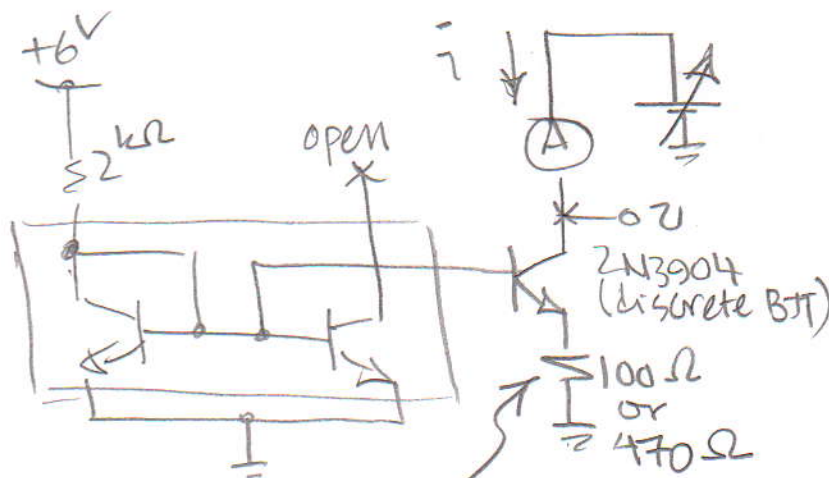At $v=4.0V$, i starts at 30 mA but quickly rises on its own since the transistor heats up, thus, further increasing the current. A thermal runaway is taking place that can eventually burn the BJT




emitter degeneration
 1- brings the current down
 2- makes the current less sensitive to v (i.e., increases R_0).

v	i ($R=100\Omega$)	i ($R=470\Omega$)
0.3V	0.931 mA	0.273 mA
0.75V	0.934 mA	0.275 mA
4.0V	0.943 mA	0.277 mA
8.0V	0.961 mA	0.279 mA
15.0V	0.994 mA	0.285 mA
24.0V	1.039 mA	0.289 mA
	$\Delta i / \Delta v \approx 4.6 \mu A/V$	$\Delta i / \Delta v \approx 0.67 \mu A/V$

Combine

5/

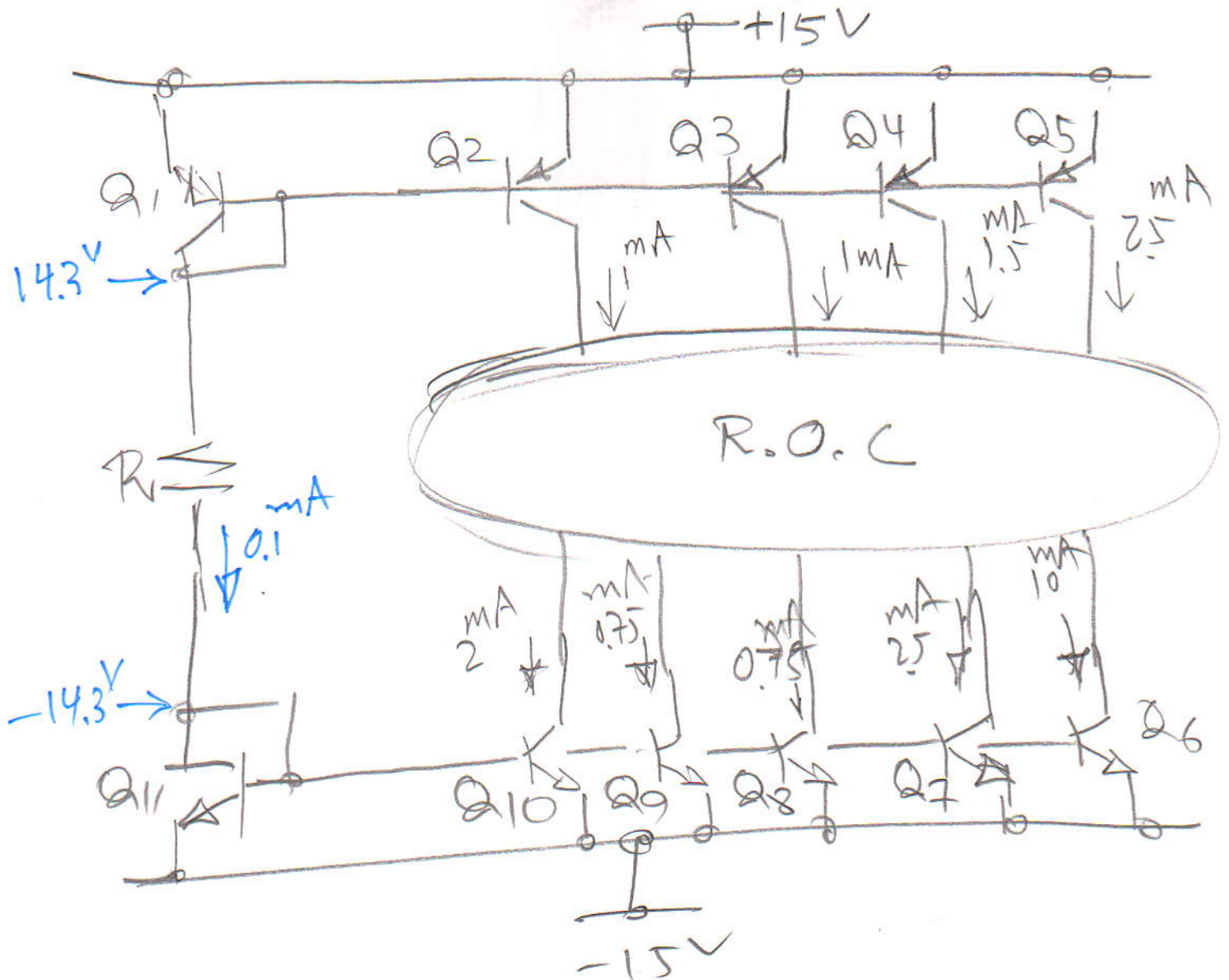

- ① Find R to make $I_{REF} = 0.1$ mA
- ② Determine the junction area ratios...

Solution


$$R = \frac{14.3 - (-14.3)}{0.1} = 286 \text{ k}\Omega$$

$$\frac{I_{S2}}{I_{S1}} = \frac{E_{BJA2}}{E_{BJA1}} = \frac{1}{0.1} = 10; \quad \frac{I_{S3}}{I_{S1}} = 10; \quad \frac{I_{S4}}{I_{S1}} = 15; \quad \frac{I_{S5}}{I_{S1}} = 25$$

$$\frac{I_{S10}}{I_{S11}} = \frac{E_{BJA10}}{E_{BJA11}} = \frac{2}{0.1} = 20; \quad \frac{I_{S9}}{I_{S11}} = 7.5; \quad \dots$$

MOS Versions

6

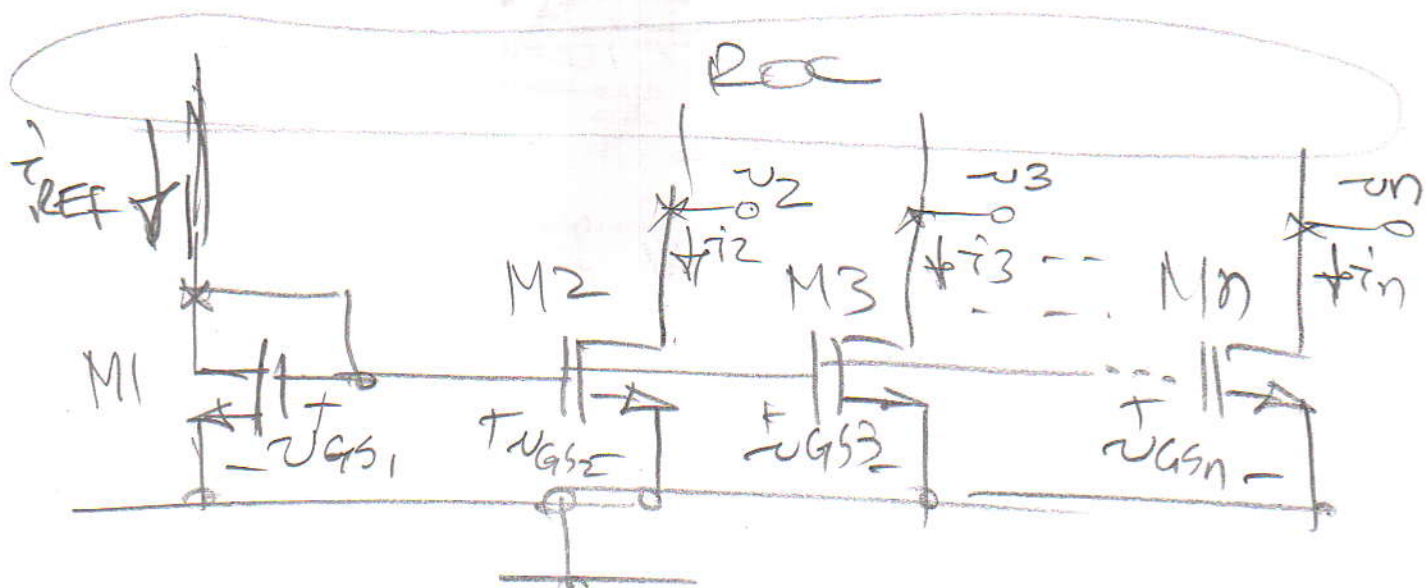

M2 ... Mn in the Saturation mode — V_{SS}

$$i_{REF} = \frac{1}{2} K_1 (v_{GS1} - V_t)^2 = \frac{1}{2} K' \left(\frac{W}{L} \right)_1 (v_{GS1} - V_t)^2$$

$$i_2 = \frac{1}{2} K_2 (v_{GS2} - V_t)^2 = \frac{1}{2} K' \left(\frac{W}{L} \right)_2 (v_{GS2} - V_t)^2$$

$$i_n = \frac{1}{2} K_n (v_{GSn} - V_t)^2 = \frac{1}{2} K' \left(\frac{W}{L} \right)_n (v_{GSn} - V_t)^2$$

$$v_{GS1} = v_{GS2} = \dots = v_{GSn}$$

Technology the same: $K'_1 = K'_2 = \dots = K'_n \triangleq K$



$$V_{t1} = V_{t2} = \dots = V_{tn} \triangleq V_t$$

$$\frac{i_2}{i_{REF}} = \frac{\left(\frac{W}{L} \right)_2}{\left(\frac{W}{L} \right)_1}$$


$$\frac{i_3}{i_{REF}} = \frac{\left(\frac{W}{L} \right)_3}{\left(\frac{W}{L} \right)_1}$$

⋮

Current Mirror

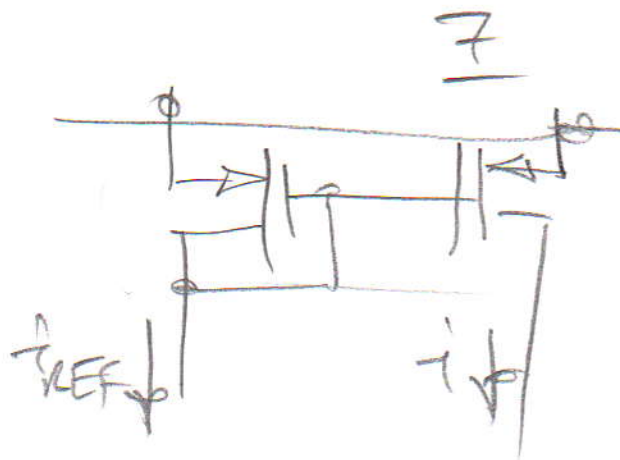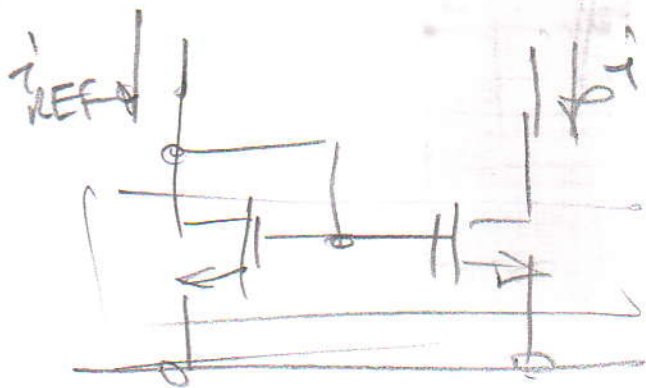
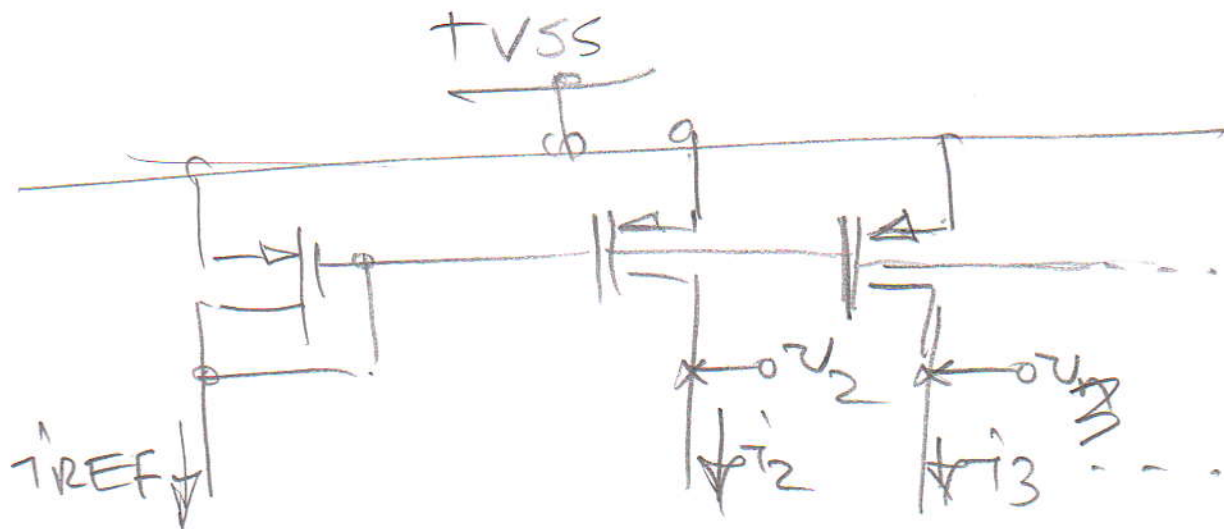
$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 \Rightarrow \boxed{i_i = i_{REF}}$$




$$k_n' = 2k_p' = 2.0 \text{ mA/V}^2$$

$$\left(\frac{W}{L}\right)_1 = 4\left(\frac{W}{L}\right)_2 = 2\left(\frac{W}{L}\right)_3 = 2\left(\frac{W}{L}\right)_4 = 2.5\left(\frac{W}{L}\right)_5$$

$$V_{tn} = 0.8 \text{ V}$$

$$V_{tp} = -1.0 \text{ V}$$

$$= 50$$

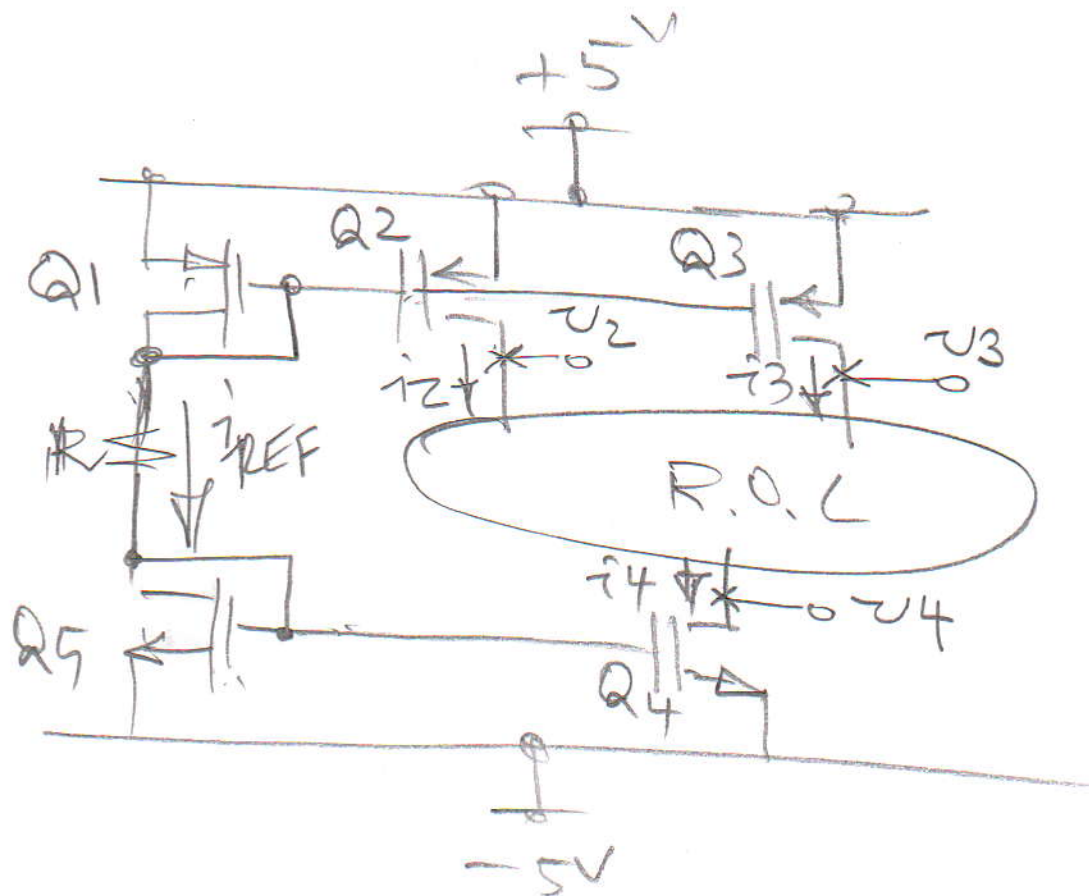

- ① Find R for $i_{REF} = 1 \text{ mA}$
- ② Calculate everything else!

$$i_{REF} = 1.0 \text{ mA}$$

$$i_1 = \frac{1}{2} k_1 V_{OV_1}^2$$

$$\Rightarrow i_1 = \frac{1}{2} \times k_p \left(\frac{W}{L} \right)_1 V_{OV_1}^2$$

$$\Rightarrow 1.0 = \frac{1}{2} \times 1.0 \times 50 \times V_{OV_1}^2$$

$$\Rightarrow V_{OV_1} = 0.2 \text{ V}$$

$$\begin{aligned} V_{SG_1} &= V_{OV_1} + |V_{tp}| \\ &= 0.2 + 1.0 \\ &= \underline{1.2 \text{ V}} \end{aligned}$$

$$i_5 = \frac{1}{2} k_5 V_{OV_5}^2$$

$$1.0 = \frac{1}{2} \times 2 \times \left(\frac{50}{2.5} \right) V_{OV_5}^2$$

$$\Rightarrow V_{OV_5} = 0.224 \text{ V}$$

$$V_{GS_5} = V_{OV_5} + V_{tn}$$

$$= 0.224 + 0.8 = 1.024 \text{ V}$$

$$R = \frac{3.8 - (-4.0)}{1.0} = \underline{7.8 \text{ k}\Omega}$$

$$i_2 = 0.25 \text{ mA}; i_3 = 0.5 \text{ mA}; i_4 = 0.125 \text{ mA}$$

