
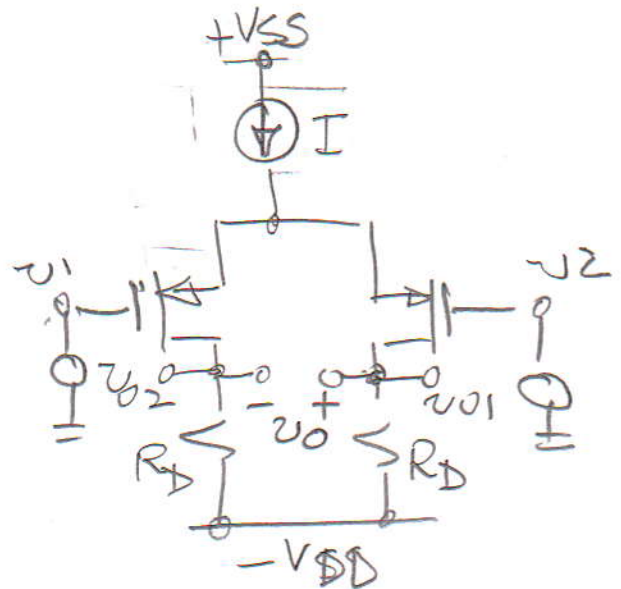
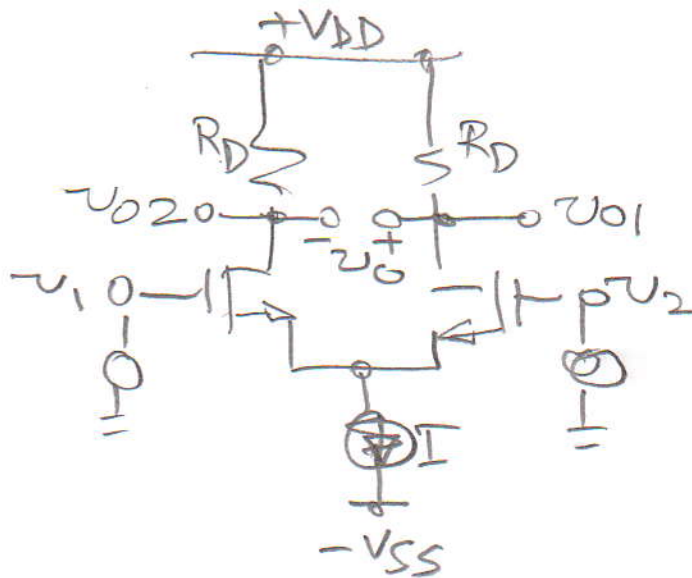
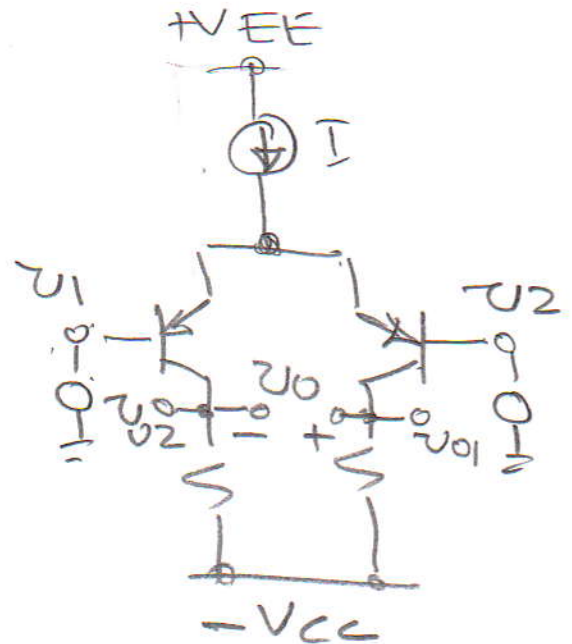


Differential Amplifiers

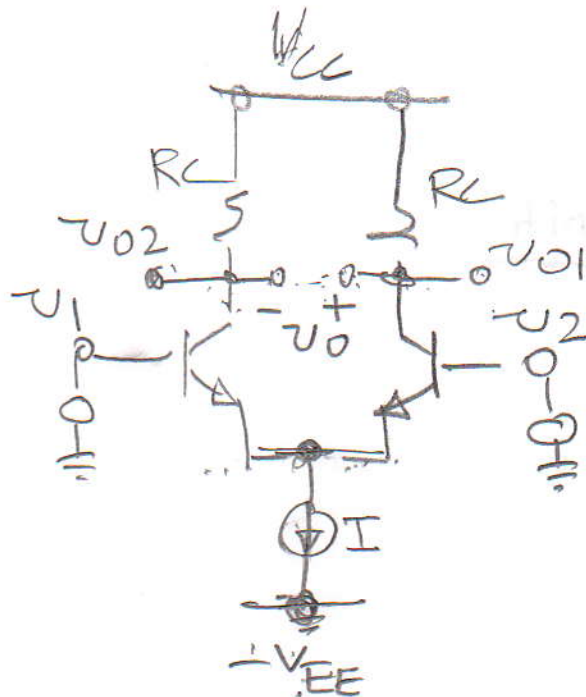

Objective


- to only amplify the difference between the two inputs

assumptions

- transistors identical
- current source ideal
- transistors are in active mode (saturation for MOS).

DC Analysis

2

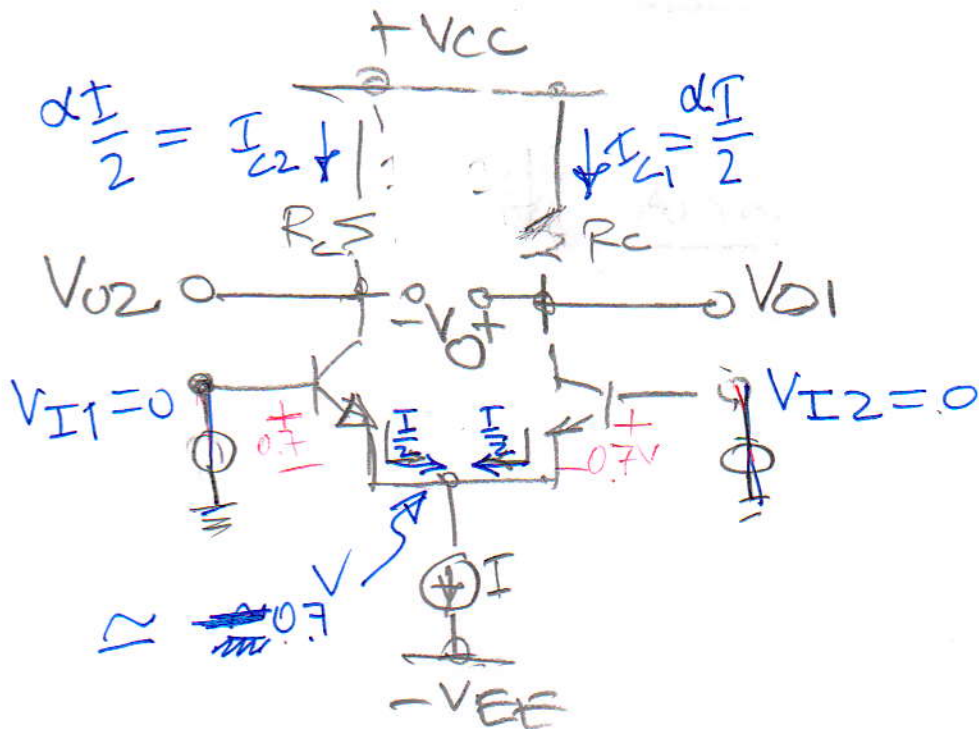

$$V_{O1} = V_{C1} = V_{CC} - R_C \frac{\alpha I}{2}$$


$$V_{O2} = V_{C2} = V_{CC} - R_C \frac{\alpha I}{2}$$

$$V_O = V_{O1} - V_{O2} = 0$$

$$g_m \triangleq g_{m1} = g_{m2} \approx 40 \frac{\alpha I}{2} \approx \underline{20 I}$$

DC Analysis (cont'd)

3

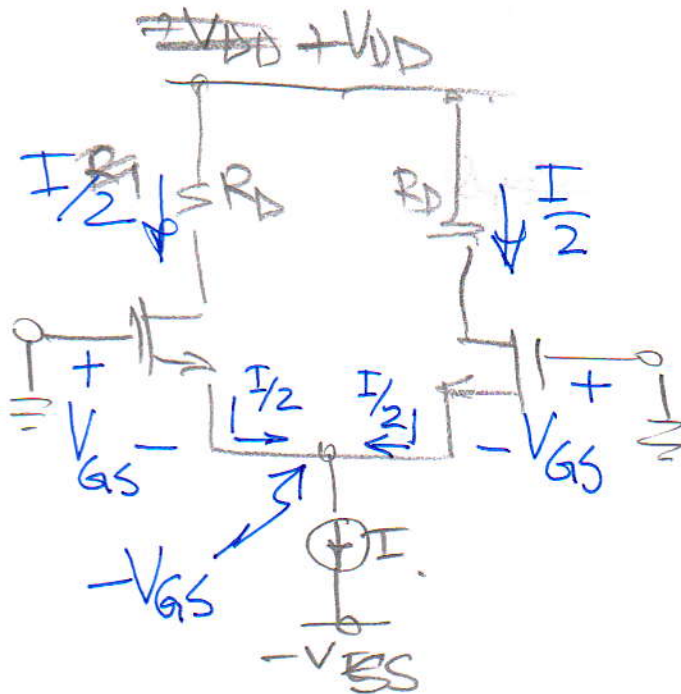

$$I_D = \frac{1}{2} K V_{OV}^2 \Rightarrow \frac{I}{2} = \frac{1}{2} K V_{OV}^2$$


$$\Rightarrow V_{OV} = \sqrt{I/K}$$

$$\Rightarrow V_{GS} = V_{OV} + V_t = \sqrt{\frac{I}{K}} + V_t$$

$$g_m \triangleq g_{m1} = g_{m2} = \sqrt{2K I_D} =$$
$$= \sqrt{2K I/2} = \sqrt{KI}$$

Big Picture

4

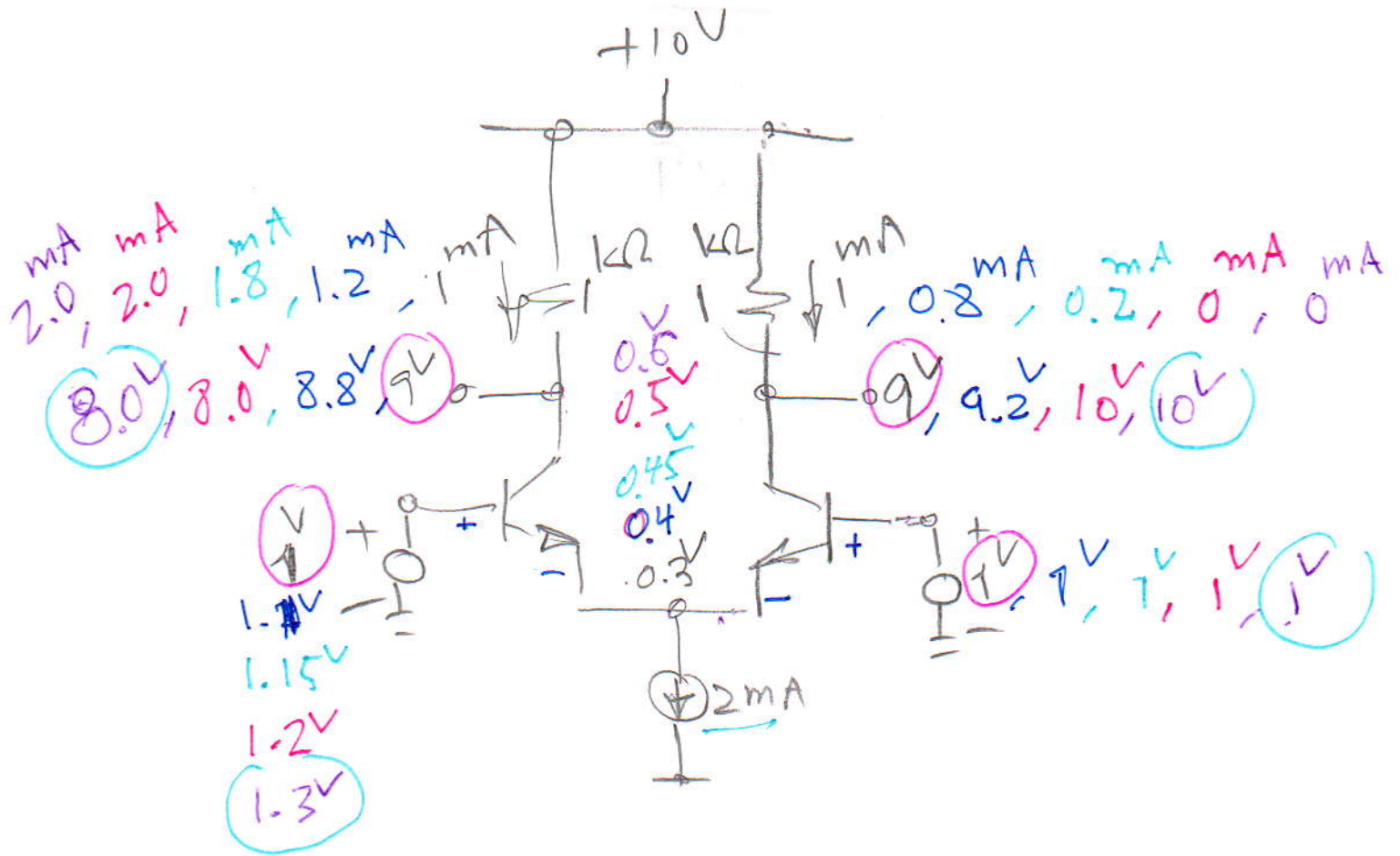

u


u u

u

u u

AC Analysis

5/

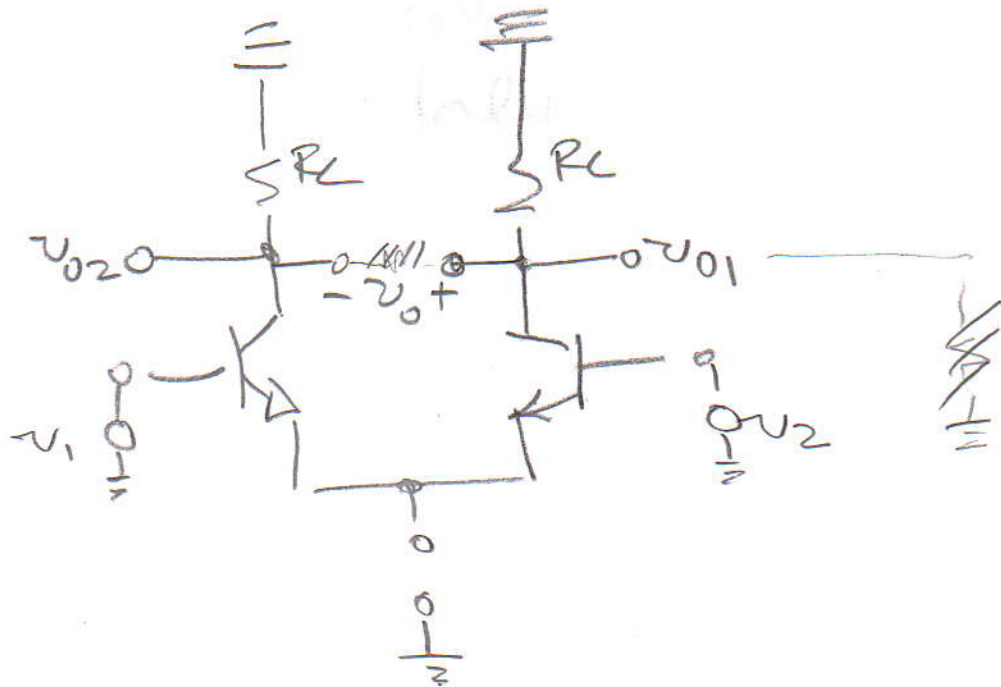

$$A_d = \frac{v_{o1}}{v_1 - v_2} = \frac{v_{o1}}{v_d} \quad \text{where } v_d = v_1 - v_2$$

$$A_d = \frac{v_{o2}}{v_1 - v_2} = \frac{v_{o2}}{v_d}$$


$$A_d = \frac{v_{o1} - v_{o2}}{v_1 - v_2} = \frac{v_o}{v_d}$$

How to do that?

— Superposition —
Sure, But tedious!

Superposition

#1 v_1 : on v_2 : off

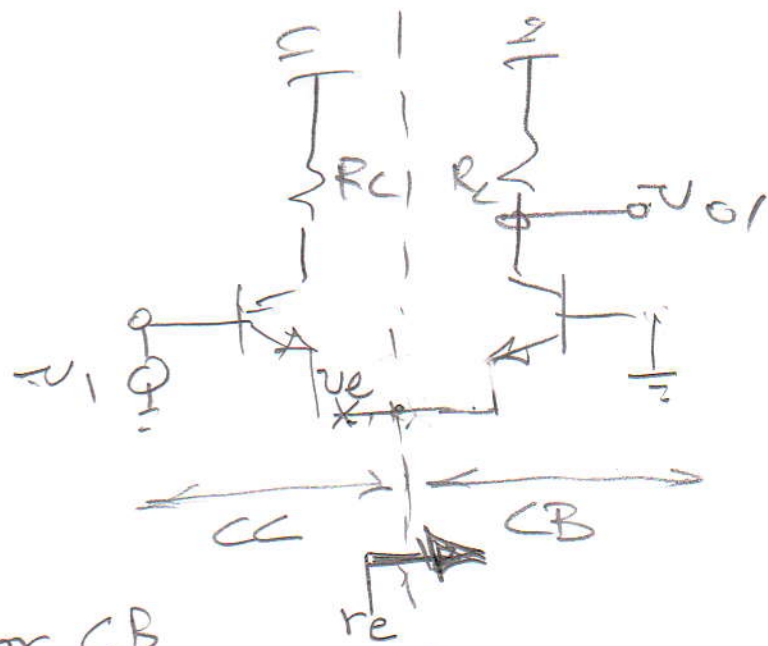


$$\frac{v_{01}}{v_1} = ?$$

for CB

$$\frac{v_{01}}{v_e} = g_m R_L$$

for CC

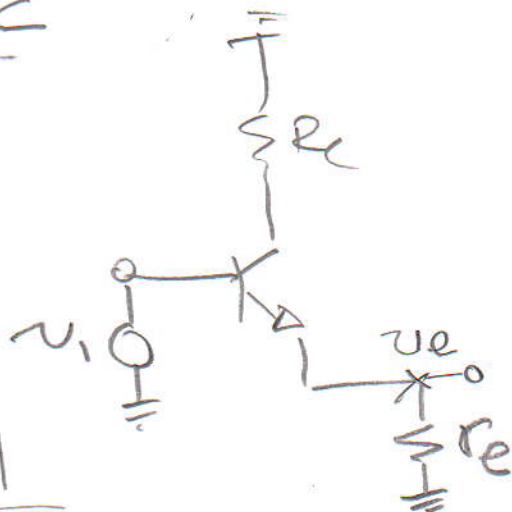

$$\frac{v_e}{v_1} = \frac{g_m r_e}{1 + g_m r_e} \approx \frac{1}{2}$$


Overall

$$\frac{v_{01}}{v_1} = \frac{v_{01}}{v_e} \times \frac{v_e}{v_1} = g_m R_L \times \frac{1}{2} \Rightarrow \boxed{\frac{v_{01}}{v_1} = \frac{1}{2} g_m R_L}$$

Superposition

7/

#2 v_1 : off, v_2 : on

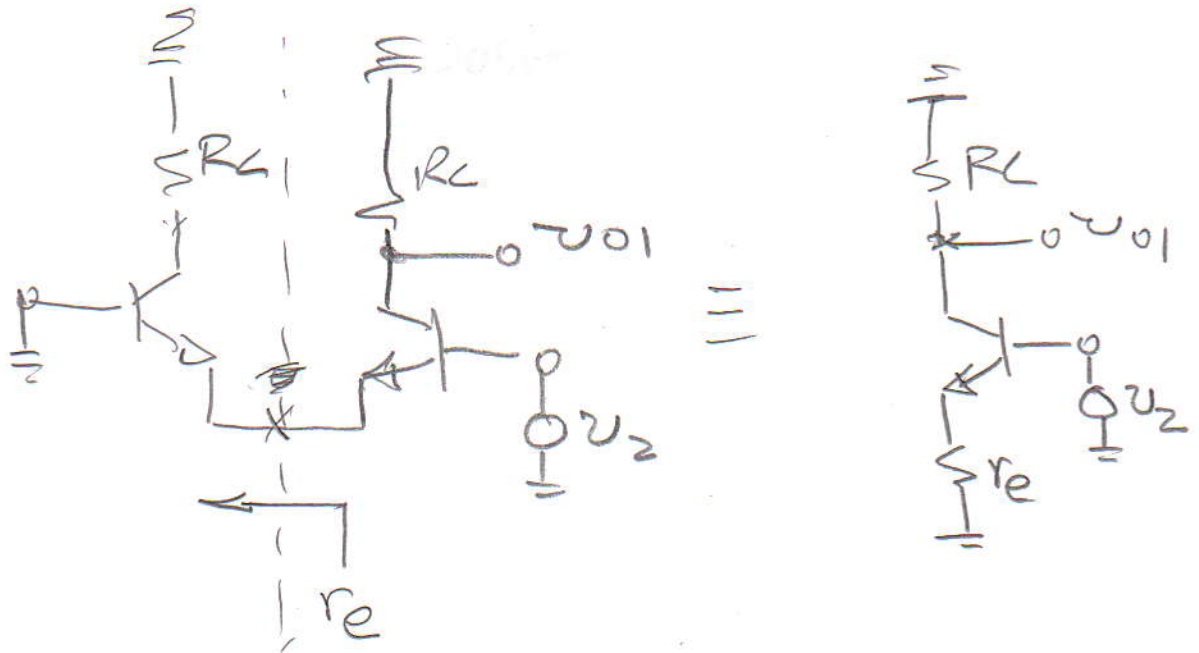

CE

$$\frac{v_{01}}{v_2} = \frac{-g_m R_C}{1 + g_m \underbrace{r_e}_{R_E}} = -\frac{1}{2} g_m R_C$$

Therefore,

$$\#1 \quad \frac{v_{01}}{v_1} = \frac{1}{2} g_m R_C \Rightarrow v_{01} = \left(\frac{1}{2} g_m R_C \right) v_1$$

$$\#2 \quad \frac{v_{01}}{v_2} = -\frac{1}{2} g_m R_C \Rightarrow v_{01} = \left(-\frac{1}{2} g_m R_C \right) v_2$$


$$\Rightarrow v_{01} = \left(\frac{1}{2} g_m R_C \right) v_1 + \left(-\frac{1}{2} g_m R_C \right) v_2$$

$$\Rightarrow v_o = \left(\frac{1}{2} g_m R_C \right) (v_1 - v_2) \Rightarrow \boxed{A_d = \frac{1}{2} g_m R_C}$$

Differential Amplifiers (cont'd)

8

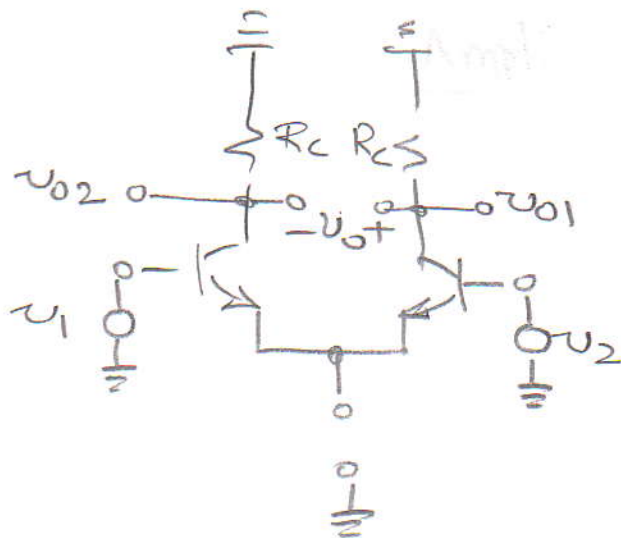Calculated the differential gain (last lecture) using superposition:



$$A_d = \frac{v_{01}}{v_1 - v_2} = \frac{1}{2} g_m R_C \quad (\text{if } v_{01} \text{ is the output})$$

$$A_d = \frac{v_{02}}{v_1 - v_2} = -\frac{1}{2} g_m R_C \quad (\text{if } v_{02} \text{ is the output})$$

$$A_d = \frac{v_0}{v_1 - v_2} = \frac{v_{01} - v_{02}}{v_1 - v_2} = g_m R_C \quad (\text{if } v_0 = v_{01} - v_{02} \text{ is the output})$$


Let us assume that v_{01} is the output:

$$\Rightarrow v_{01} = \underbrace{\left(\frac{1}{2} g_m R_C \right)}_{A_d > 0} (v_1 - v_2)$$

$$= A_d v_1 + (-A_d) v_2$$

$\Rightarrow v_{01} \uparrow \downarrow$ if $v_1 \uparrow \downarrow \Rightarrow v_1$: non-inverting input

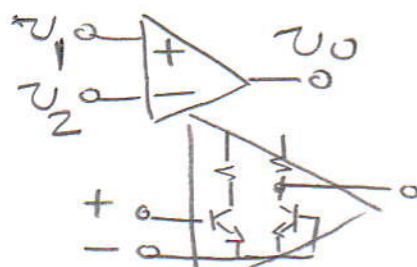$v_{01} \downarrow \uparrow$ if $v_2 \uparrow \downarrow \Rightarrow v_2$: inverting input



A Couple of Definitions

9/

$v_d \triangleq v_1 - v_2$: differential input

$v_{cm} \triangleq \frac{v_1 + v_2}{2}$: common-mode input

$$v_o = A_d v_d + A_{cm} v_{cm} \quad \text{superposition}$$

$$A_d: \text{differential gain} = \left. \frac{v_o}{v_d} \right|_{v_{cm}=0}$$

$$A_{cm}: \text{common-mode gain} = \left. \frac{v_o}{v_{cm}} \right|_{v_d=0}$$



An ideal differential amplifier features $A_{cm}=0 \Rightarrow$ the signal component common to both v_1 and v_2 , e.g., the exogenous ~~with~~ interference, will not appear in the output.

In practice, $A_{cm} \neq 0 \Rightarrow v_o$ will also be a function of $\frac{v_1 + v_2}{2}$. However, A_{cm} is very small (by proper design), in a commercial op-amp.

CMRR: Common-Mode Rejection Ratio $\triangleq \left| \frac{A_d}{A_{cm}} \right|$
CMRR is very large in a commercial amp.
 $CMRR(dB) = 20 \log \left| \frac{A_d}{A_{cm}} \right|$


61
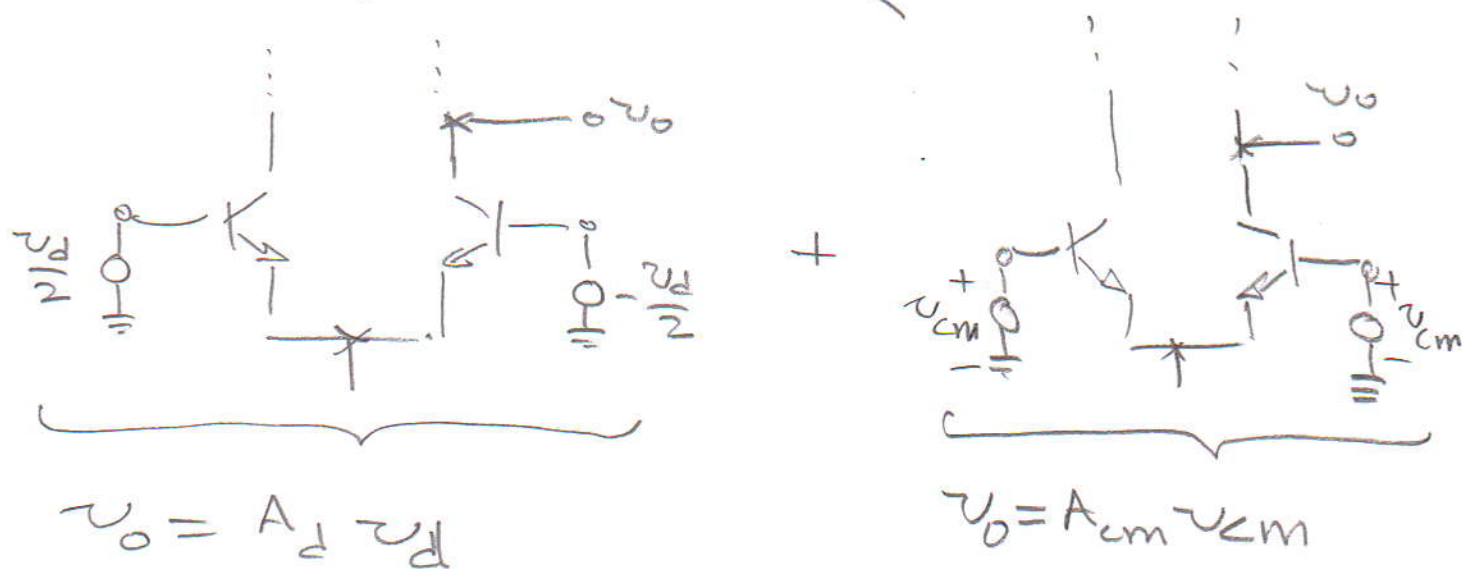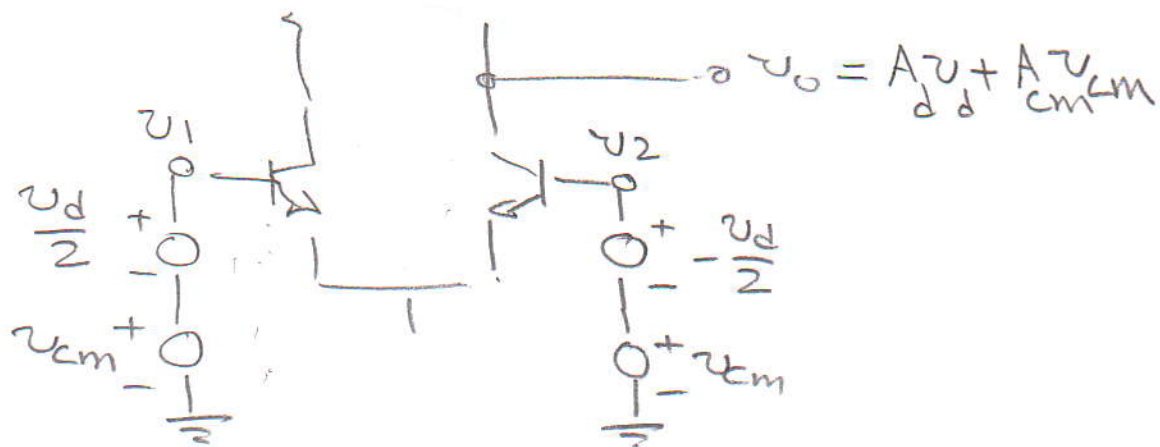
$$\begin{aligned}
 v_o &= v_{cm} + \frac{R_D}{2} v_2 \\
 v_o &= v_{cm} + \frac{R_D}{2} v_1
 \end{aligned}
 \Rightarrow v_2 = v_1$$





Calc. Common-mode gain

13

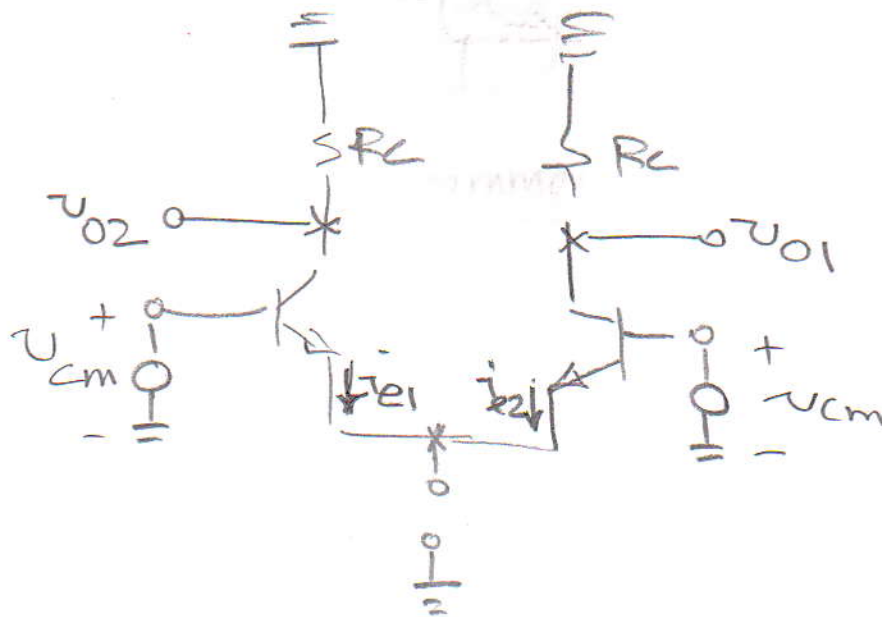

$$\left. \begin{array}{l} i_{e1} = i_{e2} \text{ (because the circuit is symmetrical)} \\ i_{e1} + i_{e2} = 0 \text{ (by KCL)} \end{array} \right\} \Rightarrow i_{e1} = i_{e2} = 0$$

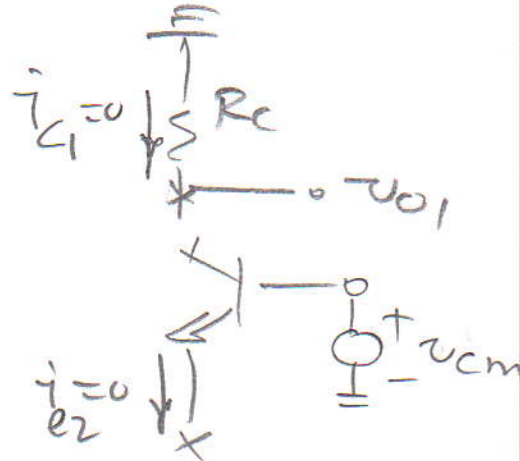
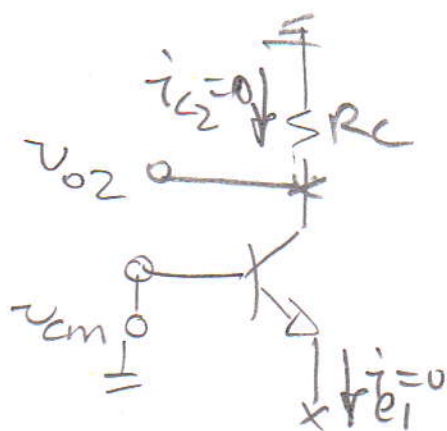
\Rightarrow The link between E_1 & E_2 can be cut open!




$$\left. \begin{array}{l} v_{o1} = 0 \\ v_{o2} = 0 \end{array} \right\} \Rightarrow A_{cm} = 0$$

Calc. Diff. Gain

11

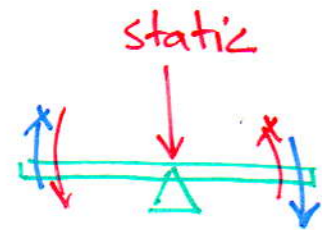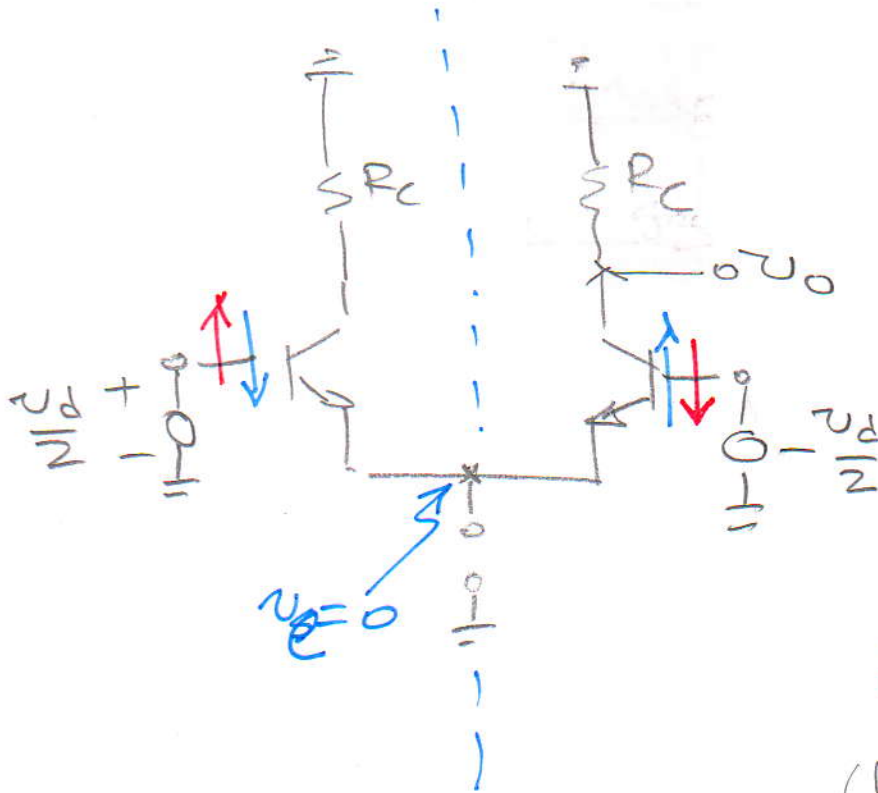

(Mechanical Analogy:
The Seesaw)

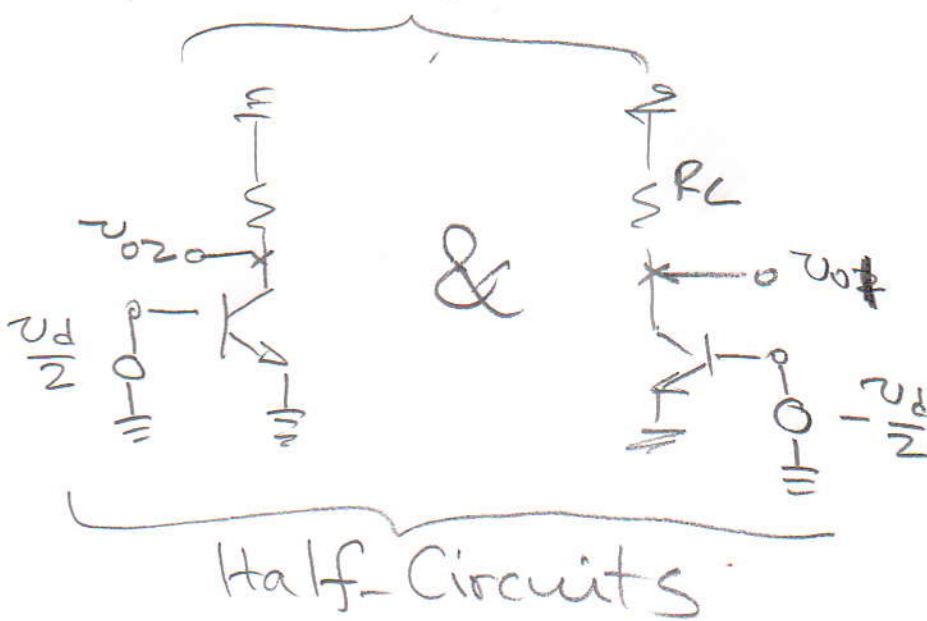


$$\frac{v_{o1}}{\left(\frac{v_d}{2}\right)} = -g_m R_C \Rightarrow \boxed{\frac{v_{o1}}{v_d} = -\frac{1}{2} g_m R_C}$$


$$\frac{v_{o2}}{\left(\frac{v_d}{2}\right)} = -g_m R_C \Rightarrow \boxed{\frac{v_{o2}}{v_d} = -\frac{1}{2} g_m R_C}$$


Situation for the Case with a non-ideal current source

13/

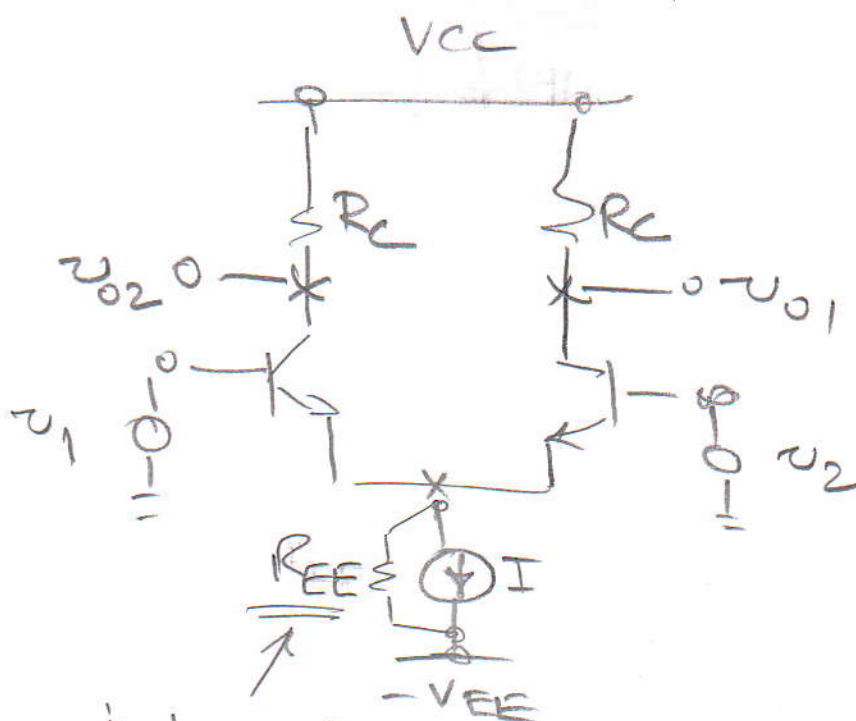

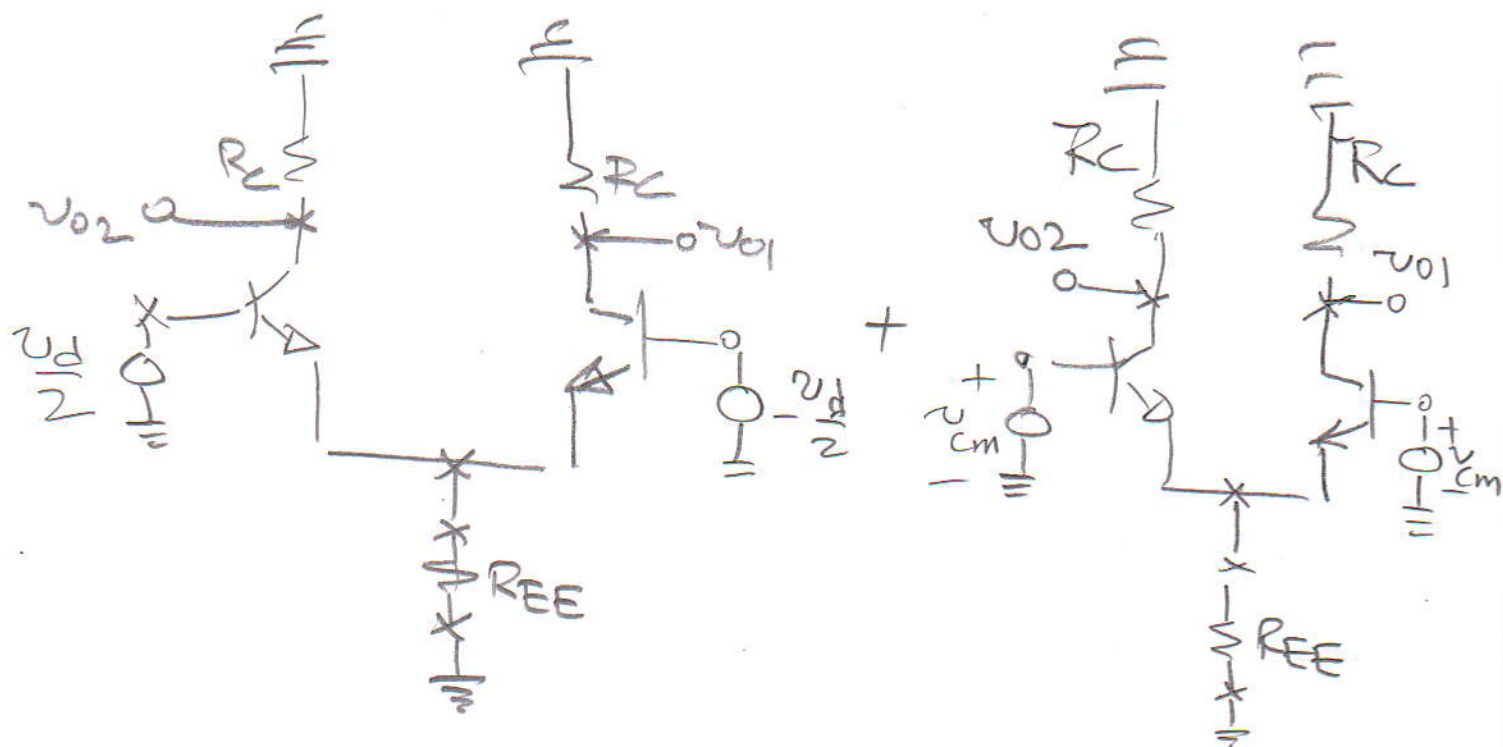internal resistance of the current source.



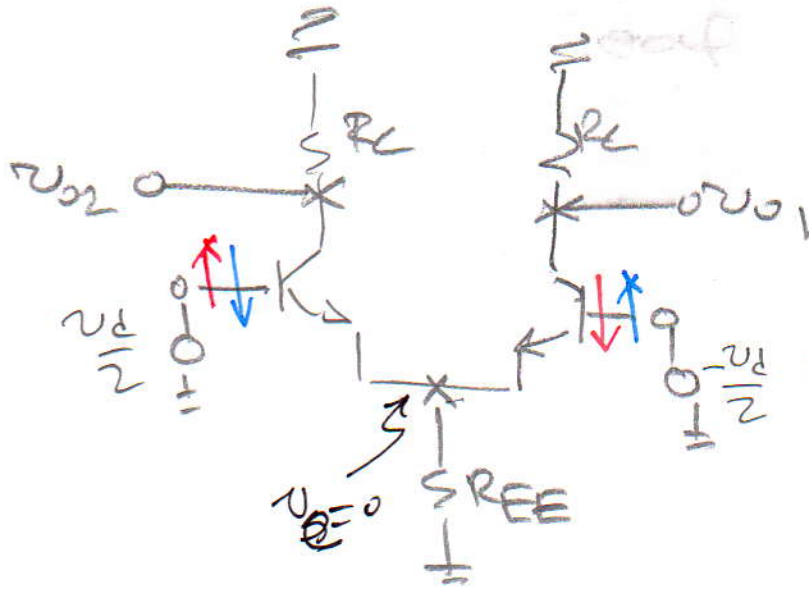


$$\Rightarrow \frac{v_{o1}}{\left(-\frac{v_d}{2}\right)} = -g_m R_C$$

$$\Rightarrow \boxed{\frac{v_{o1}}{v_d} = \frac{1}{2} g_m R_C}$$

$$\frac{v_{o2}}{\left(\frac{v_d}{2}\right)} = -g_m R_C$$

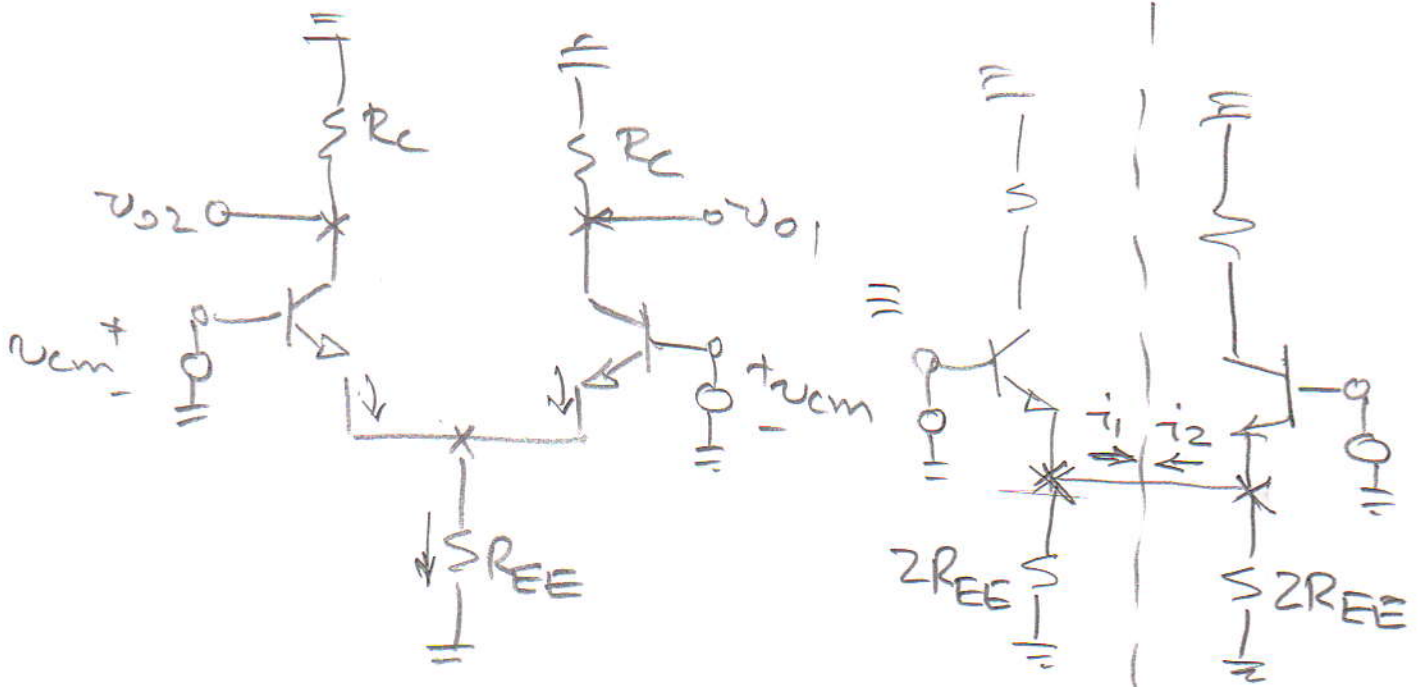
$$\Rightarrow \boxed{\frac{v_{o2}}{v_d} = -\frac{1}{2} g_m R_C}$$



$$i_1 = i_2 \text{ (Symmetry)}$$

$$i_1 + i_2 = 0 \text{ (by KCL)}$$

$$\Rightarrow i_1 = i_2 = 0$$

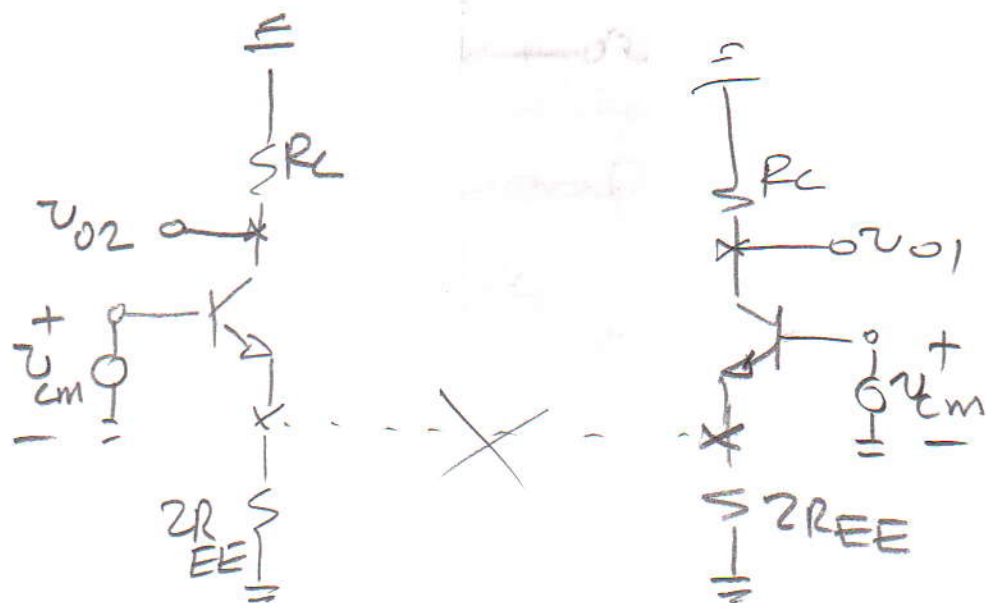

$$A_{cm} = \frac{v_{01}}{v_{cm}} = \frac{-g_m R_C}{1 + g_m (2R_{EE})}$$

$$A_{cm} = \frac{v_{02}}{v_{cm}} = \frac{-g_m R_C}{1 + g_m (2R_{EE})}$$

If $v_o \triangleq v_{01} - v_{02}$ was taken as the input, then $A_{cm} = 0$

Example

$$\Rightarrow I = 2\text{mA} \rightarrow g_m = 40\text{mS}$$

$$R_C = 1\text{k}\Omega$$


$$R_{EE} = 20\text{k}\Omega$$

$$A_d = \frac{1}{2} \times 40 \times 1\text{k}\Omega = 20 \frac{\text{V}}{\text{V}}$$

$$A_{cm} = \frac{-40 \times 1}{1 + 40 \times 40} \approx -\frac{1}{40} = -2.5 \times 10^{-2} \frac{\text{V}}{\text{V}}$$

$$\text{CMRR} = \left| \frac{20}{-2.5 \times 10^{-2}} \right| = \frac{2000}{2.5} = \frac{8000}{10} = 800$$

$$\text{CMRR (dB)} \approx 58\text{dB}$$

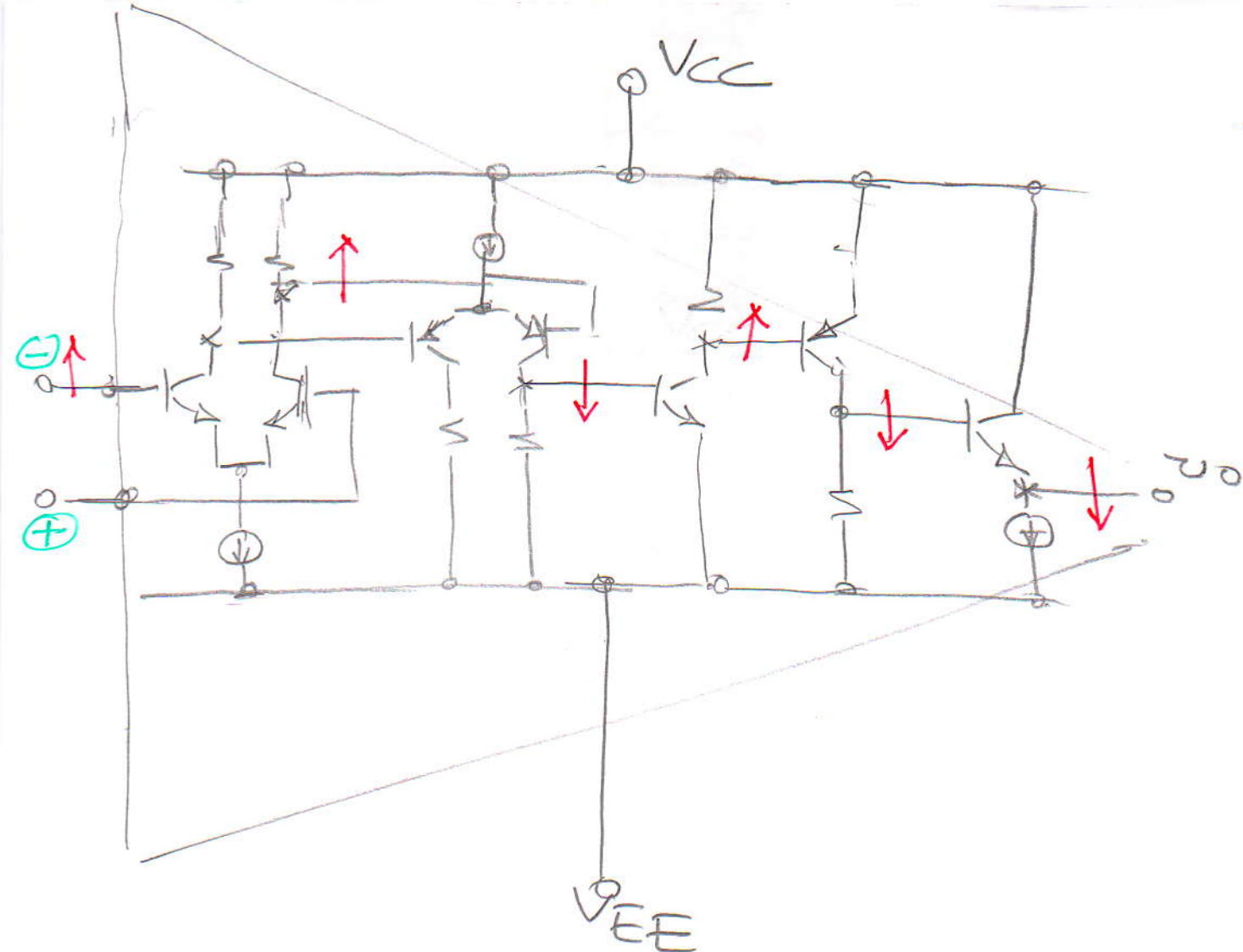

An increase in the top input has resulted in a decrease in the output. Therefore, the top input is the inverting input (-) whereas the bottom input is the non-inverting input (+).