

Ryerson University
Department of Electrical and Computer Engineering

ELE202: Electric Circuits Analysis
Final Examination, April, 29 2009
Duration: 3 hours

Solutions

- ☐ Prof. X. Gu
☐ Prof. A. Ye / Prof. T. Ghorab


NOTES:

1. Please **TICK** mark against the name of your professor.
2. This is a **Closed Book** examination. No aids other than the approved calculators are allowed.
3. Answer all **SIX** questions.
- 4.

Question No.	Mark for each question	Mark obtained
Q1	15	
Q2	15	
Q3	15	
Q4	20	
Q5	15	
Q6	20	
Total (100)		

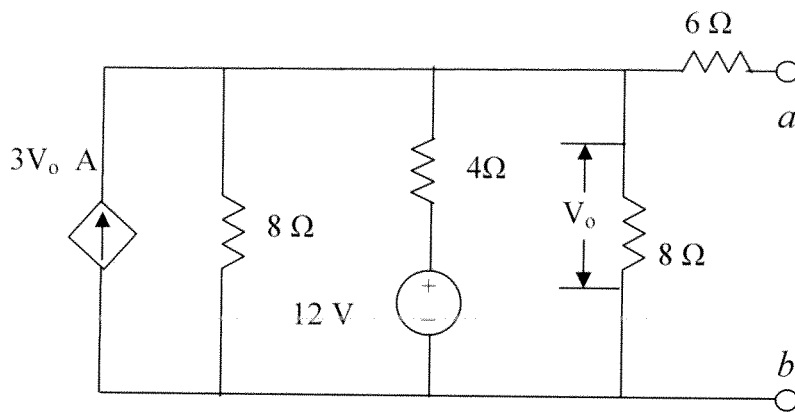
Problem 1 (15 marks):

Find the Thevenin equivalent, V_{th} and R_{th} , at terminal $a-b$ of the following circuit.



$$\begin{aligned} \text{or: } -3V_o + \frac{V_o}{8} + \frac{V_o - 12}{4} + \frac{V_o}{8} &= 0 \\ -12V_o + V_o + V_o - 12 &= 0 \\ -10V_o &= 12 \\ V_o &= -1.2 \\ V_{th} = V_o &= -1.2 \text{ V} \\ (V_b > V_a) \end{aligned}$$

a) Find V_{th} .

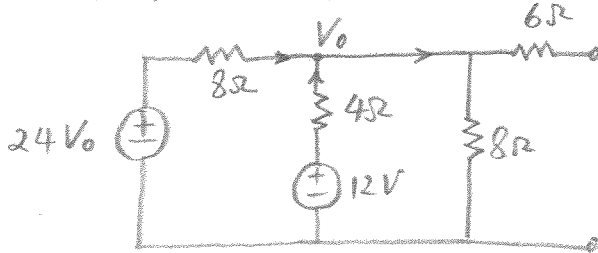

The node voltage is the same as V_o , using nodal analysis


$$\frac{24V_o - V_o}{8} + \frac{12 - V_o}{4} = \frac{V_o}{8} \quad \underline{\underline{3}}$$

$$\frac{23V_o}{8} - \frac{3V_o}{8} = -3$$

$$V_o = \frac{-24}{20} = -1.2 \text{ V} = V_{th} \quad \underline{\underline{2}} \quad \textcircled{1}$$

b) Find R_{th} . Apply 1V source across terminal $a-b$, and combine 4 ohm and 8 ohm branches

2 cct

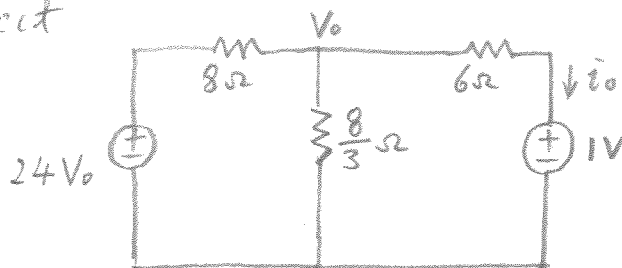

$$i_o = \frac{-\frac{1}{14} - 1}{6} = \frac{-15}{14 \times 6} = \frac{-5}{28} = -0.179 \text{ A} \quad V_o = \frac{-4}{56} = \frac{-1}{14} \quad \underline{\underline{2}}$$


$$\underline{\underline{3}} \quad R_{th} = \frac{1}{i_o} = \frac{28}{5} = 5.6 \Omega$$

$$\text{answers} = \begin{cases} V_{th} = -1.2 \text{ V} & (V_b > V_a) \\ R_{th} = 5.6 \Omega \end{cases}$$

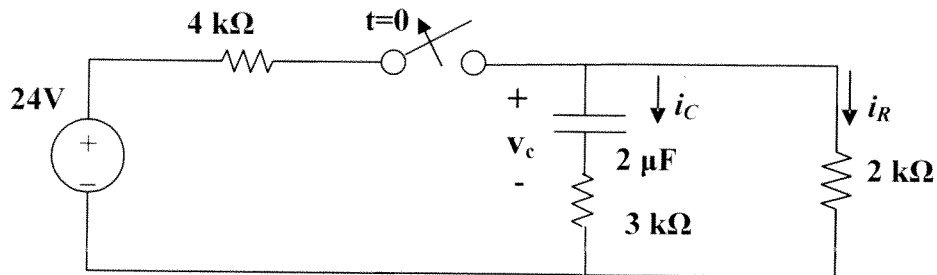Problem 2 (15 marks):

In the circuit below, the switch was closed for a long time and is opened at $t = 0$.

Find $i_R(t)$, $i_C(t)$ and $v_C(t)$ for $t < 0$ and $t > 0$.



For $t < 0$, switch is closed,

$$\textcircled{1} \quad i_C = 0$$

$$\textcircled{2} \quad i_R = \frac{24}{(4+2) \times 10^3} = 4 \text{ mA}$$

$$\textcircled{2} \quad V_C = 24 \cdot \frac{2}{(4+2)} = 8 \text{ V}$$

Notice that 3 kΩ Resistor
doesn't play a role in V_C
calculation

For $t > 0$, The right loop forms a sourceless cct,

$$\textcircled{1} \quad \tau = RC = (3+2) \times 10^3 \times 2 \times 10^{-6} = 10^{-2} = 0.01 \text{ sec}$$

$$\textcircled{1} \quad V_C(0) = 8 \text{ V},$$


$$\textcircled{1} \quad V_C(\infty) = 0 \text{ V}$$

$$\textcircled{2} \quad V_C(t) = V_C(0) e^{-t/\tau} = 8 e^{-100t}$$

$$\textcircled{2} \quad i_C(t) = C \frac{dV_C}{dt} = 2 \times 10^{-6} \cdot 8 \times (-100) e^{-100t} = -1.6 e^{-100t} \text{ mA},$$

$$\textcircled{2} \quad i_R(t) = -i_C(t) = 1.6 e^{-100t} \text{ mA}$$


(cw)
 $\textcircled{1}$

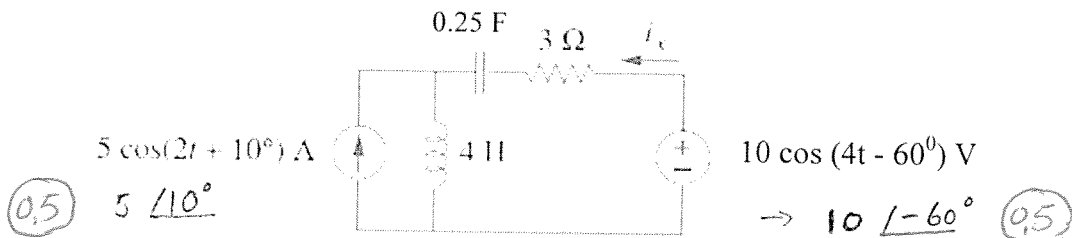Problem 3 (15 marks):Using superposition principle, find $i_x(t)$ in the circuit below.

Let $i_x = i_1 + i_2$,

i_1 — due to voltage source

i_2 — " current source.

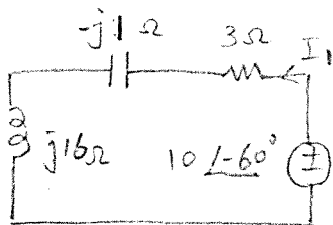

$$I_1 = \frac{10 \angle -60^\circ}{3 + j16 - j2} = \frac{10 \angle -60^\circ}{3 + j15} = \frac{10 \angle -60^\circ}{15.297 \angle 78.69^\circ}$$

$$I_1 = 0.6537 \angle -138.69^\circ \quad (4) \quad (-0.491 - j0.4314)$$

(0.5) $i_1(t) = 0.6537 \cos(4t - 138.69^\circ) \text{ A}$

Use current division:

$$\begin{aligned}
 I_2 &= 5 \angle 10^\circ \frac{-j8}{3 - j2 + j8} = \frac{-40j \angle 10^\circ}{3 + j6} \\
 &= \frac{-40j \angle 10^\circ}{6.708 \angle 63.43^\circ} = 5.963 \angle -90^\circ - 10^\circ - 63.43^\circ
 \end{aligned}$$

$$I_2 = 5.963 \angle -143.43^\circ \quad (4) \quad (-4.79 - j3.553)$$


(0.5) $i_2(t) = 5.963 \cos(2t - 143.43^\circ) \text{ A}$

(1) $i_x = i_1(t) + i_2(t)$

$$\begin{aligned}
 &= 0.6537 \cos(4t - 138.69^\circ) \\
 &\quad + 5.963 \cos(2t - 143.43^\circ) \text{ A}
 \end{aligned}$$

Problem 4 (20 marks):

Using nodal analysis, find the phasor voltage V_1 and V_2 in the following circuit.

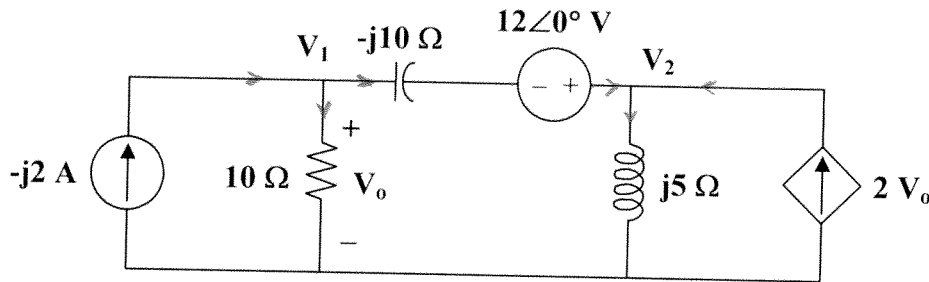at V_1

$$-j2 = \frac{V_1}{10} + \frac{V_1 - V_2 + 12}{-j10} \quad (5)$$

$$\textcircled{x} -j10, \quad -20 = -jV_1 + V_1 - V_2 + 12$$

$$(1-j)V_1 - V_2 = -32 \quad (2)$$

add two eqs. $(2-21j)V_1 = -44$

$$V_1 = \frac{-44}{2-21j} = \frac{-44}{21.095 \angle -84.56^\circ}$$

$$= -2.086 \angle 84.56^\circ$$

$$= 2.086 \angle 84.56^\circ - 180^\circ$$

$$= 2.086 \angle -95.44^\circ \text{ V}$$

$$= -0.1978 - j2.077 \quad (3)$$

at V_2

$$\frac{V_1 - V_2 + 12}{-j10} + 2V_1 = \frac{V_2}{j5} \quad (5)$$

$$\textcircled{x} -j10, \quad V_1 - V_2 + 12 - 20jV_1 = -2V_2$$

$$(1-20j)V_1 + V_2 = -12 \quad (2)$$

substitute V_1 into above eq.

$$V_2 = -12 - (1-20j) \times 2.086 \angle -95.44^\circ$$

$$= -12 - 20.025 \angle -87.14^\circ \times 2.086 \angle -95.44^\circ$$

$$= -12 - 41.772 \angle -182.58^\circ$$

$$= -12 + 41.772 \angle 2.58^\circ$$

$$= -12 + 41.772 (0.999 - j0.0450)$$

$$= -12 + 41.73 - j1.8797$$


$$= 29.73 - j1.8797$$

$$= 29.789 \angle -3.618^\circ \text{ V}$$

$$= 29.729 - j1.8797 \quad (3)$$

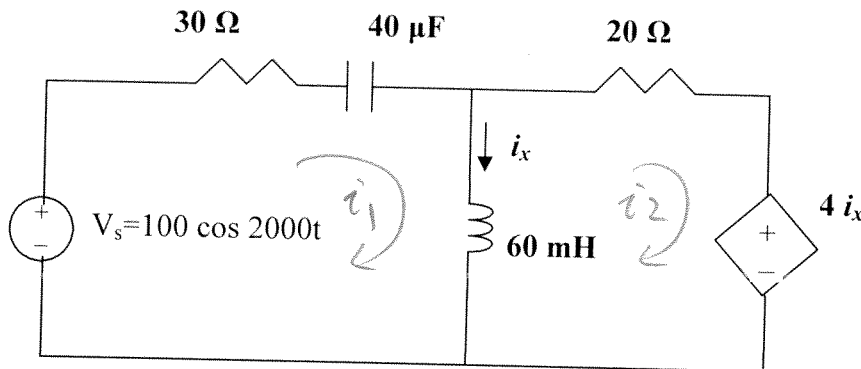Problem 5 (15 marks):

In the circuit below: find the time-domain expression for current $i_x(t)$ using mesh analysis.



$$\omega = 2000 \text{ rad/s}$$

$$40 \mu\text{F} \rightarrow \frac{1}{j\omega C} = -j12.5 \Omega$$

$$60 \text{ mH} \rightarrow j\omega L = j120 \Omega$$

$$V_s = 100 \angle 0^\circ$$

From Left loop :

$$\textcircled{3} \quad -100 + i_1(30 - j12.5 + j120) - j120 i_2 = 0$$

$$\textcircled{2} \quad (30 + j107.5) i_1 - j120 i_2 = 100$$

Substitute i_1 into above eq.

$$(30 + j107.5)(0.9945 - j0.1665) i_2 - j120 i_2 = 100$$

$$(29.835 - j4.995 + j106.91 + 17.90 - j120) i_2 = 100$$

$$\textcircled{1} \quad i_2 = \frac{100}{47.735 - j18.085} = \frac{100}{51.046 \angle -20.75^\circ}$$

$$= 1.959 \angle 20.75^\circ \text{ A}$$

$$= 1.832 + j0.694$$

$$\textcircled{1} \quad i_1 = 1.975 \angle 11.25^\circ$$

$$= 1.937 + j0.385 \text{ A}$$

$$i_x = i_1 - i_2 = 0.105 - j0.309$$

$$= 0.326 \angle -71.23^\circ \text{ A}$$

From right Loop :

$$\textcircled{3} \quad i_2(20 + j120) + 4i_x - j120 i_1 = 0$$

$$i_x = i_1 - i_2 \quad \textcircled{1}$$

$$(200 + j120) i_2 + 4i_1 - 4i_2 - j120 i_1 = 0$$

$$(4 - j120) i_1 + (16 + j120) i_2 = 0$$

$$\textcircled{2} \quad (1 - j30) i_1 + (4 + j30) i_2 = 0$$

$$i_1 = \frac{-(4 + j30)}{(1 - j30)} i_2 = \frac{i_2}{901} (896 - j150)$$

$$= (0.9945 - j0.1665) i_2$$

$$= 1.0083 \angle -9.504^\circ i_2$$

$\textcircled{1}$

$$i_x(t) = 0.326 \cos(2000t - 71.23^\circ) \text{ A}$$


$\textcircled{0.5}$

Problem 6 (20 marks):

A sinusoidal voltage source with $V(t) = 10\cos 100t$ V is connected to a load as shown below.

Find: a) the load impedance of inductive branch, Z_2 ; phase current, \bar{I}_2 , complex power, \bar{S}_2 and power factor pf_2 (indicate leading or lagging pf). Draw its power triangle.

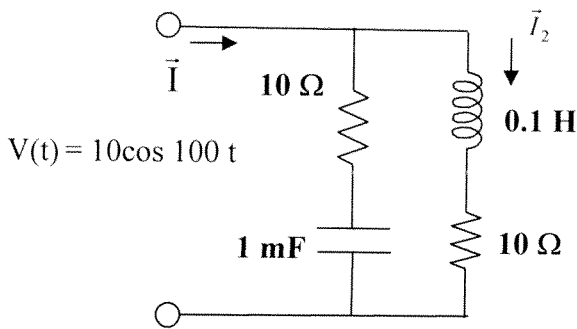b) load impedance, Z_{tot} ; phase current, \bar{I} and complex power, \bar{S} for the source.



$$\omega = 100 \text{ rad/s}$$

$$0.1 \text{ H} \rightarrow j\omega L = j10 \Omega \quad (1)$$

$$1 \text{ mF} \rightarrow \frac{-j}{\omega C} = -j10 \Omega \quad (1)$$

$$\vec{V} = 10 \angle 0^\circ$$

$$a) Z_2 = 10 + j10 = 10\sqrt{2} \angle 45^\circ \Omega$$


$$\bar{I}_2 = \frac{\vec{V}}{Z_2} = \frac{10}{10 + j10} = \frac{1}{1 + j} = \frac{1}{\sqrt{2} \angle 45^\circ}$$

$$= 0.707 \angle -45^\circ = 0.5 - j0.5 \text{ A}$$

$$\bar{S}_2 = \frac{1}{2} \vec{V} \cdot \bar{I}_2^* = \frac{10}{2} \times 0.707 \angle 45^\circ = 3.54 \angle 45^\circ$$

$$= \frac{1}{2} (5 + j5) = 2.5 \text{ (W)} + j2.5 \text{ (V}\cdot\text{A)}$$
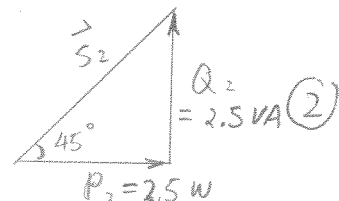
$$\text{pf}_2 = \cos 45^\circ = 0.707 \text{ (Lagging)} \quad (1)$$



a)	Z_2	$10 + j10 \Omega$	(2)
	\bar{I}_2	$0.707 \angle -45^\circ \text{ A}$	(2)
	\bar{S}_2	$2.5 + j2.5$	(3)
	pf_2	0.707 Lagging	(2)
b)	Z_{tot}	10Ω	(2)
	\bar{I}	$1 \angle 0^\circ \text{ A}$	(2)
	\bar{S}	5 W	(2)

b) The left branch of the Load:

$$Z_1 = 10 - j10 \Omega$$

$$Z_{\text{tot}} = Z_1 \parallel Z_2 = \frac{10(1-j) \cdot 10(1+j)}{10-j10 + 10+j10}$$

$$= \frac{100 \times 2}{20} = 10 \Omega$$

$$\bar{I} = \frac{\vec{V}}{Z_{\text{tot}}} = \frac{10 \angle 0^\circ}{10} = 1 \angle 0^\circ \text{ A}$$

$$\bar{S} = \frac{1}{2} \vec{V} \cdot \bar{I}^* = \frac{1}{2} \times 10 \times 1 = 5, \quad \bar{S} = P = 5 \text{ W}$$