

# Solution & Marking scheme

## Ryerson University

Department of Electrical and Computer Engineering

**ELE404** (Electronic Circuits I)

**Midterm Examination (P2013)**

**May 2013**

**Duration: 120 minutes**

Examiner: Prof. A. Yazdani

Name:.....  
[Print Last Name] [Print First Name]

Student No:..... Section:....

### NOTES


1. This is a closed-book examination. No aids other than basic calculators are permitted.
2. The examination paper is comprised of **FOUR QUESTIONS**, *each* question worth as indicated in the following Table. The entire examination is worth *100* marks.

Question #	Maximum Mark	Mark Earned
1	<b>30</b>	
2	<b>30</b>	
3	<b>10</b>	
4	<b>30</b>	
Total	100	

3. Answer all questions in the booklet, within the blank spaces provided under each question in this booklet. Use the reverse if needed.
4. **No Questions to be asked during the examination.** *If in doubt about any question, clearly state your assumptions in answering the question.*
5. Part marks for an answer will only be given if the *correct methodology* is clearly shown.
6. **DO NOT DETACH** any pages from this booklet.

Q1: In the diode circuit of **Fig. 1**, the diodes assume a constant voltage drop of  $0.7\text{ V}$  if they conduct, and  $R_1 = 1.2\text{ k}\Omega$ ,  $R_2 = 2.7\text{ k}\Omega$ ,  $R_3 = 1.8\text{ k}\Omega$ , and  $R_4 = 3.3\text{ k}\Omega$ . Showing all the work, determine the conduction states ("on" or "off") of the diodes, and calculate the voltages  $V_1$  through  $V_3$ . Summarize your findings in **Table 1**.

Each answer worth (5) marks provided that they are supported by the calculations of the next page, especially the checkings. Otherwise, deduct considerable mark

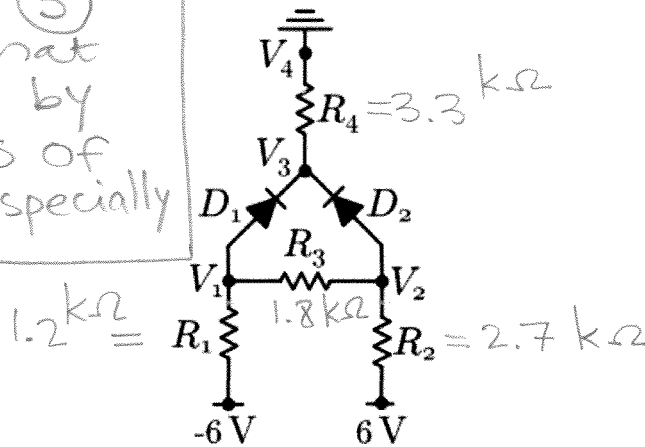

**Fig. 1:** Diode circuit of Q1.

**Table 1:** Results of the diode circuit of Q1. [each five marks]

$D_1$	$D_2$	$V_1 [\text{V}]$	$V_2 [\text{V}]$	$V_3 [\text{V}]$	$V_4 [\text{V}]$
OFF	OFF	-3.47	0.316	0	0


systematically, we would solve the circuit for each of the following assumed states, and check the corresponding conditions, until we found the correct state:

state#	$D_1$	$D_2$
1	ON	ON
2	ON	OFF
3	OFF	ON
4	OFF	OFF

However, we show here that state #4 is the right state and consistent with the conditions:

State #4

D1: OFF, D2: OFF

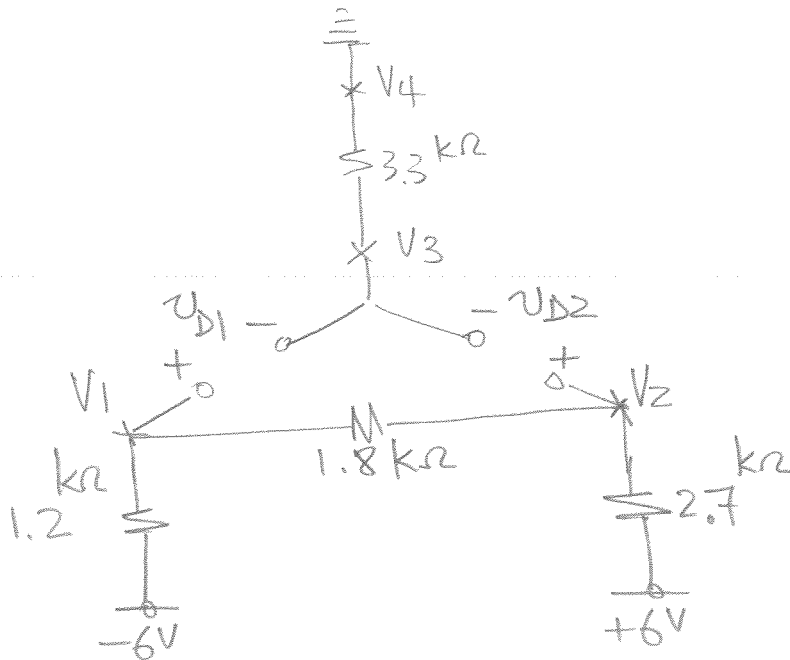 $V_4 = 0$  (the ground) $V_3 = V_4 = 0$  due to zero current in  $R_4$ 

$$V_1 = \frac{-6}{1.2 + 1.8 + 2.7} \times (1.8 + 2.7) + \frac{6}{1.2 + 1.8 + 2.7} \times 1.2 = -3.47 \text{ V}$$

$$V_2 = \frac{6}{1.2 + 1.8 + 2.7} \times (1.8 + 1.2) + \frac{-6}{1.2 + 1.8 + 2.7} \times 2.7 = 0.316 \text{ V}$$


checking

$$u_{D1} = V_1 - V_3 = -3.47 - 0 = -3.47 \text{ V} < 0.7 \text{ V} \checkmark \text{ diode "off"}$$


$$u_{D2} = V_2 - V_3 = 0.316 - 0 = 0.316 \text{ V} < 0.7 \text{ V} \checkmark \text{ diode "off"}$$

**Blank Page**

Q2: Assuming ideal diodes, derive and mathematically express the transfer characteristic ( $v_I - v_O$  characteristic) of the diode circuit of **Fig. 2a**. Then, plot the transfer characteristic on **Fig. 2b**.

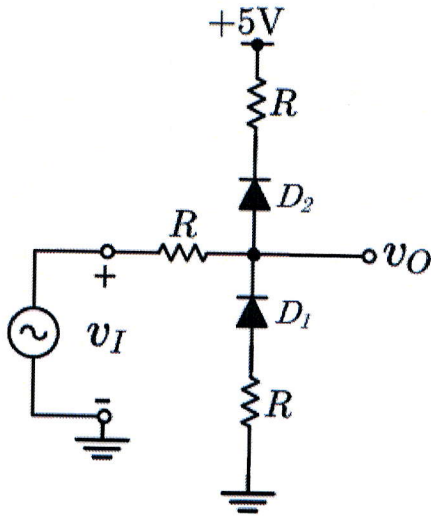


**Fig. 2a:** Diode circuit of Q2.

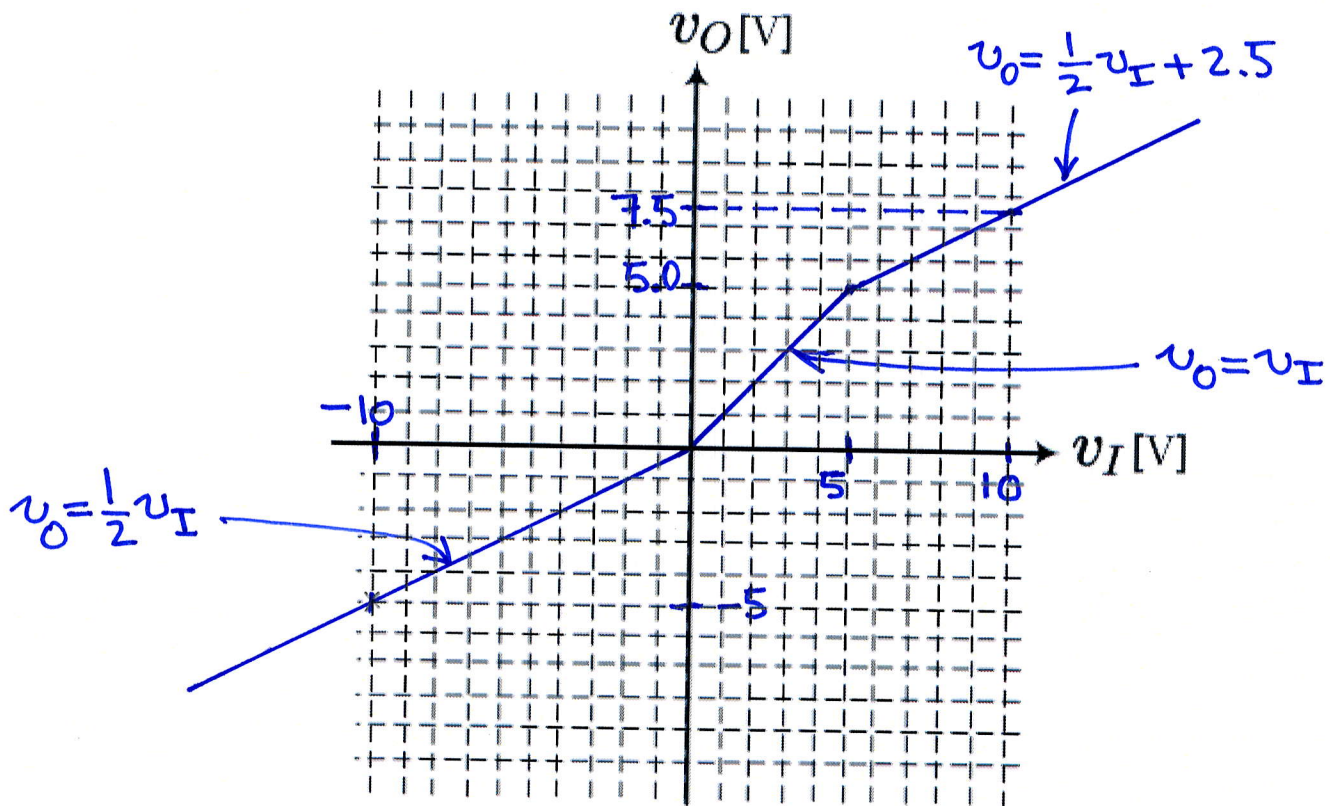

**Fig. 2b:** Transfer characteristic of the diode circuit of Fig. 2a.

start with  $v_I \rightarrow -\infty$  (very negative)

$D_1$ : ON  $D_2$ : OFF

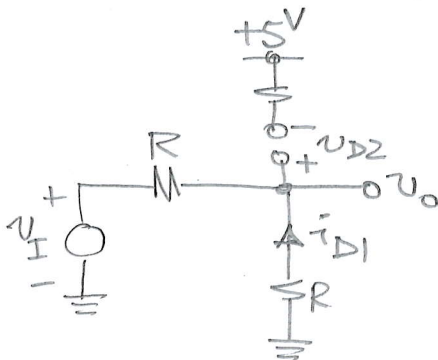

$$v_O = \frac{v_I}{R+R} \times R = \frac{1}{2} v_I$$


$$i_{D1} = -\frac{v_I}{R+R} \quad (1)$$

$$v_{D2} = v_O - 5 = \frac{1}{2} v_I - 5 \quad (2)$$

$$\left. \begin{array}{l} i_{D1} > 0 \xrightarrow{(1)} \frac{-v_I}{R+R} > 0 \Rightarrow v_I < 0 \\ v_{D2} < 0 \xrightarrow{(2)} \frac{1}{2} v_I - 5 < 0 \Rightarrow v_I < 10 \end{array} \right\} \Rightarrow \boxed{-\infty < v_I < 10}$$

Then, if  $v_I > 0$

$D_1$ : OFF  $D_2$ : OFF

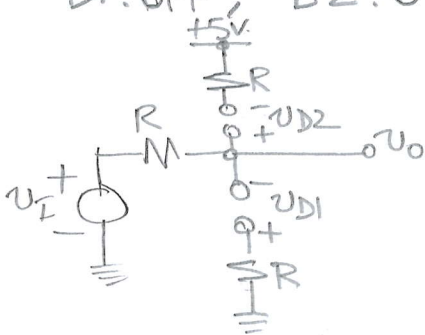

$$\boxed{v_O = v_I}$$

$$v_{D1} = 0 - v_O = -v_O = -v_I \quad (3)$$

$$v_{D2} = v_O - 5 = v_I - 5 \quad (4)$$


$$v_{D1} < 0 \xrightarrow{(3)} -v_I < 0 \Rightarrow v_I > 0 \text{ (which holds)}$$

$$v_{D2} < 0 \xrightarrow{(4)} v_I - 5 < 0 \Rightarrow v_I < 5$$

Therefore,  $v_O = v_I$  if  $\boxed{0 < v_I < 5}$

Then, if  $v_I > 5$

$D_1$ : OFF,  $D_2$ : ON

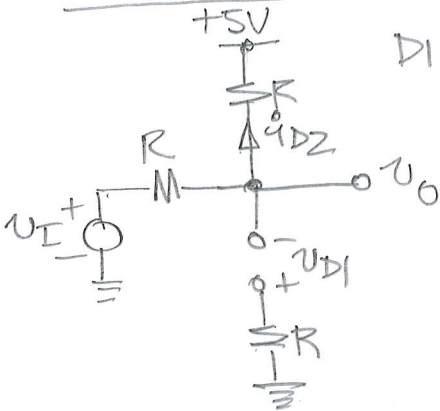

$$v_O = \frac{v_I}{R+R} \times R + \frac{5}{R+R} \times R$$

$$\Rightarrow \boxed{v_O = \frac{1}{2} v_I + 2.5}$$

$$v_{D1} = 0 - v_O = -\frac{1}{2} v_I + 2.5 \quad (5)$$

$$i_{D2} = \frac{v_O - 5}{R} = \frac{v_I - 5}{2R} \quad (6)$$

$$v_{D1} < 0 \stackrel{(5)}{\Rightarrow} -\frac{1}{2}v_I + 2.5 < 0 \Rightarrow v_I > 5 \text{ (which holds)}$$

$$i_{D2} > 0 \stackrel{(6)}{\Rightarrow} \frac{v_I - 5}{2R} > 0 \Rightarrow v_I - 5 > 0 \Rightarrow v_I > 5 \text{ (which holds)}$$

$$\text{So, } v_O = \frac{1}{2}v_I + 2.5 \text{ if } \boxed{v_I > 5}$$

The characteristic, then, is

$$v_O = \begin{cases} \frac{1}{2}v_I & \text{if } v_I < 0 \\ v_I & \text{if } 0 < v_I < 5 \\ \frac{1}{2}v_I + 2.5 & \text{if } v_I > 5 \end{cases}$$

The plot consists of 3 lines; as depicted on Fig. 2b.

### Mark breakdown

- Each region with the corresponding expression for  $v_O$  worth (5) marks 3 × (5)

- Each line on the plot of Fig. 2b worth (5) marks.

3 × (5)  
total (30) marks



Q3: For the clamping circuit of Fig. 3a, assume that the diode exhibits a constant forward voltage drop of  $0.7\text{ V}$ , the capacitor has no initial charge, and the input signal  $v_I$  is zero until the instant  $t = t_0$ . Thereafter,  $v_I$  is given the voltage waveform shown by the topmost graph of Fig. 3b. Plot the waveforms of the voltages  $v_O$  and  $v_C$ , on Fig. 3b.

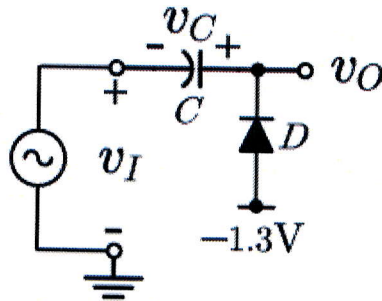


Fig. 3a: Clamping circuit of Q3.

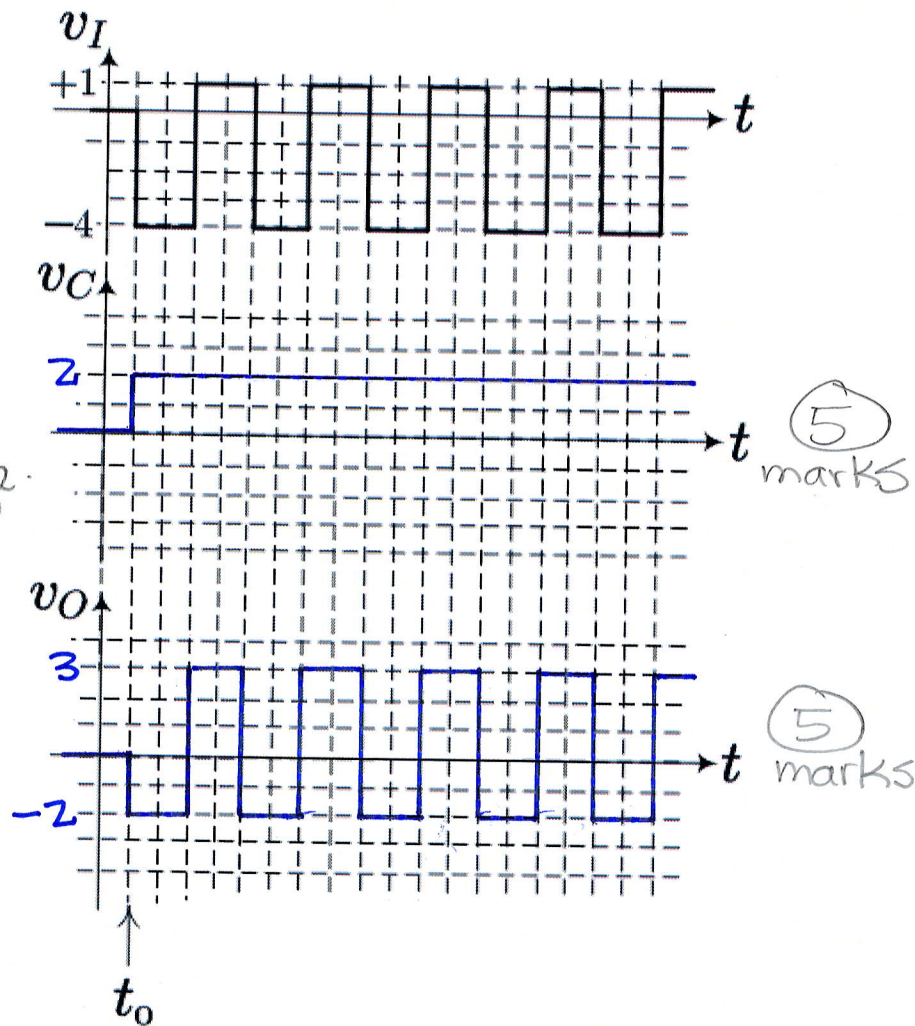


Fig. 3b: Voltage waveforms of the clamping circuit of Fig. 3a.

Explanations are not required; only the waveforms are to be marked.  
Explanations are, however, given on the next page.



### Explanation of the waveforms

Initially, the input, the capacitor voltage, and the output are all zero. At  $t=t_0$ , the input jumps down by  $5V$  (to  $-4V$ ), and, since the capacitor's voltage tends to remain at its initial value, the output also jumps down. Once this happens, the diode turns on and clamps the output voltage to  $-2V$  ( $-1.3V - 0.7V$ ). Therefore, the capacitor voltage jumps to  $V_C - V_I = -2 - (-4)$  or  $+2V$ . Thereafter, the capacitor voltage remains constant at  $2V$  (since it neither charges nor gets discharged), and the output voltage will always be  $2V$  more than the input voltage. That is why from  $t=t_0$  onwards,  $V_O$  is shifted-up version of  $V_I$ , by  $2V$ .


Q4: In the bridge rectifier of Fig. 4, the source voltage  $v_I$  is a 60-Hz, 24-Vrms sinusoid. Determine the *reading of a DC voltmeter* of the output voltage  $v_O$ , under each of the following conditions:

- (4a) Only the load  $R_L$  is connected (the smoothing capacitor  $C$  has been removed);
- (4b) Only  $C$  is connected ( $R_L$  has been removed);
- (4c)  $R_L = 1.0\text{ k}\Omega$  and  $C = 100\text{ }\mu\text{F}$ ;
- (4d)  $R_L = 1.0\text{ k}\Omega$  and  $C = \infty$ ;
- (4e) Same as (4a) but with  $D_3$  and  $D_4$  removed; and
- (4f) Same as (4b) but with  $D_3$  and  $D_4$  removed.

Assume that the diodes are ideal and the meter does not draw any current. Support your answers by calculations and/or explanations. Summarize your results in **Table 4**.

**Table 4:** results of the circuit of Q4.

Answer of (4a)	Answer of (4b)	Answer of (4c)	Answer of (4d)	Answer of (4e)	Answer of (4f)
21.6	33.9	32.5	33.9	10.8	33.9

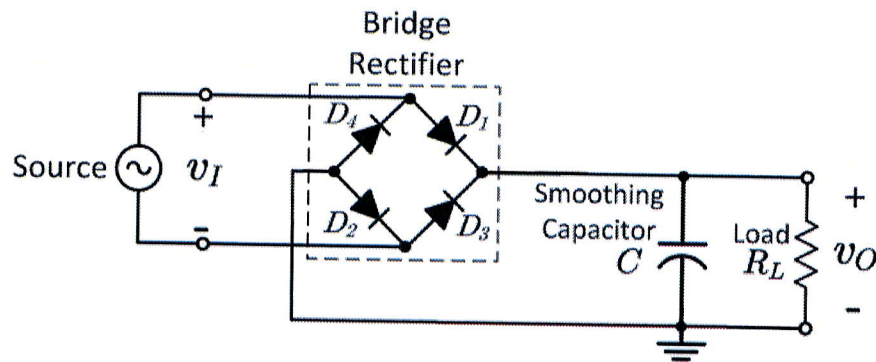

**Fig. 4:** Bridge rectifier of Q4.

Each item worth (5) marks if supported by the analyses of the next page.  $6 \times (5) = (30)$  marks total

4a) C: out  $R_L$ : in

The circuit is a full-wave rectifier with pure resistive load:

$$V_m = 24 \times \sqrt{2} = 33.9 \text{ V (peak value of } v_i)$$

∴ DC voltmeter shows the average voltage:


$$\overline{v_o} = \frac{2V_m}{\pi} = \frac{2 \times 33.9}{\pi} = 21.6 \text{ V}$$

4b) C: in  $R_L$ : out

The circuit turns into a peak detector; that is, the capacitor gets charged to the peak voltage  $V_m$ :

$$\overline{v_o} = V_m = 33.9 \text{ V}$$

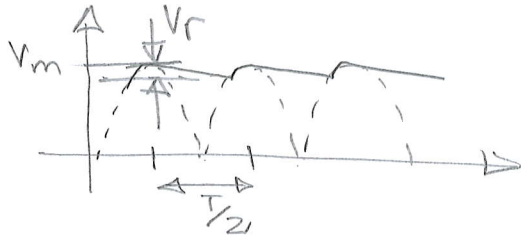4c) C = 100  $\mu$ F,  $R_L = 1.0 \text{ k}\Omega$



$V_m$ : peak voltage

$V_r$ : peak-to-peak ripple

$$\overline{v_o} = V_m - \frac{1}{2} V_r \text{ (average)}$$

Use equation (4.33) to calculate  $V_r$ :

$$V_r = \frac{V_m}{2fCR} = \frac{33.9}{2 \times 60 \times 100 \times 10^{-6} \times 1000} = 2.83 \text{ V}$$

$$\overline{v_o} = V_m - \frac{1}{2} V_r = 33.9 - \frac{1}{2} \times 2.83 = 32.5 \text{ V}$$

4d) C =  $\infty$ ,  $R_L = 1.0 \text{ k}\Omega$


Based on Eq. (4.33), if  $C = \infty$ , then  $V_r = 0$  (no ripple).  
Hence,

$$\overline{v_o} = V_m = 33.9 \text{ V}$$

4e) C: out, R<sub>L</sub>: in, D3 & D4: out

This turns the rectifier to a half-bridge rectifier
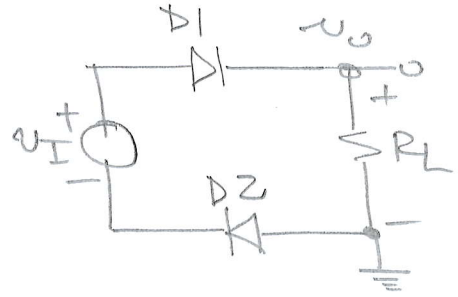
$$\overline{V_0} = \frac{V_m}{\pi} = \frac{33.9}{\pi} = \boxed{10.8 \text{ V}}$$



4f) C: in, R<sub>L</sub>: out, D3 & D4: out

The circuit becomes a half-wave peak detector, still capturing the peak

$$\overline{V_0} = V_m = \boxed{33.9 \text{ V}}$$