

ELE 202

Electric Circuit Analysis

LAB COVER PAGE for **Part I** submission.

Lab #:		Lab Title:	
--------	--	------------	--

Last Name:	
First Name:	

Student #:	
Signature:	Sayeed Ahamad

Section #:	
Submission date and time:	
Due date and time:	

Document submission for Part I:

- A completed and signed “COVER PAGE – **Part I**” has to be included with your submission. The report will not be graded if the signed cover page is not included.
- Your completed handwritten pages of **Section 4.0** should be scanned (via a scanner or phone images), together with the required MultiSIM images. **Note:** *MultiSIM results must be generated using the Department’s licensed version of MultiSIM, and the captured screenshots should show your name (at the center-top) and the timestamp (at the bottom-right corner of your screen).*
- Collate and create a **.pdf** or **.docx** file of the above, and upload it via D2L **any time prior to the start of your scheduled lab**. Upload instructions are provided on D2L.

Zero marks will be assigned for the entire lab if this Part I is not submitted prior to your scheduled lab.

**By signing above, you attest that you have contributed to this submission and confirm that all work you have contributed to this submission is your own work. Any suspicion of copying or plagiarism in this work will result in an investigation of Academic Misconduct and may result in a “0” on the work, an “F” in the course, or possibly more severe penalties, as well as a Disciplinary Notice on your academic record under the Student Code of Academic Conduct, which can be found online at: www.ryerson.ca/senate/current/pol60.pdf.*

Pre lab 3

Date: _____

a (i) $E = IR$

$$\frac{15}{3.3+2.2+1} = I = 2.307 \text{ mA}$$

$$V_a = 15 \text{ V}$$

$$V_d = 0 \text{ V}$$

$$V_b = 15 - (1)(2.307)$$
$$= 12.693 \text{ V}$$

$$V_{cd} = V_c - V_d$$
$$= 7.617 \text{ V}$$

$$V_c = V_b - IR_2$$

$$= 12.693 - 2.307(2.2)$$
$$= 7.617 \text{ V}$$

$$V_{ab} = V_a - V_b$$

$$= 15 - 12.693 = 2.307 \text{ V}$$

$$V_{bc} = V_b - V_c$$

$$= 12.693 - 7.617 = 5.076 \text{ V}$$

ii) $I = \frac{15}{3.3+2.2+1} = 2.307 \text{ mA}$

$$V_L = 0 \text{ V}$$

$$V_d = V_c - IR_2$$
$$= 0 - 2.307(3.3)$$
$$= -7.613 \text{ V}$$

$$V_a = V_d + 15$$
$$= 7.387$$

$$V_b = V_c + IR_2$$

$$= 0 + 2.307 \times 2.2$$
$$= 5.075 \text{ V}$$

$$V_{ab} = V_a - V_b$$
$$= 7.387 - 5.075$$
$$= 2.312 \text{ V}$$

$$V_{cd} = V_c - V_d$$
$$= 7.613 \text{ V}$$

$$V_{bc} = V_b - V_c$$
$$= 5.075 \text{ V}$$

iv) Current and P.d across resistors remain same. Because potential is dependant on reference assumed but P.d is independent of potential assumed.



Date: _____

b) $V_a = 15 \text{ V}$

$$\frac{15 - V_b}{2.2} + \frac{15 - V_c}{1} = 0$$

$$-V_b - 2 \cdot 2 V_c = -15 = 15 \times 2.2 \quad \text{eq i}$$
$$V_b + 2 \cdot 2 V_c = 48 \quad \text{eq i}$$

$$\frac{V_b - 15}{2.2} + \frac{V_b - V_c}{5 \cdot 1} + \frac{V_c}{3 \cdot 3} = 0$$
$$V_b \left[-\frac{1}{2.2} + \frac{1}{5 \cdot 1} + \frac{1}{3 \cdot 3} \right] - \frac{V_c}{5 \cdot 1} = 0 \quad \text{eq ii}$$

$$V_b = 22.43 \quad V_c = 11.619$$

$$I_x = 6.796 \text{ mA}$$

$$-15 + V_B + V_c = 0$$

$$V_B = 3.381$$

W.L mesh 1a

$$-15 + 2 \cdot 2 (I_A - I_C) + 3 \cdot 3 (I_A - I_B) = 0$$
$$I_A (5 \cdot 5) - 3 \cdot 3 I_B - 2 \cdot 2 I_C = 15 \quad \text{eq i}$$

$$3 \cdot 3 (I_B - I_A) + 5 \cdot 1 (I_B - I_C) + I_B = 0$$
$$-3 \cdot 3 I_A + 9 \cdot 4 I_B - 5 \cdot 1 I_C = 0 \quad \text{eq ii}$$

$$-2 \cdot 2 I_A - 5 \cdot 1 I_B + 8 \cdot 3 I_C \quad \text{eq iii}$$

$$\begin{cases} I_A = 10 \text{ mA} \\ I_1 = 2.7 \text{ mA} \end{cases} \quad \begin{cases} I_B = 7.6 \text{ mA} \\ I_2 = 0.3 \text{ mA} \end{cases} \quad \begin{cases} I_C = 7.3 \text{ mA} \\ I_3 = 7.3 \text{ nA} \end{cases} \quad \begin{cases} I_x = 2.4 \text{ mA} \\ V_x = 7.3 \text{ V} \end{cases}$$


		Using Reference Node “d”	Using Reference Node “c”
I (mA)	Theoretical value =>	2.307	2.307
	MultiSIM value =>	2.308	2.308
V_a (Volts)	Theoretical value =>	15	7.387
	MultiSIM value =>	15	7.39
V_b (Volts)	Theoretical value =>	12.693	5.075
	MultiSIM value =>	12.693	5.075
V_c (Volts)	Theoretical value =>	7.617	0
	MultiSIM value =>	7.617	0
V_d (Volts)	Theoretical value =>	0	-7.613
	MultiSIM value =>	0	-7.62
V_{ab} (Volts)	Theoretical value =>	2.307	2.312
	MultiSIM value =>	2.308	2.308
V_{bc} (Volts)	Theoretical value =>	5.076	5.075
	MultiSIM value =>	5.076	5.077
V_{cd} (Volts)	Theoretical value =>	7.617	7.613
	MultiSIM value =>	7.62	7.615

Table 2.0: Theoretical and MultiSIM results of the Figure 2.0 circuits

		Nodal Analysis	Mesh Analysis
V_a (Volts)	Theoretical value =>	15	
	MultiSIM value =>	15	
V_b (Volts)	Theoretical value =>	22.43	
	MultiSIM value =>	12.9	
V_c (Volts)	Theoretical value =>	11.619	
	MultiSIM value =>	7.98	
I_A (mA)	Theoretical value =>		10
	MultiSIM derived =>		10
I_B (mA)	Theoretical value =>		7.6
	MultiSIM derived =>		7.6
I_C (mA)	Theoretical value =>		7.3
	MultiSIM derived =>		7.3
I_X (mA)	Theoretical value =>	6.796	2.4
	MultiSIM value =>	6.8	2.6
V_X (Volts)	Theoretical value =>	3.381	7.3
	MultiSIM value =>	7.09	7.39

I₁ (mA)	Theoretical value =>		2.7
	MultiSIM value =>		2.61
I₂ (mA)	Theoretical value =>		0.3
	MultiSIM value =>		0.21
I₃ (mA)	Theoretical value =>		7.3
	MultiSIM value =>		7.39



