

# Multi-Stage Amplifiers


Amplifiers typically consist of more than one amplification stage (transistor).

The reason is, almost always, to offer a large (enough) input resistance, and a small (enough) output resistance, while a large (enough) voltage gain is ensured. This lecture provides illustrative examples for presenting the methodology for analyzing multi-stage amplifiers.
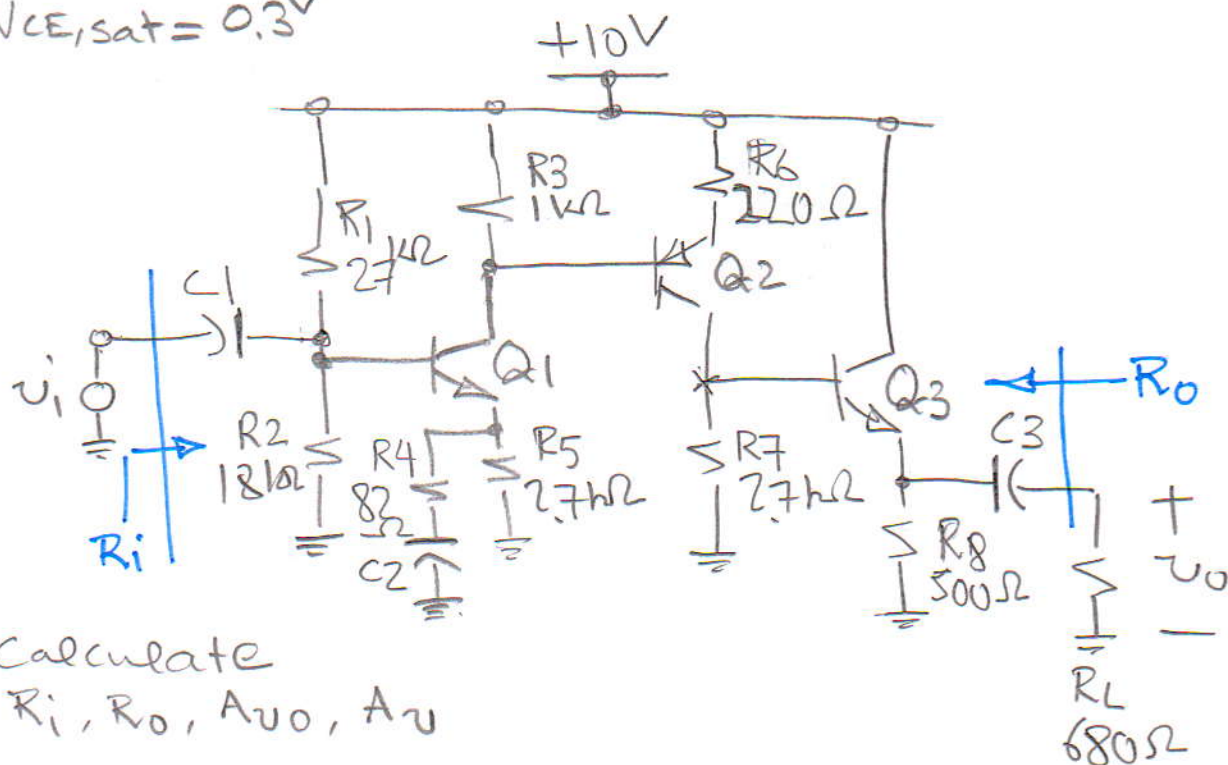
## Example #1

Analyze the following amplifier


$\beta_1 = \beta_2 = \beta_3 = 100$ ;  $V_{A1} = V_{A2} = V_{A3} = \infty$ ;  $V_{BE, on} = 0.7V$  for all.  
 $V_{CE, sat} = 0.3V$



Calculate

$R_i, R_o, A_{v0}, A_v$

## DC analysis

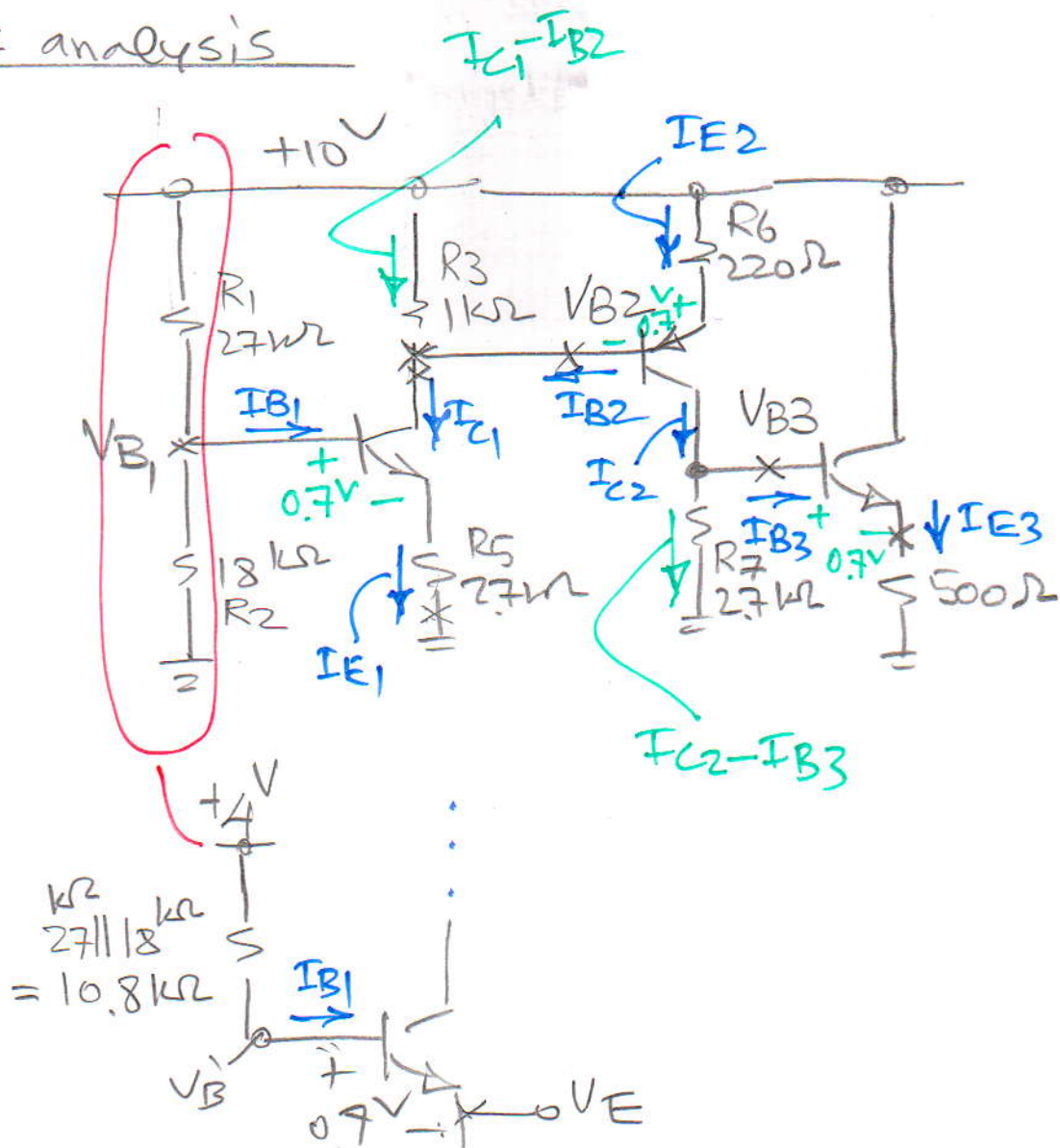

$$\text{KVL } 18 + 4 - 10.8 I_{B1} - 0.7 - 2.7 I_{E1} = 0$$

$$I_B = \frac{1}{\beta} I_C, \quad I_E = \frac{\beta + 1}{\beta} I_C$$

$$I_{L1} = \frac{(4 - 0.7) \times 100}{10.8 + (100 + 1) 2.7} = 1.164 \text{ mA}$$




$$I_{E1} = \frac{10}{100} \times 1.164 = 1.175 \text{ mA}$$

$$V_E = 2.7 \times 1.175 = 3.17 \text{ V}$$

$$V_{B_1} = V_E + 0.7 = 3.87V$$

# DC analysis (cont.)

3/

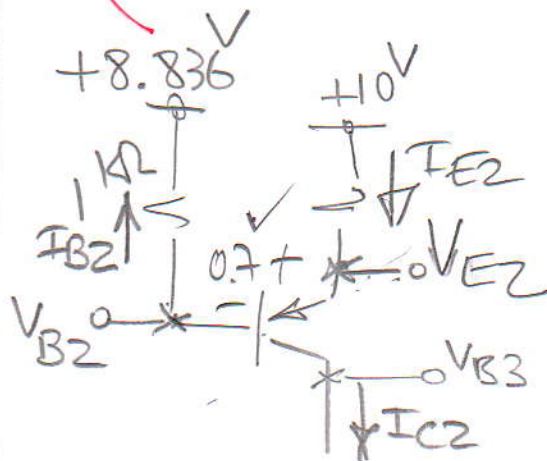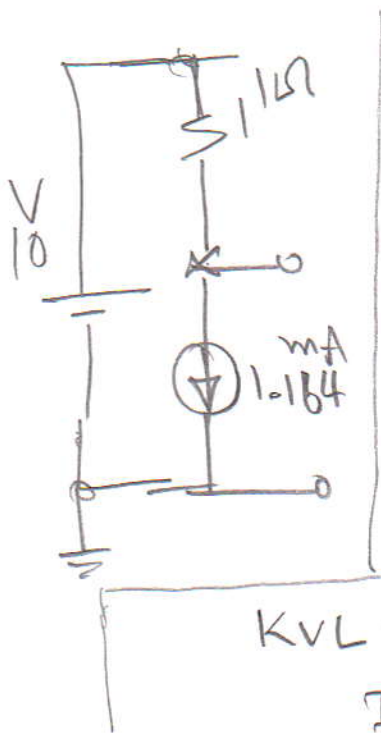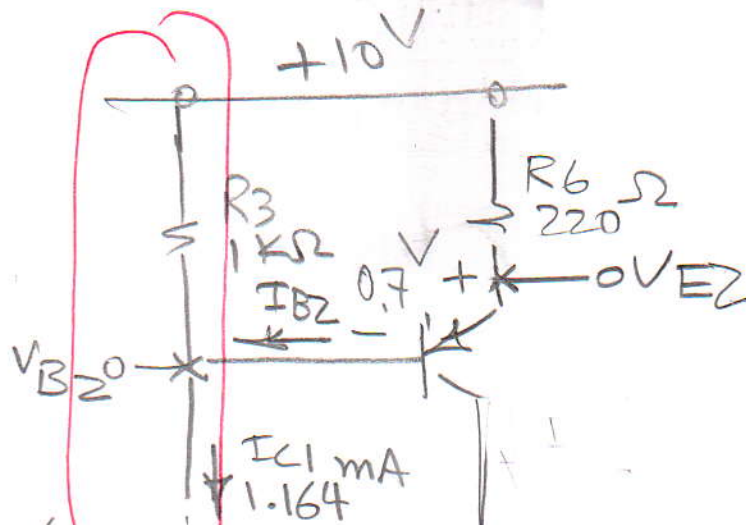

$$\text{KVL: } 8.836 + I_{B2} \times 1 \text{ k}\Omega + 0.7 \text{ V} + 0.22 I_{E2} = 10 \text{ V}$$

$$I_{B2} = \frac{1}{\beta} I_{C2}; \quad I_{E2} = \frac{\beta + 1}{\beta} I_{C2}$$

$$\Rightarrow I_{C2} = \frac{(10 - 0.7 - 8.836) \times 100}{1 + (100 + 1) \times 0.22} \text{ mA} = 1.998 \text{ mA} \approx 2.0 \text{ mA}$$

$$I_{E2} = \frac{100}{100} \times 2.0 = 2.02 \text{ mA}$$



$$V_{E2} = 10 - 0.22 \times 2.02 = 9.56 \text{ V}$$

$$V_{B2} = V_{E2} - 0.7 = 8.86 \text{ V}$$



# DC analysis

4/

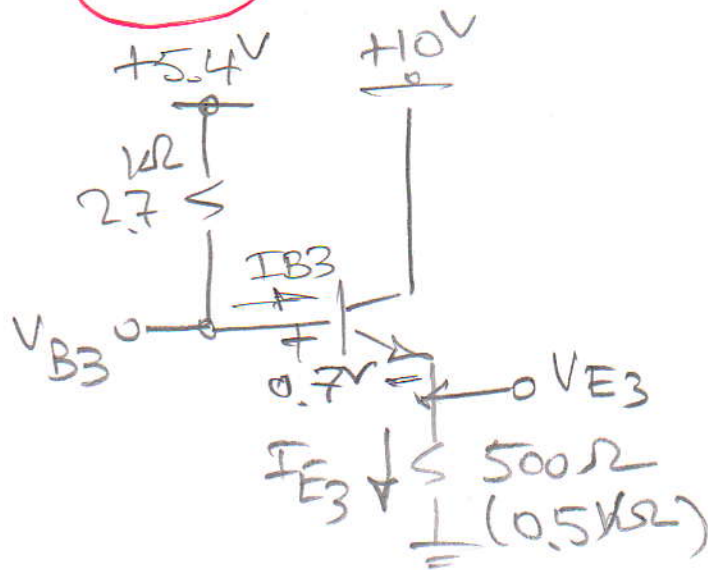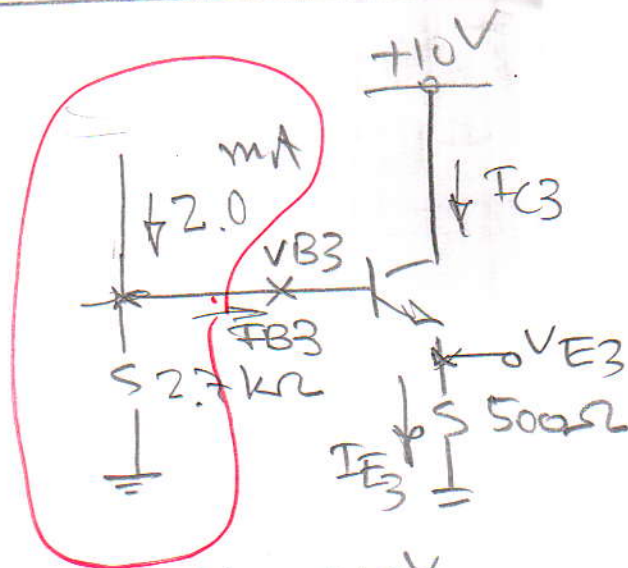

$$KVL: 5.4 - 2.7 \times I_{B3} - 0.7 - 0.5 I_{E3} = 0$$

$$I_{B3} = \frac{1}{\beta} I_{C3} ; I_{E3} = \frac{\beta + 1}{\beta} I_{C3}$$

$$I_{C3} = \frac{(5.4 - 0.7) \times 100}{2.7 + 0.5 \times (100 + 1)} = 8.83 \text{ mA}$$

$$I_{E3} = \frac{101}{100} \times 8.83 = 8.92 \text{ mA}$$

$$V_{E3} = 8.92 \times 0.5 = 4.46 \text{ V}$$


$$V_{B3} = 4.46 + 0.7 = 5.16 \text{ V}$$

$$V_{CE1} = V_{B2} - V_{E1} = 8.86 - 3.17 > 0.3 \checkmark$$

$$V_{CE2} = V_{E2} - V_{B3} = 9.55 - 5.16 > 0.3 \checkmark$$

$$V_{CE3} = V_{C3} - V_{E3} = 10 - 4.46 > 0.3 \checkmark$$

All Three transistors are  
in the active mode.

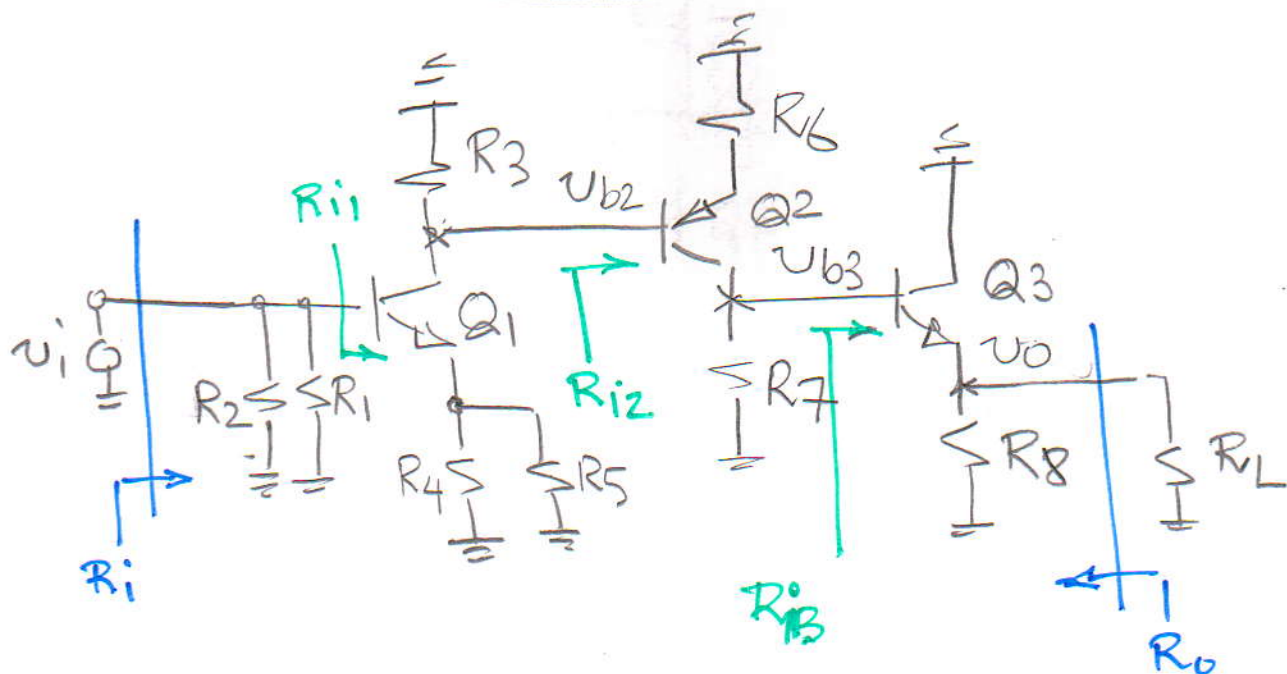ac analysis

$$R_{i3} = r_{\pi 3} + (\beta + 1)(R_8 \parallel R_L)$$

$$R_{i2} = r_{\pi 2} + (\beta + 1)R_6$$

$$R_{i1} = r_{\pi 1} + (\beta + 1)(R_4 \parallel R_5)$$

$$R_i = R_{i1} \parallel R_1 \parallel R_2$$

$$\frac{v_{b2}}{v_i} = \frac{-g_{m1}(R_3 \parallel R_{i2})}{1 + g_{m1}(R_4 \parallel R_5)}$$

$$\frac{v_{b3}}{v_{b2}} = \frac{-g_{m2}(R_7 \parallel R_{i3})}{1 + g_{m2}R_6}$$

$$\frac{v_o}{v_{b3}} = \frac{g_{m3}(R_8 \parallel R_L)}{1 + g_{m3}(R_8 \parallel R_L)}$$

$$A_v = \frac{v_o}{v_i} = \frac{v_o}{v_{b3}} \times \frac{v_{b3}}{v_{b2}} \times \frac{v_{b2}}{v_i}$$



$$A_{v0} = A_v \big|_{R_L \rightarrow \infty}$$

## ac analysis (cont.)

7/

Calculation of  $R_o$ :

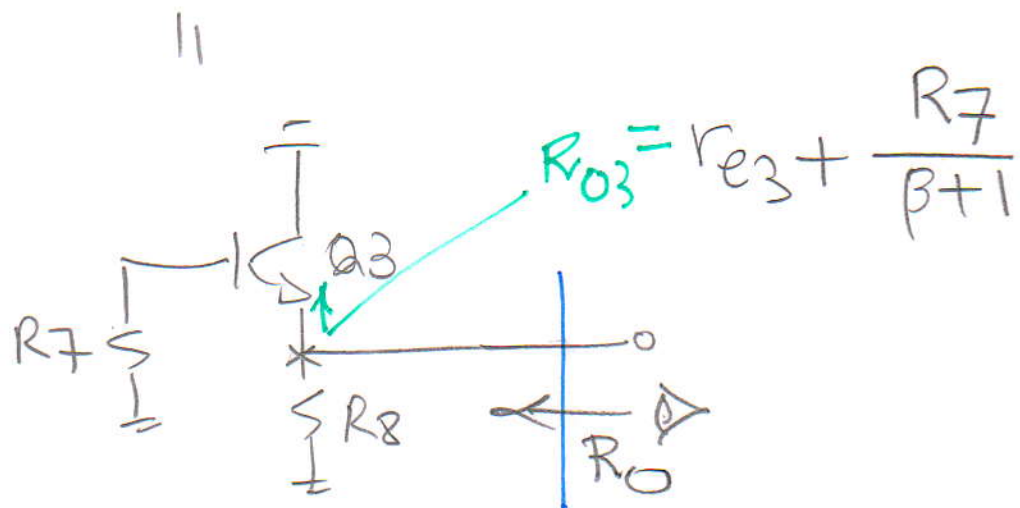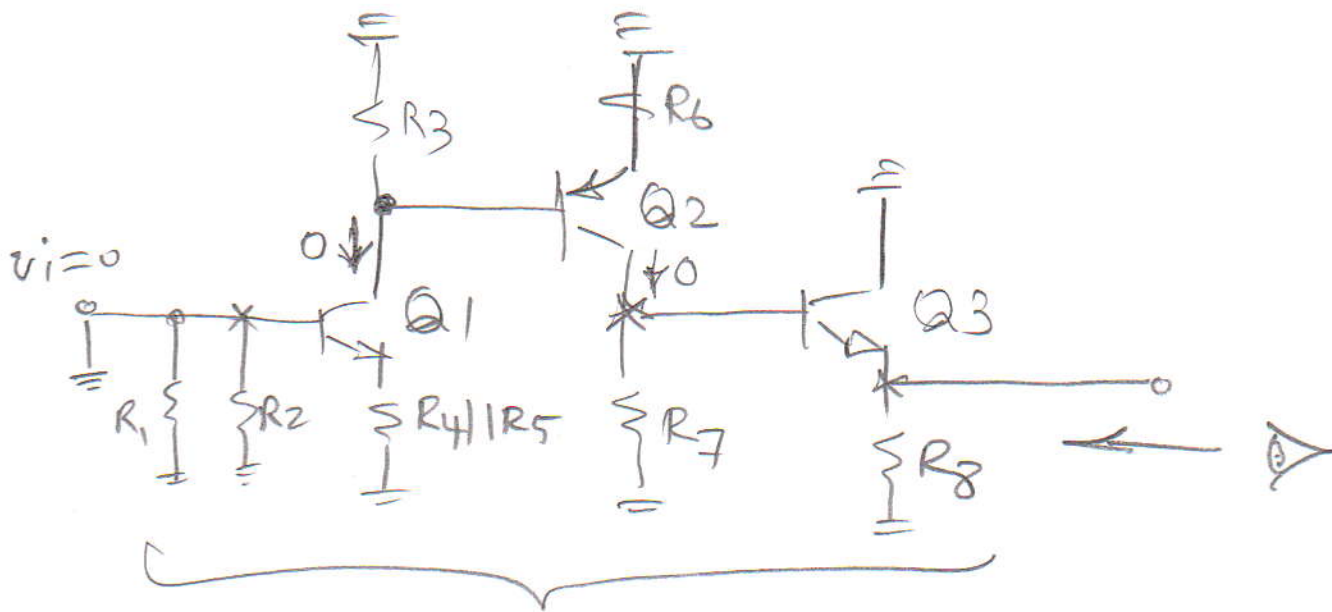$v_i = 0 \Rightarrow$  resistance seen when one looks into the amp. from the output terminal.



$$\begin{aligned} R_o &= R_8 \parallel R_{o3} \\ &= R_8 \parallel \left[ r_{e3} + \frac{R_7}{\beta + 1} \right] \end{aligned}$$



## Numerical Calculations

8/

$$g_{m1} = 40 \times 1.164 = 46.56 \text{ mS'}$$

$$r_{\pi 1} = \frac{\beta}{g_{m1}} = \frac{100}{46.56} = 2.15 \text{ k}\Omega \Rightarrow r_{e1} = \frac{r_{\pi 1}}{\beta + 1} \text{ k}\Omega = 0.021$$

$$g_{m2} = 40 \times 2.0 = 80 \text{ mS'}$$

$$r_{\pi 2} = \frac{\beta}{g_{m2}} = \frac{100}{80} = 1.25 \text{ k}\Omega \Rightarrow r_{e2} = \frac{1.25}{101} = 0.012 \text{ k}\Omega$$

$$g_{m3} = 40 \times 8.83 = 353.2 \text{ mS'}$$

$$r_{\pi 3} = \frac{100}{353.2} = 0.283 \text{ k}\Omega \Rightarrow r_{e3} = 0.0028 \text{ k}\Omega$$

$$R_{i1} = r_{\pi 1} + (\beta + 1)(R_4 \parallel R_5) \\ = 2.15 + 101 \times (0.082 \parallel 2.7) = 10.18 \text{ k}\Omega$$

$$R_{i2} = r_{\pi 2} + (\beta + 1)R_6 \\ = 1.25 + 101 \times 0.22 = 23.47 \text{ k}\Omega$$

$$R_{i3} = r_{\pi 3} + (\beta + 1)(R_8 \parallel R_L) = 0.283 + 101 \times (0.5 \parallel 0.68) \text{ k}\Omega \text{ k}\Omega \\ 0.288 = 29.38 \text{ k}\Omega$$

$$\frac{v_{b2}}{v_i} = \frac{-46.56 \times (1 \parallel 23.47) \text{ k}\Omega \text{ k}\Omega}{1 + 46.56 \times (0.082 \parallel 2.7) \text{ k}\Omega} \approx -9.54 \frac{\text{V}}{\text{V}}$$

0.079



$$\frac{v_{b3}}{v_i} = \frac{-80 \times \overbrace{(2.7 \parallel 29.38)}^{2.47 \text{ k}\Omega}}{1 + 80 \times 0.22} = -10.63 \frac{\text{V}}{\text{V}}$$

$$\left. \frac{v_o}{v_{b3}} \right|_{R_L = \infty} = \frac{353.2 \times \overbrace{(0.5 \parallel \infty)}^{\infty}}{1 + 353.2 \times (0.5 \text{ k}\Omega \parallel \infty)} = 0.994 \frac{\text{V}}{\text{V}}$$

$$\left. \frac{v_o}{v_{b3}} \right|_{R_L = 0.68 \text{ k}\Omega} = \frac{353.2 \times \overbrace{(0.5 \parallel 0.68)}^{0.288}}{1 + 353.2 \times (0.5 \parallel 0.68)} = 0.990 \frac{\text{V}}{\text{V}}$$


$$\begin{aligned} A_{v_o} &= (-9.54) \times (-10.63) \times 0.994 \approx 100.8 \frac{\text{V}}{\text{V}} \\ A_v &= (-9.54) \times (-10.63) \times 0.990 = 100.4 \frac{\text{V}}{\text{V}} \end{aligned} \left. \vphantom{\begin{aligned} A_{v_o} \\ A_v \end{aligned}} \right\} \begin{array}{l} \text{practically} \\ \text{the} \\ \text{same!} \end{array}$$

$$R_o = \left\{ 0.5 \text{ k}\Omega \parallel \underbrace{\left[ 0.0028 + \frac{2.7}{101} \right]}_{0.0295} \right\} \approx 0.028 \text{ k}\Omega \text{ or } \underline{28 \Omega}$$

That is why the amplifier does not care when the  $680\text{-}\Omega$  load is connected to it!

## Example #2: A BiCMOS OP-AMP

10/

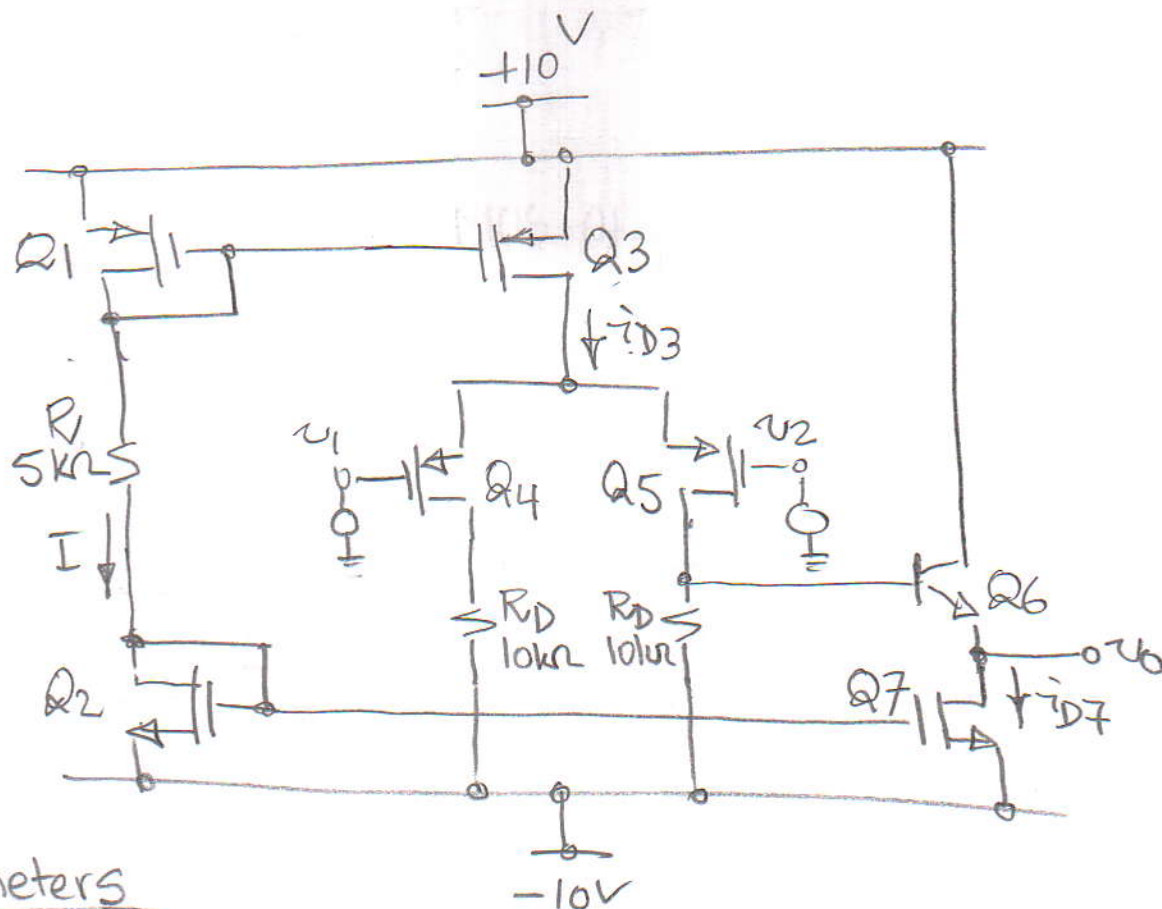

### Parameters

$$k'_n = 2k'_p = 0.2 \text{ mA/V}^2; V_{tn} = 0.8 \text{ V}; V_{tp} = -1.0 \text{ V}$$


$$\left(\frac{W}{L}\right)_{1,2,4,5} = 10; V_{An} = |V_{Ap}| = V_{Ag} = \infty$$

$$\beta = 50; V_{BE, \text{on}} = 0.7 \text{ V}; V_{CE, \text{sat}} = 0.3 \text{ V}$$

- Determine  $\left(\frac{W}{L}\right)_3$  and  $\left(\frac{W}{L}\right)_7$  for  $I_{D3} = 2.2 \text{ mA}$  and  $I_{D7} = 1.5 \text{ mA}$ .
- Determine all node voltages and branch currents for  $v_1 = v_2 = 0$ .
- Determine the Common-Mode input voltage range.
- Determine the differential-mode gain  $A_d = v_0 / (v_1 - v_2)$ .
- Repeat if  $V_{An} = 40 \text{ V}$ ;  $V_{Ap} = -20 \text{ V}$ ; and  $V_A = 80 \text{ V}$ .

# DC Analysis

11/

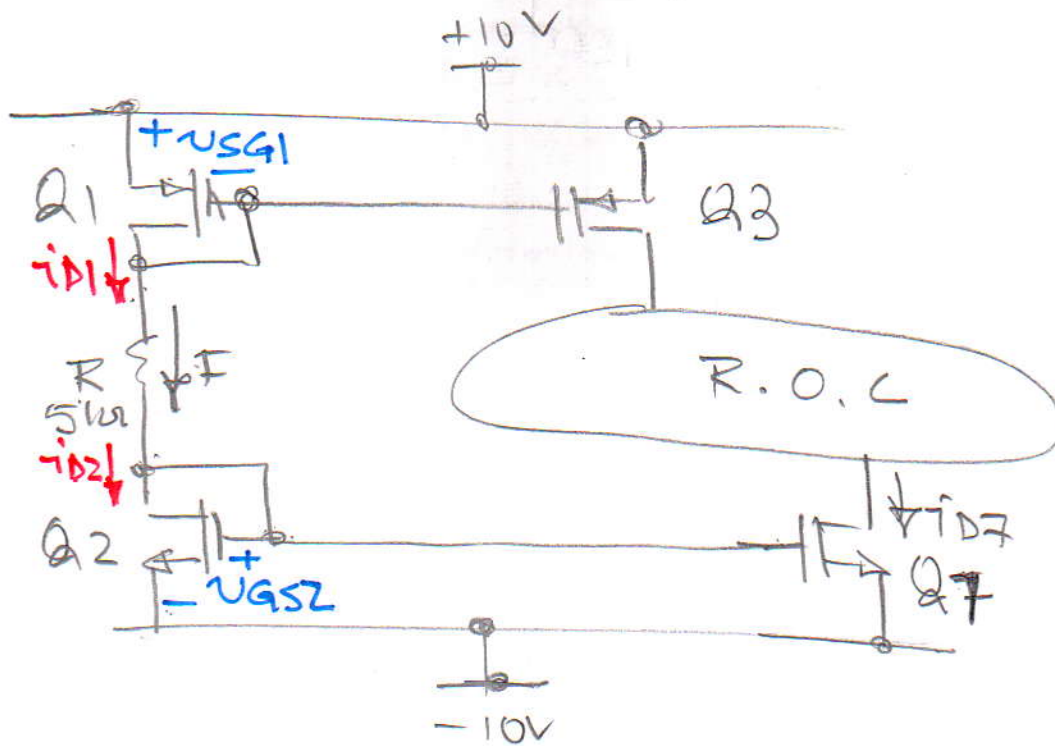

First task: to calc.  $I$ .  $(\frac{W}{L})_1$

$$i_{D1} = \frac{1}{2} K_1 V_{OV1}^2 = \frac{1}{2} \times 0.1 \times 10 \times V_{OV1}^2 = 0.5 V_{OV1}^2$$

$$\Rightarrow I = 0.5 V_{OV1}^2 \Rightarrow \boxed{V_{OV1} = \sqrt{2I}} \quad (1)$$

$$i_{D2} = \frac{1}{2} K_2 V_{OV2}^2 = \frac{1}{2} \times 0.2 \times 10 \times V_{OV2}^2 = V_{OV2}^2$$

$$\Rightarrow \boxed{V_{OV2} = \sqrt{I}} \quad (2) \quad (\frac{W}{L})_2$$

$$\text{KVL: } 10 - V_{SG1} - RI - V_{GS2} = -10V$$

$$10 - (V_{OV1} + |V_{tp}|) - 5I - (V_{OV2} + |V_{tn}|) = -10$$

$$\boxed{I = 3.64 - 0.2(V_{OV1} + V_{OV2})} \quad (3)$$



12/

So let us resort to iterations to solve:

$$\begin{aligned}
 V_{OV1} = V_{OV2} = 0 &\xrightarrow{(3)} I = 3.64 \text{ mA} \\
 I = 3.64 \text{ mA} &\xrightarrow{(1) \& (2)} V_{OV1} \approx 2.7 \text{ V} \& V_{OV2} \approx 1.9 \text{ V} \\
 V_{OV1} = 2.7 \text{ V} \& V_{OV2} = 1.9 \text{ V} &\xrightarrow{(3)} I = 2.72 \text{ mA} \\
 I = 2.72 \text{ mA} &\xrightarrow{(1) \& (2)} V_{OV1} \approx 2.33 \text{ V} \& V_{OV2} \approx 1.65 \text{ V} \\
 V_{OV1} \approx 2.33 \text{ V} \& V_{OV2} \approx 1.65 \text{ V} &\xrightarrow{(3)} I = \cancel{2.84} 2.84 \text{ mA} \\
 I = 2.84 \text{ mA} &\xrightarrow{(1) \& (2)} V_{OV1} \approx 2.38 \text{ V} \& V_{OV2} \approx 1.69 \text{ V} \\
 V_{OV1} = 2.38 \text{ V} \& V_{OV2} = 1.69 \text{ V} &\xrightarrow{(3)} I = 2.83 \text{ mA} \\
 I = 2.83 \text{ mA} &\xrightarrow{(1) \& (2)} V_{OV1} \approx 2.38 \text{ V} \& V_{OV2} \approx 1.68 \text{ V}
 \end{aligned}$$

Values are repeating wrt the previous iteration. Stop it!

$$I \approx 2.83 \text{ mA} ; V_{OV1} \approx 2.38 \text{ V} ; V_{OV2} \approx 1.68 \text{ V}$$


$$V_{SG1} = 2.38 + |-1.0| = 3.38 \text{ V}$$

$$V_{GS2} = 1.68 + 0.8 = 2.48 \text{ V}$$

$$\begin{aligned}
 \frac{i_{D3}}{i_{D1}} &= \frac{(\frac{W}{L})_3}{(\frac{W}{L})_1} \Rightarrow \frac{2.2}{2.83} = \frac{(\frac{W}{L})_3}{10} \Rightarrow \boxed{(\frac{W}{L})_3 = 7.77} \\
 \frac{i_{D7}}{i_{D2}} &= \frac{(\frac{W}{L})_7}{(\frac{W}{L})_2} \Rightarrow \frac{4.5}{2.83} = \frac{(\frac{W}{L})_7}{10} \Rightarrow \boxed{(\frac{W}{L})_7 = 5.3}
 \end{aligned}$$




13/

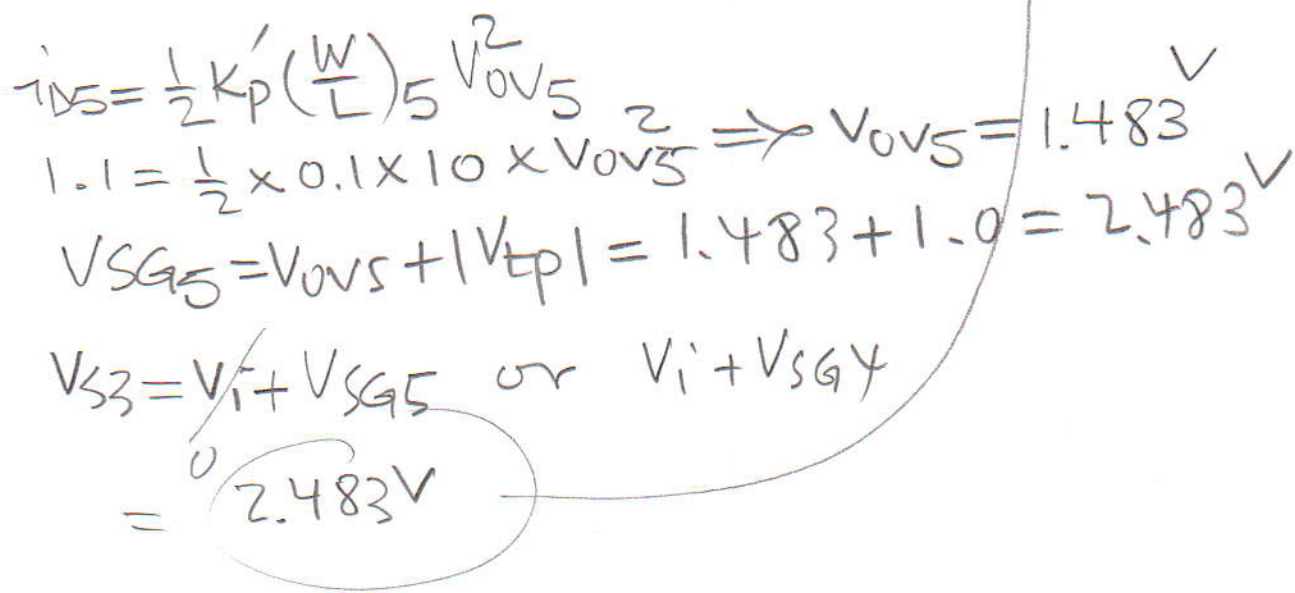

$$i_{DS} = \frac{1}{2} K_P' \left( \frac{W}{L} \right)_5 V_{OV5}^2$$
$$1.1 = \frac{1}{2} \times 0.1 \times 10 \times V_{OV5}^2 \Rightarrow V_{OV5} = 1.483 \text{ V}$$
$$V_{SG5} = V_{OV5} + |V_{tp}| = 1.483 + 1.0 = 2.483 \text{ V}$$
$$V_{S3} = V_i + V_{SG5} \text{ or } V_i + V_{SG4}$$
$$= 0 + 2.483 \text{ V}$$

# C) Common-Mode Range

14

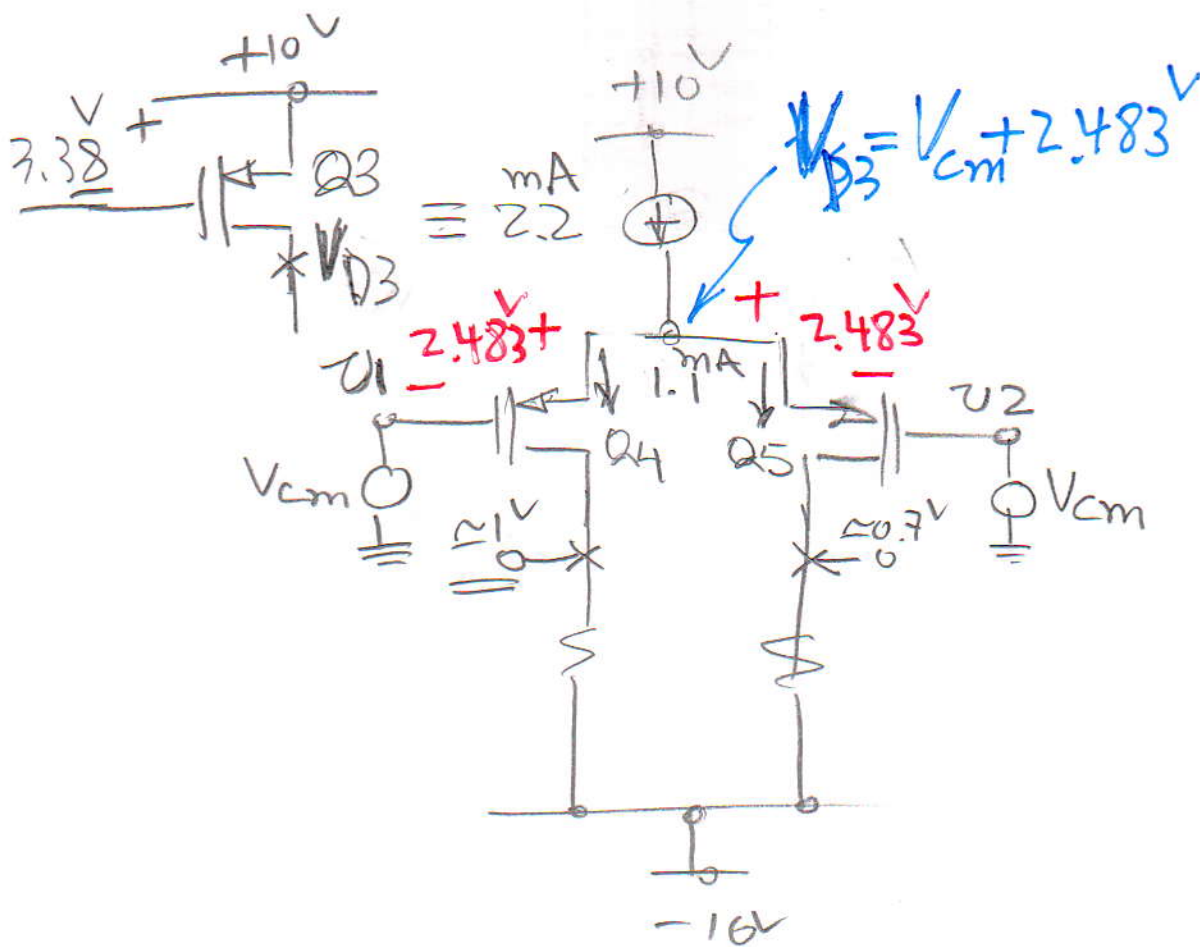

Find range of  $V_{cm}$  over which no transistor goes into the triode mode.

For  $Q_3$  to remain in sat. mode:

$$V_{SD3} > V_{SG3} - |V_{tp}|$$

$$10 - V_{D3} \geq 7.38 - |-1.0|$$

$$10 - (V_{cm} + 2.483) \geq 2.38$$

$$\Rightarrow \boxed{V_{cm} \leq 5.137V}$$

c (cont.)

15/

For Q4 & Q5 to be in sat.  
mode:

$$V_{SD4} \geq V_{SG4} - |V_{tp}|$$

$$V_{S4} - 1.0^V \geq 2.483 - |-1.0|$$

$\Downarrow$

$$V_{D3} - 1.0 \geq 2.483$$

$\Downarrow$

$$V_{cm} + 2.483 \geq 2.483$$



$$\Rightarrow \boxed{V_{cm} \geq 0}$$

Overall,

$$\boxed{0 \leq V_{cm} \leq 5.137^V}$$

# d) Differential Gain. ac analysis

16/

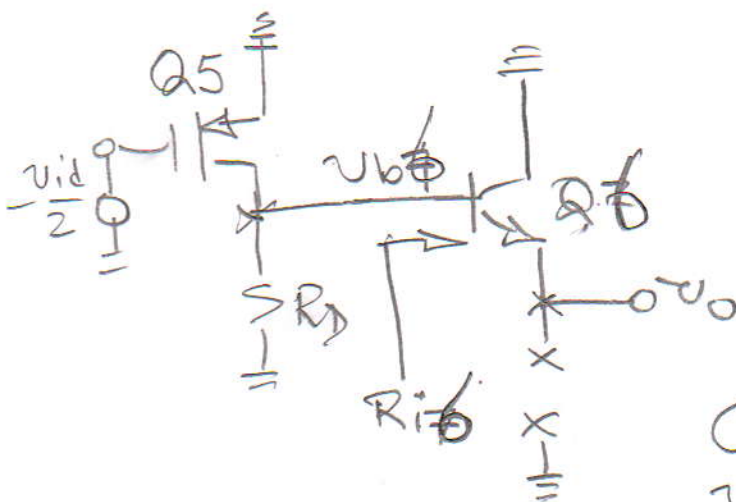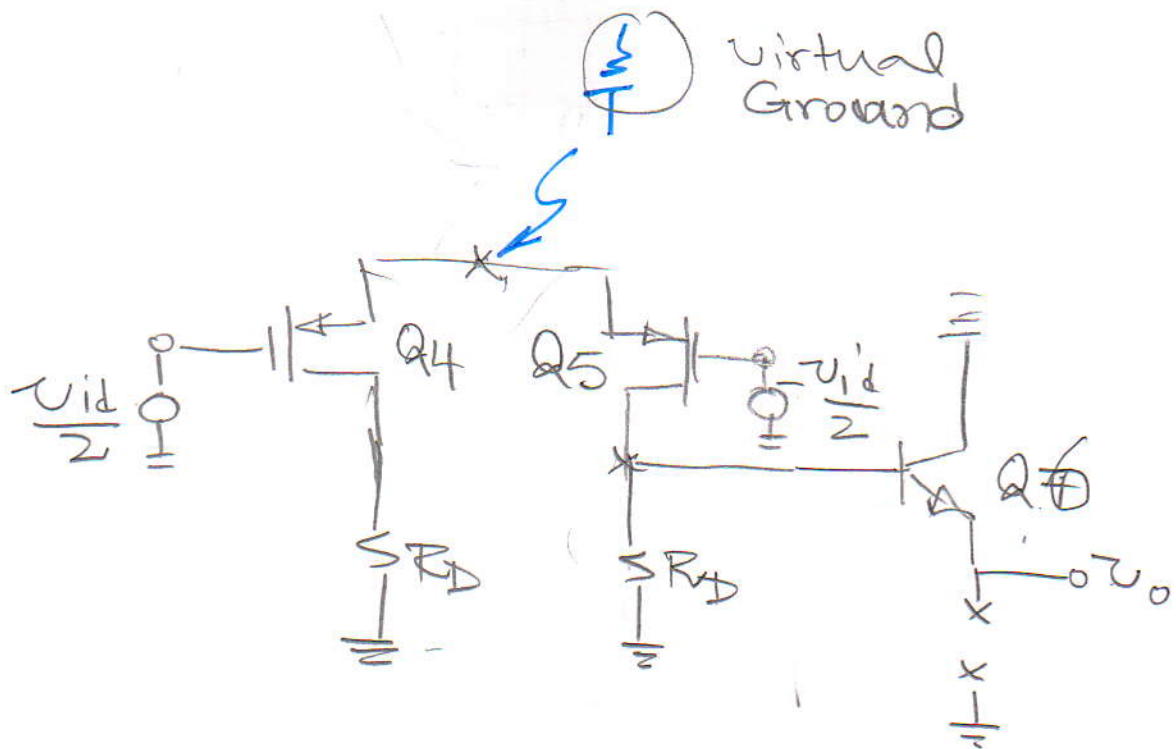

$$R_{i7} = r_{\pi 7} + (\beta + 1) \infty = \infty$$

CS:

$$\frac{v_{b7}}{-\frac{v_{id}}{2}} = -g_{m5}(R_D \parallel \underbrace{R_{i7}}_{\infty})$$



$$= -g_{m5} R_D$$

$$\Rightarrow \boxed{\frac{v_{b7}}{v_{id}} = \frac{1}{2} g_{m5} R_D}$$

$$\Leftarrow \left( \frac{v_o}{v_{b7}} = \frac{g_{m7} R_E}{1 + g_{m7} R_E} = 1 \right) \quad \left| \quad \frac{v_o}{v_{id}} = \frac{v_o}{v_{b7}} \times \frac{v_{b7}}{v_{id}} = \frac{1}{2} g_{m5} R_D \right.$$



e) With Early effect considered 17

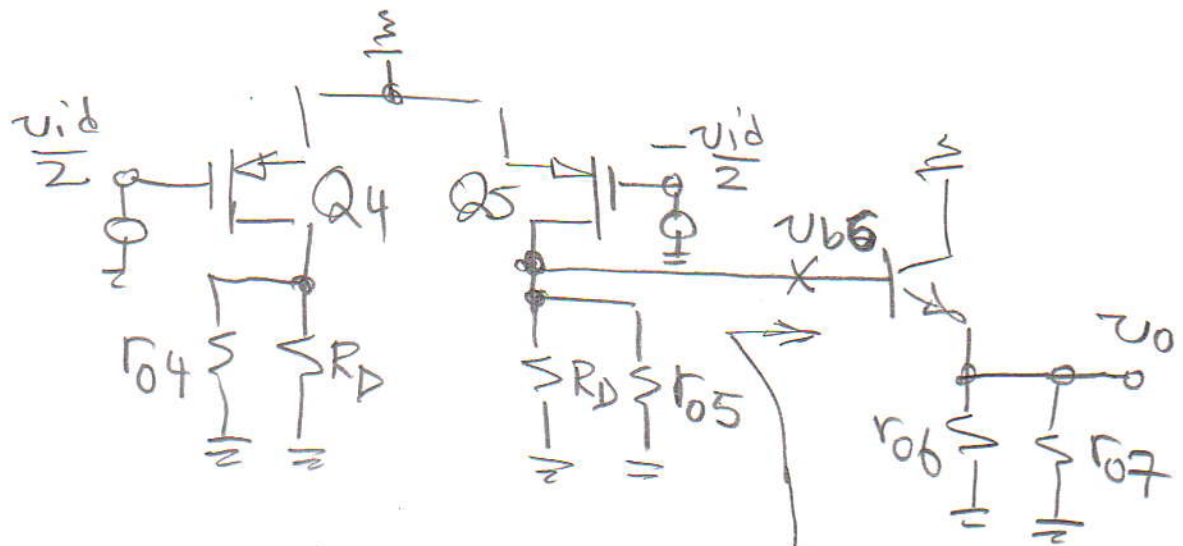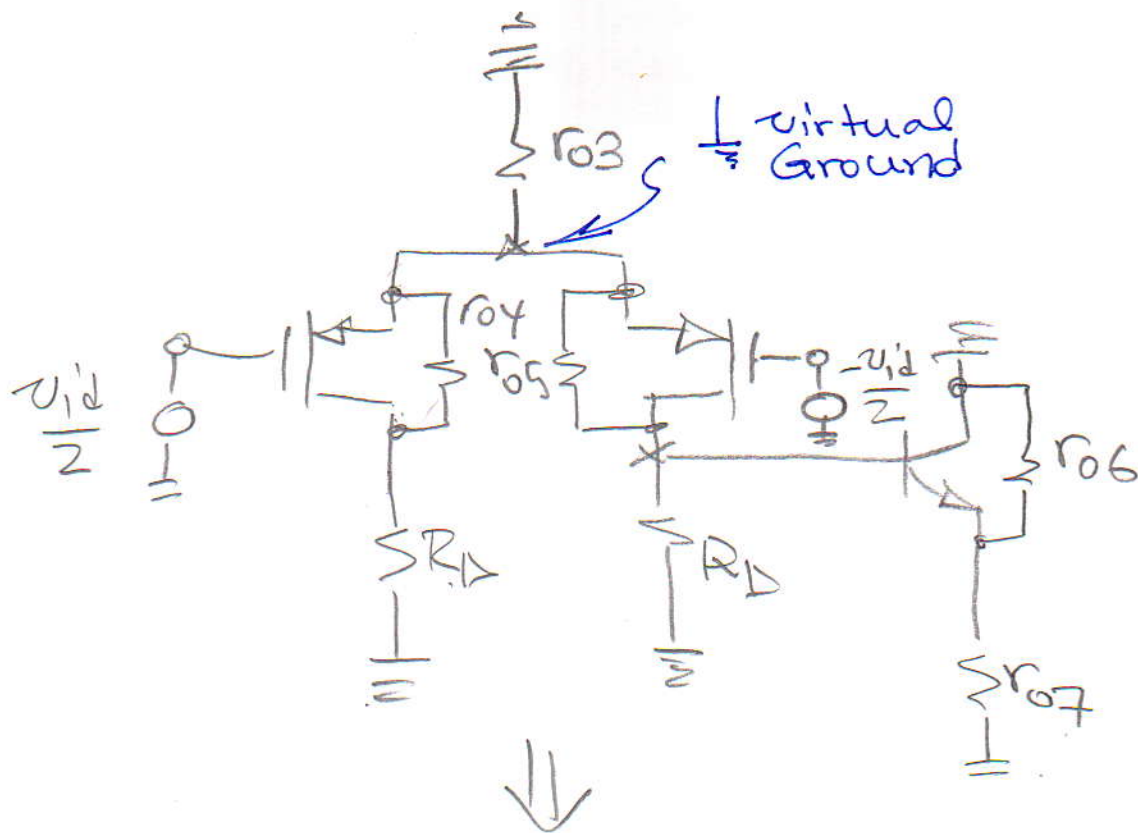

$$R_{i6} = r_{\pi 6} + (\beta + 1)(r_{o6} \parallel r_{o7})$$

$$CS: \frac{v_{b6}}{(-\frac{v_{id}}{2})} = -g_{m5}(R_D \parallel r_{o5} \parallel R_{i6}) \Rightarrow \frac{v_{b6}}{v_{id}} = \frac{1}{2} g_{m5}(R_D \parallel r_{o5} \parallel R_{i6})$$

$$CC: \frac{v_o}{v_{b6}} = \frac{g_{m6}(r_{o6} \parallel r_{o7})}{1 + g_{m6}(r_{o6} \parallel r_{o7})}$$

$$\frac{v_o}{v_{id}} = \frac{v_o}{v_{b6}} \times \frac{v_{b6}}{v_{id}}$$