

B

ELCE Department, Ryerson University**MIDTERM TEST**

October 27, 2006

**NAME (Print):** Charles Gilmour**SECTION:** 14**Student Number:** 050497205**Read all questions carefully ! Use opposing pages for rough work**Round off final answers to 3 significant digits, attach proper units  
and copy all final answers to the indicated space**TIME AVAILABLE: 90 minutes****For marking use only (do not fill):**

Question 1 (Max. 8)	8
Question 2 (Max. 10)	10
Question 3 (Max. 5)	5
Question 4 (Max. 7)	7
<b>Total (out of 30):</b>	<b>30</b>


(1) Given three resistors

$$R_1 = 20 \, \Omega \text{ rated } 2.5 \, \text{W}$$

$$R_2 = 40 \, \Omega \text{ rated } 1.5 \, \text{W}$$

$$R_3 = 60 \, \Omega \text{ rated } 1.0 \, \text{W}$$

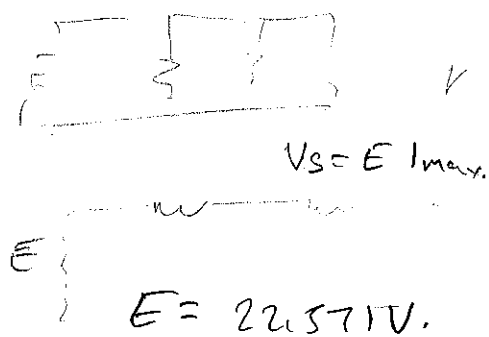after 7.071  
 $P_{\text{max}} \rightarrow 7.75$   
 $\rightarrow 7.75$   
 $E I_{\text{max}}$



(a) What is the largest voltage  $V_s$  that can be safely applied to the **series** combination of these three resistors?

(b) What is the largest current  $I_s$  that can be safely passed through the **series** combination of these three resistors?

(c) What is the largest voltage  $V_p$  that can be safely applied to the **parallel** combination of these three resistors?

(d) If resistor  $R_2$  dissipates 2.5 J of energy in 2 seconds, what is the voltage  $V_2$  applied across this resistor?

a)  $V_s = R_T I_{\text{max}}$   
 $= (120 \, \Omega) (0.129 \, \text{A})$   
 $[V_s = 15.48 \, \text{V}]$

b)  $I_{\text{max}_1} = \sqrt{\frac{2.5}{20}}$   
 $= 0.354 \, \text{A}$   
 $I_{\text{max}_2} = \sqrt{\frac{1.5}{40}}$   
 $= 0.194 \, \text{A}$

$I_{\text{max}_3} = \sqrt{\frac{1.0}{60}}$   
 $= 0.129 \, \text{A}$

c)  $V_{\text{max}_1} = \sqrt{2.5(20)}$   
 $= 7.071 \, \text{V}$   
 $V_{2 \text{ max}} = \sqrt{1.5(40)}$   
 $= 7.75$

$V_{3 \text{ max}} = \sqrt{1.0(60)}$   
 $= 7.75 \, \text{V}$

Attach proper units!  
 (2 points each)

$V_s = 15.48 \, \text{V}$

$I_s = 0.129 \, \text{A}$

$V_p = 7.071 \, \text{V}$

$V_2 = 7.071 \, \text{V}$

d)  $P = \frac{W}{t}$

$= \frac{7.5 \, \text{J}}{2 \, \text{s}}$

$P = 1.25 \, \text{W} = \frac{V^2}{R}$

$1.25 = \frac{V^2}{40}$


$[V = 7.071 \, \text{V}]$

B

← Evl results

(2) The voltage at node A is + 40 V (with respect to the ground). Analyze the following circuit and find the values indicated below (cross-check all your answers !)


$$I_3 = I_4 + I_5$$

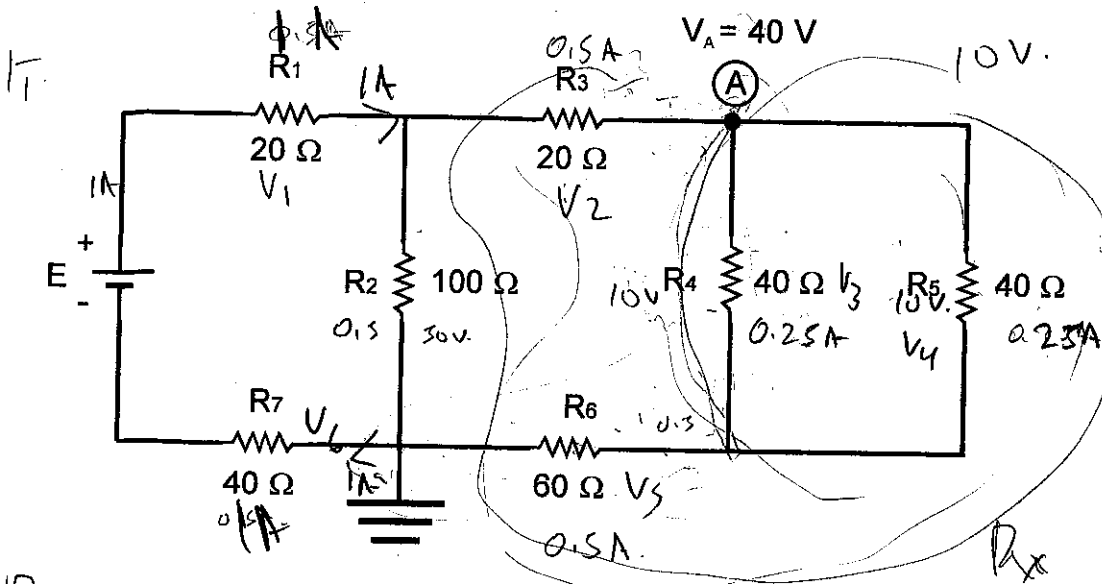

$$V_3 = V_4$$

$$I_3 = I_6$$

$$30V$$

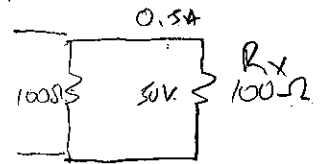

$$R_{456} = \frac{40 \cdot 40}{80}$$

$$V = R_{456} I_{456}$$

$$= 20\Omega + 60$$

$$I_{456} = \frac{40}{80}$$

$$R_{456} = 80\Omega$$

$$= 0.5A$$

$$V_{456} = 80(0.5)$$

$$= 10V$$

Attach proper units !

(1 point each)

$$V \text{ drop across } R_1 = 20V$$

$$\text{Current through } R_3 = 0.5A$$

$$V \text{ drop across } R_2 = 50V$$

$$\text{Current through } R_6 = 0.5A$$

$$E = 110V$$

$$\text{Power in } R_4 = 2.5W$$

$$\text{Total power delivered by } E = 110W$$

$$\text{Current through } R_5 = 0.25A$$

$$V \text{ drop across } R_3 = 10V$$

$$\text{Total current delivered by } E = 1A$$

$$E = 20 + 50 + 40$$

$$= 110V$$

$$R_{2X} = \frac{100 \cdot 100}{200}$$

$$V_1 = 50V$$

$$V_{2X} = 50V (1)$$

$$[V_{1X} = 50V]$$

$$V_1 = R_1 I_T$$

$$= 20\Omega (1)$$

$$[V_1 = 20V]$$

$$I_X = I_T \frac{R_X}{R_2 + R_X}$$

$$0.5A = I_T \frac{100\Omega}{200\Omega}$$

$$[I_T = 1A]$$

$$V_2 = R_2 I_T$$

$$= 100 (0.5)$$

$$[V_2 = 50V]$$

$$40 (0.25)^2$$

$$P_{R_4} = 2.5W$$


$$R_7 = 40\Omega (1)$$

$$= 40V$$

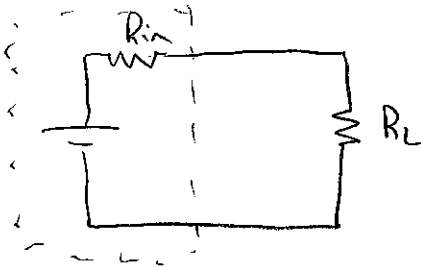(3) Real power supply delivers 4 W of power into a load  $R_L = 30 \Omega$  with 60% efficiency.

Draw the circuit diagram and find:

- The terminal voltage  $V_{AB}$  when no load is connected ( $R_L = \infty$ )
- The current through  $R_L$  when  $R_L = 0$  (short circuit)
- The internal resistance  $R_i$
- The power that would be delivered into a  $10 \Omega$  load.



$$\eta = \frac{R_L}{R_i + R_L}$$

$$0.6 = \frac{30}{R_i + 30}$$

$$[R_i = 20 \Omega]$$

$$V_{sc} = E$$

$$V = E - R_i I$$

$$10.95 = E - 20(0.365)$$

$$[E = 18.25 \text{ V}]$$

$$\therefore V_{oc} = E = 18.75 \text{ V}$$

$$I_{sc} = \frac{E}{R_i}$$

$$= \frac{18.25 \text{ V}}{20 \Omega}$$

$$[I_{sc} = 0.913 \text{ A}]$$

$$P_L = \frac{V^2}{R_L}$$

$$4(30) = V^2$$

$$[V = 10.95 \text{ V}]$$

$$P_L = \left( \frac{E}{R_i + R_L} \right)^2 R_L$$

$$= \left( \frac{18.25 \text{ V}}{20 + 10} \right)^2 \times 10$$

$$[P = 3.70 \text{ W}]$$

$$V = R_L I$$

$$\frac{10.95}{30} = I$$

$$[I = 0.365 \text{ A}]$$

Attach proper units !

(a)  $V_{AB} = 18.75 \text{ V}$  (2 points)


(b)  $I = 0.913 \text{ A}$  (1 point)

(c)  $R_i = 20 \Omega$  (1 point)

(d)  $P = 3.70 \text{ W}$  (1 point)

B

(4)

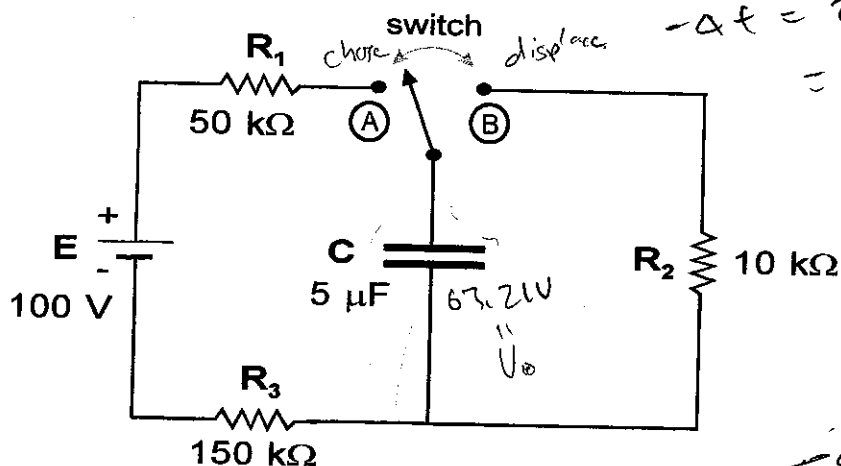

- for 1 sec charge C

$$-\Delta t = 2 - 1 = 1 \text{ sec.}$$

allow to discharge for 1s

In the capacitor circuit above, the switch has been in position B for a long time. At time  $t = 0$ , the switch is placed in position A, and at time  $t = 1$  sec the switch is placed back in position B where it remains. Find the values of the quantities indicated below:

- The current  $i_3$  through resistor  $R_3$  at time  $t = 0^+$
- The voltage across C at  $t = 1$  sec
- The current  $i_2$  through resistor  $R_2$  at time  $t = 2$  sec
- The voltage across C at time  $t = 2$  sec

$$\tau = \frac{R}{C} = \frac{200 \text{ k}\Omega}{5 \mu\text{F}}$$

$$= 1 \text{ s}$$

$$\tau_d = R C = 10 \text{ k}\Omega \cdot 5 \mu\text{F} = 0.05 \text{ s}$$

$$a) i_c(0^+) = I_0$$

$$I_0 = \text{total current}$$

$$= \frac{E}{R_T} = \frac{100 \text{ V}}{200 \text{ k}\Omega}$$

$$[I_0 = 0.0005 \text{ A}]$$

$$b) V_c(1) = V_f (1 - e^{-t/\tau})$$

$$V_0 = 0$$

$$V_f = E$$

$$= 100 \text{ V} (1 - e^{-1/1})$$

$$[V_c(1) = 63.21 \text{ V}] = V_0$$

$$c) i_c(2) = I_0 e^{-t/\tau}$$

$$= (0.00032 \text{ A}) e^{-2}$$

$$= 6.59 \times 10^{-13} \text{ A}$$

$\therefore$  after 1s the is 63.21V of charge on C.

$\rightarrow V_f = 0$  all the neutral

$$d) V_c(2) = V_0 e^{-t/\tau_d} = (63.21 \text{ V}) e^{-1/0.05} = 1.3 \times 10^{-7} \text{ V}$$

Attach proper units!

$$(a) i_3(0^+) = 0.0005 \text{ A} \quad (2 \text{ points})$$

$$(b) v_c(1) = 63.21 \text{ V} \quad (2 \text{ points})$$

$$(c) i_2(2) = 6.59 \times 10^{-13} \text{ A} \quad (2 \text{ points})$$

$$(d) v_c(2) = 1.3 \times 10^{-7} \text{ V} \quad (1 \text{ point})$$