

Ryerson University
Department of Electrical and Computer Engineering
ELE202: Electric Circuits Analysis
Mid-Term Examination, March 2, 2012

Duration: 2 hours

Student's Name: [REDACTED]

Student's Number: [REDACTED] Section: [REDACTED]


NOTES:

1. This is a **Closed Book** examination. No aids other than the approved calculators are allowed.
2. There are four questions. Answer all **four questions**.
3. You must **show all working**. Answers without working will receive zero marks.
4. **No questions are to be asked** in the examination hall. If doubt exists as to the interpretation of any question, the student is urged to submit with the answer paper, a clear statement of any assumptions made.


<i>Question No.</i>	<i>Mark of each question</i>	<i>Mark obtained</i>
Q1	25	15
Q2	25	23.5
Q3	25	23
Q4	25	20
Total (Out of 100):		83

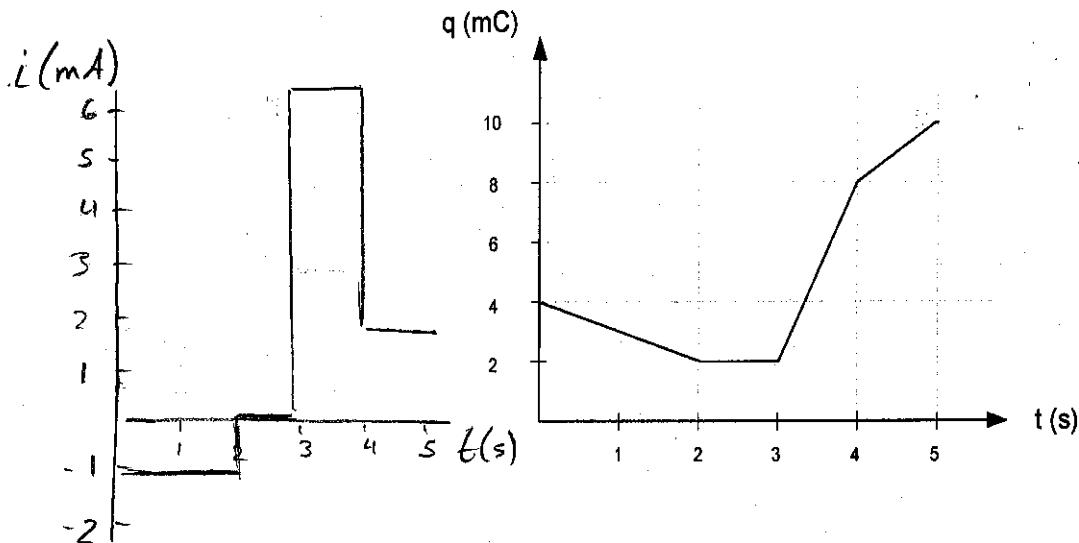Question 1(i):

The following figures show the charge entering; and voltage across a certain element:



$$i = \frac{dq}{dt}$$

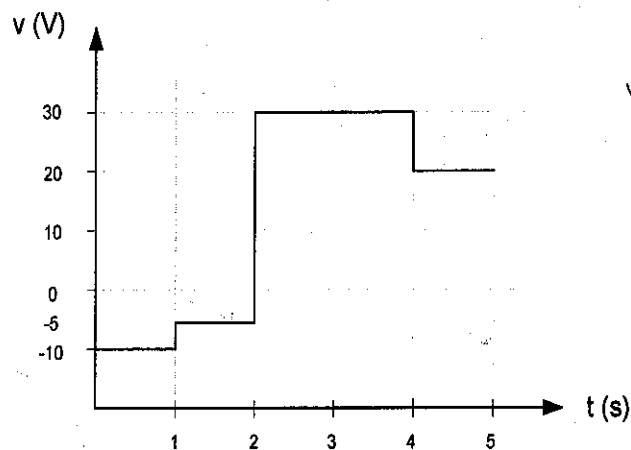

$$v = \frac{dw}{dq}$$

$$p = \frac{dw}{dt}$$

Find the current through the element at:

- (a) $t = 1$ sec
- (b) $t = 2.5$ sec
- (c) $t = 3.5$ sec

a) $i = -1 \text{ mA}$ ✓

b) $i = 0 \text{ mA}$ ✓

c) $i = 6 \text{ mA}$ ✓

$$(a) -1 \text{ mA}$$

$$(b) 0 \text{ mA}$$

$$(c) 6 \text{ mA}$$

Find the total energy absorbed by the device over the period $0 < t < 5 \text{ sec}$:

$$\begin{array}{llll}
 \frac{1s}{(-10V)(-1mA)} & \frac{2s}{(-5V)(-1mA)} & \frac{3s}{(30V)(0mA)} & \frac{4s}{(30V)(6mA)} \\
 = 10 \text{ mJ} & = 5 \text{ mJ} & = 0 \text{ mJ} & = 180 \text{ mJ} \\
 \checkmark & \checkmark & \checkmark & - \\
 \frac{5s}{(20V)(2A)} & E_T = 235 \text{ mJ} & & \\
 = 40 \text{ mJ} & & &
 \end{array}$$


15

$$E = P * t$$

$$\text{Total Energy} = 235 \text{ mJ}$$

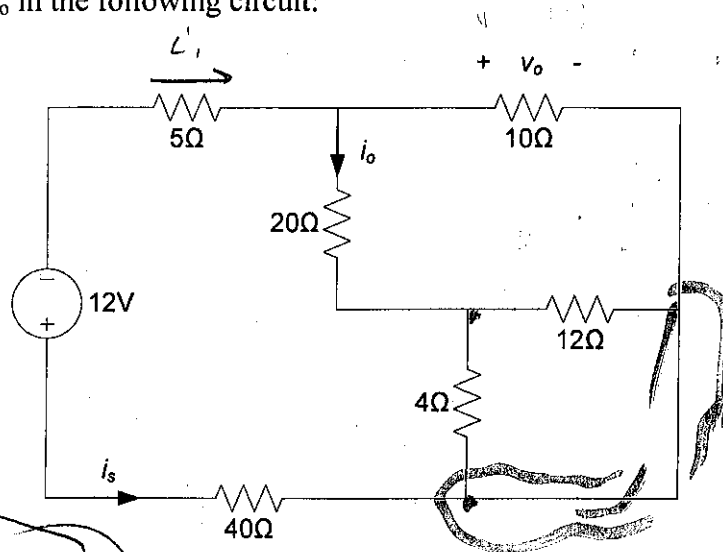Question 1(ii):

Find i_s , i_o and v_o in the following circuit:



$$i_s = \frac{12V}{40\Omega} = 0.3A$$

$$i_1 = \frac{-12V}{5\Omega} = -2.4A$$

$$i_o = \frac{10}{20+10} i_1 = \frac{10}{20+10} \times 2.4 = -0.8A$$

0

$$v_{R20} = (20)(-0.8) \quad v_o = -16V$$

$$= -16V$$



$$i_s = 0.3 A$$


$$i_o = -0.8 A$$

$$v_o = -16 V$$

Question 2:

Use mesh analysis to solve for i_x in the following circuit:

$$i_1 = i_x$$

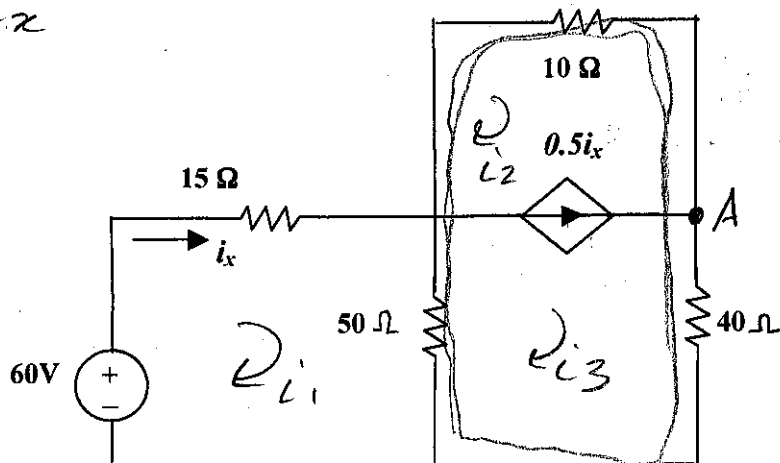

$$\text{M1} \quad -60 + 15i_1 + 50(i_1 - i_2) = 0$$

$$65i_1 - 50i_2 = 60$$

$$13i_1 - 10i_2 = 12$$

$$\begin{bmatrix} 13 & 0 & -10 \\ 5 & -1 & -9 \\ 1 & 2 & -2 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix}$$

Using calculator...

$$\Delta = 150 \quad \Delta_1 = 240$$

$$\frac{240}{150} = 1.6 \text{ A} = i_x$$

SM

$$10i_2 + 40i_3 + 50(i_3 - i_1) = 0$$

$$10i_2 + 40i_3 + 50i_3 - 50i_1 = 0$$

$$-50i_1 + 40i_2 + 90i_3 = 0$$

$$5i_1 - i_2 - 9i_3 = 0$$

@ A

$$i_3 = i_2 + 0.5i_x$$

$$0.5i_1 + i_2 - i_3 = 0$$


$$i_1 + 2i_2 - 2i_3 = 0$$

25

$i_x = 1.6 A$

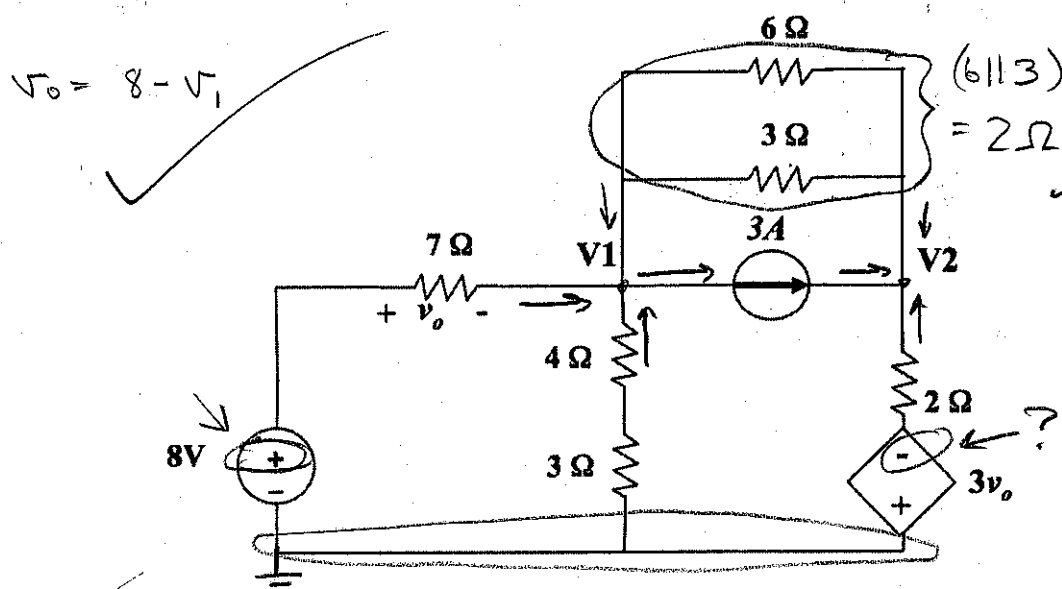Question 3:

Using nodal analysis, determine V_1 and V_2 in the following circuit:



@1

$$\frac{8-v_1}{7} + \frac{v_2-v_1}{2} + \frac{0-v_1}{3} - 3 = 0$$

$$\begin{bmatrix} 11 & -7 \\ 2 & -1 \end{bmatrix} = \begin{bmatrix} -26 \\ 9 \end{bmatrix}$$

$$16 - 2v_1 + 7v_2 - 7v_1 - 2v_1 - 42 = 0$$

using calculator...

$$-26 - 11v_1 + 7v_2 = 0$$

$$11v_1 - 7v_2 = -26$$

$$\Delta = 3 \quad \Delta_1 = 89 \quad \Delta_2 = 41$$

$$v_1 = \frac{89}{3} = 29.67 \text{ V}$$

$$v_2 = \frac{41}{3} = 13.67 \text{ V}$$

@2

$$\frac{v_1-v_2}{2} + 3 + \frac{-3v_o-v_2}{2} = 0$$

$$v_1 - v_2 + 6 - 3v_o - v_2 = 0$$

$$v_1 - v_2 + 6 - 3(8-v_1) - v_2 = 0$$

$$v_1 - v_2 + 6 - 24 + 3v_1 - v_2 = 0$$

$$4v_1 - 2v_2 = 18$$

$$2v_1 - v_2 = 9$$

$$-1v_1 - 1v_2 = -32$$

$$\Delta = -18 \quad v_1 = \frac{-198}{-18} = 11 \text{ V}$$

$$\Delta_1 = -198 \quad v_2 = \frac{-378}{-18} = 21 \text{ V}$$

23

$$V_1 = 29.67 \text{ V}$$

$$V_2 = 13.67 \text{ V}$$

Question 4:


Find the maximum power that can be transferred to the resistor R_L in the following circuit:

applying current of 1A

$$P_{MAX} = \frac{V_{th}^2}{4 \times R_{th}}$$

$$R_{th} = \frac{V_o}{I_o} = \frac{V_o}{1}$$

Exciting circuit with 1A.

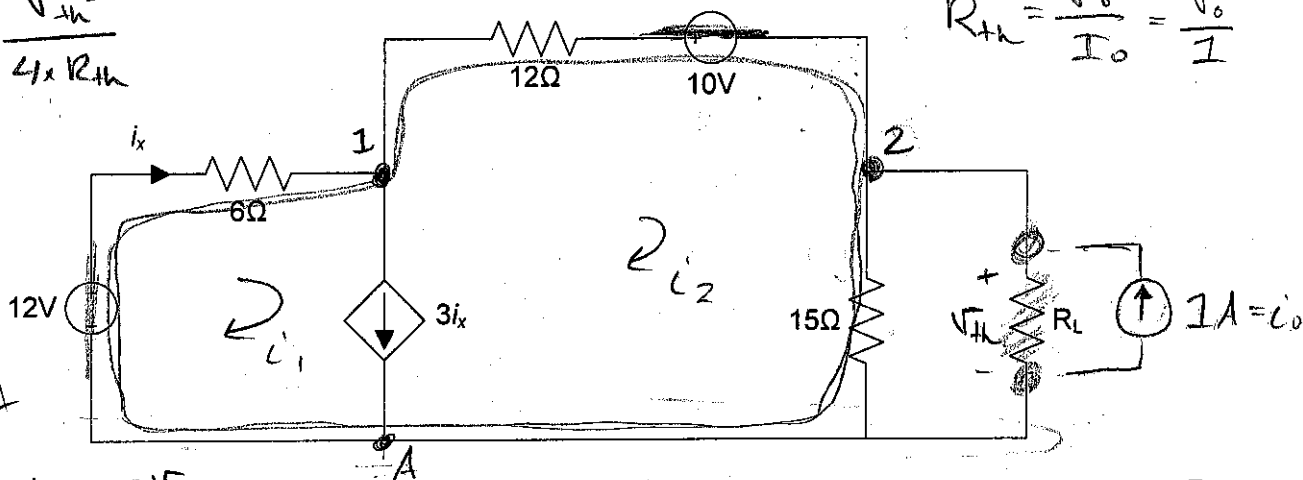

@1 $i_2 = -\frac{v_1}{6}$

$$\frac{0-v_1}{6} - 3i_x + \frac{v_2-v_1}{12} = 0$$

$$\frac{0-v_1}{6} + \frac{v_1}{2} + \frac{v_2-v_1}{12} = 0$$

$$-2v_1 + 6v_1 + v_2 - v_1 = 0$$

$$3v_1 + v_2 = 0$$

@2

$$\frac{v_1-v_2}{12} + \frac{0-v_2}{15} + 1 = 0$$

$$15v_1 - 15v_2 - 12v_2 + 180 = 0$$

$$15v_1 - 27v_2 = -180$$

$$5v_1 - 9v_2 = -60$$

$$\begin{bmatrix} 3 & 1 \\ 5 & -9 \end{bmatrix} = \begin{bmatrix} 0 \\ -60 \end{bmatrix} \text{ using calculator...}$$

$$\Delta = -32 \quad \Delta_2 = +180$$

$$v_2 = \frac{-180}{-32} = 5.625V$$

$$R_{th} = \frac{5.625}{1} = 5.625\Omega \quad \checkmark$$

Solving for V_{th}

SM

$$-12 + 6i_1 + 12i_2 + 10 + 15i_2 = 0$$

$$6i_1 + 27i_2 = 22$$

CA

$$i_1 = i_2 + 3i_x$$

$$i_1 = i_2 + 3i_1$$

$$-2i_1 = i_2$$

$$i_1 = -\frac{i_2}{2}$$

$$6\left(-\frac{i_2}{2}\right) + 27i_2 = 22$$

$$-3i_2 + 27i_2 = 22$$

$$24i_2 = 22$$

$$i_2 = \frac{11}{12}$$

$$i_x = i_1 \quad V_{th} = 15i_2$$

$$V_{th} = 15 \times i_2 = 13.75$$

Max power

$$\frac{(13.75)^2}{4 \times 5.625}$$

$$= 8.41W$$

20

$$P_{L(max)} = 8.4 \text{ W}$$