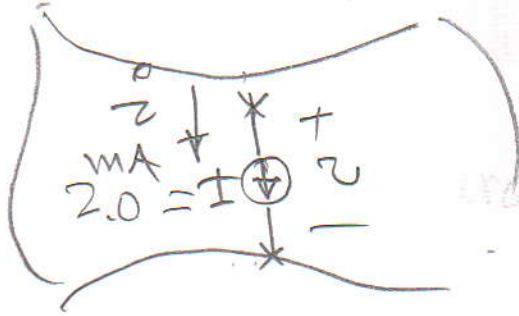



Current Sources & Current Sinks

Ideal current source.



$i = I$, say 2.0 mA
irrespective
of v

$R_o \ll$

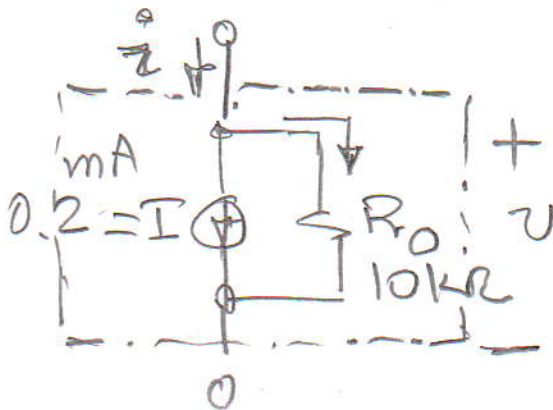

$$i = I + \frac{v}{R_o}$$


i depends on v

If $R_o \rightarrow \infty \Rightarrow \underline{i = I}$


R_o : internal resistance, or,
output resistance, or,
Norton resistance.

$$\Delta i = \frac{\Delta v}{R_o} \quad (\text{since } I \text{ is constant})$$
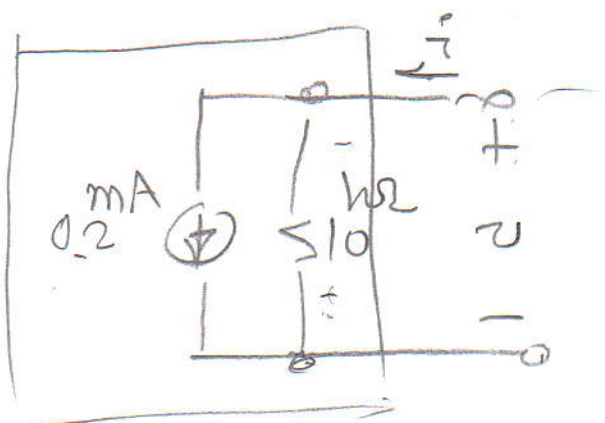
$$\Rightarrow \boxed{\frac{\Delta i}{\Delta v} = \frac{1}{R_o}}$$




||

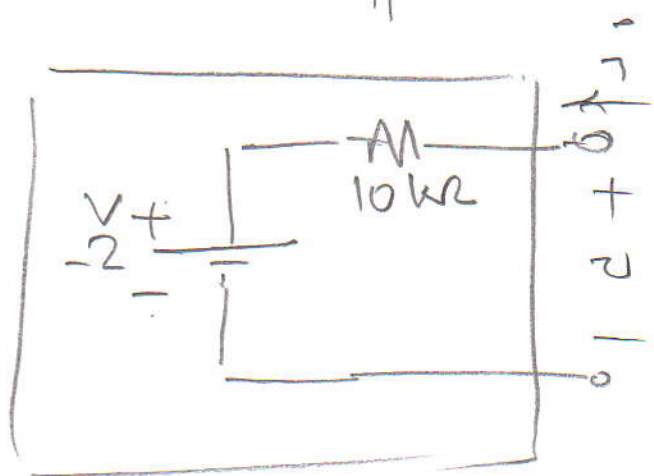


Implement

3/

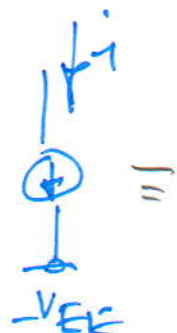

=

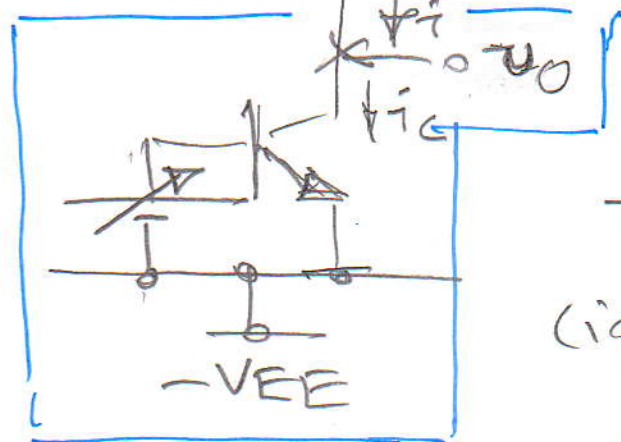

Current Sink

$$i_c = I_s e^{v_{BE}/V_T}$$

(ignoring Early eff.)

$$\Rightarrow i = i_c \Rightarrow$$


$$i = I_s e^{v_{BE}/V_T}$$

if $v_{CE} \geq 0.3V$ (active mode)


$$v_o - (-V_{EE}) \geq 0.3V$$

$$\Rightarrow v_o \geq -V_{EE} + 0.3V$$

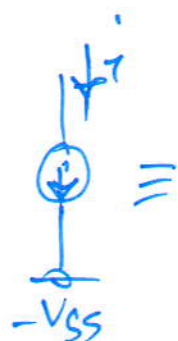condition for the current sink to remain a current sink aka "compliance".



=




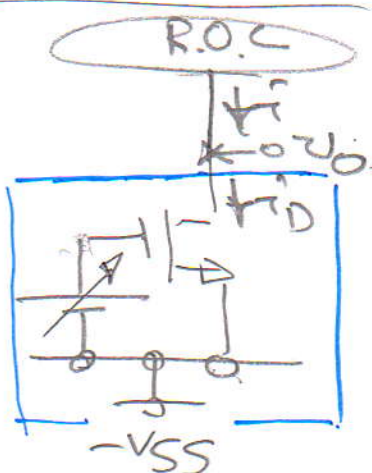


$$i = i_D = \frac{1}{2} K (V_{GS} - V_t)^2$$

(ignoring E. Eff.)

if $v_{DS} \geq V_{GS} - V_t$
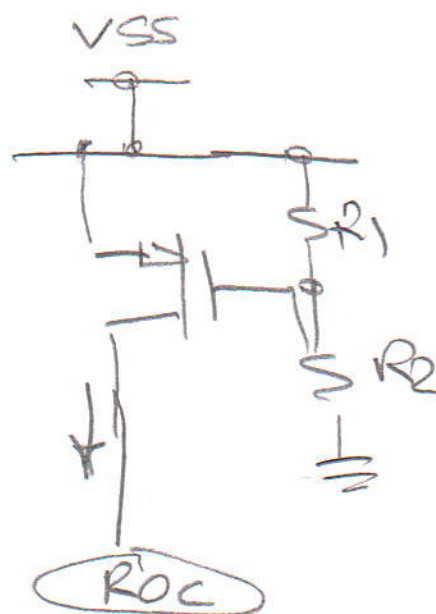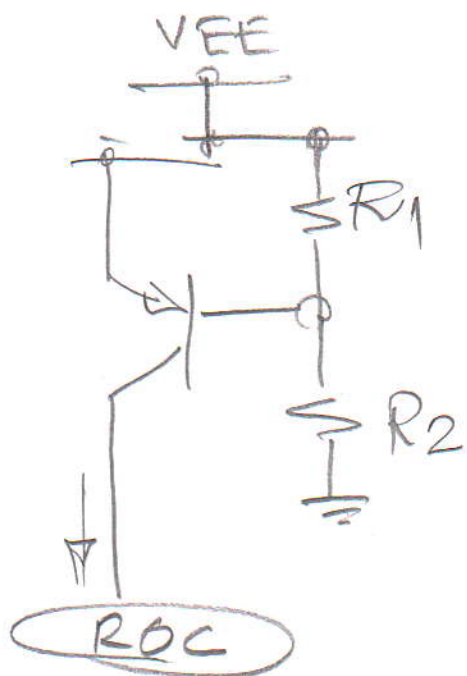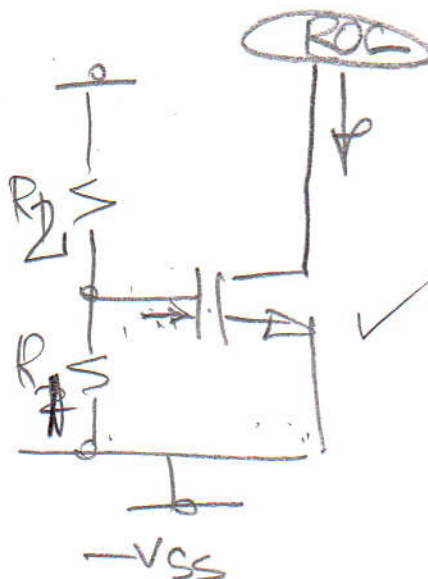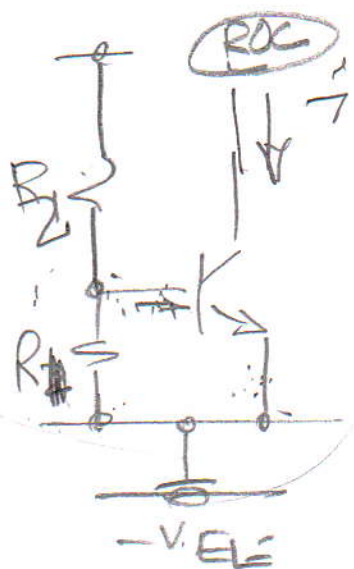
$$\Rightarrow v_o - (-V_{SS}) \geq V_{GS} - V_t$$



Example #1

$$K = 1.0 \text{ mA/V}^2$$


$$V_t = -0.8 \text{ V}$$

$$V_A = \infty$$

- Current Source

$$- I \approx 0.125$$
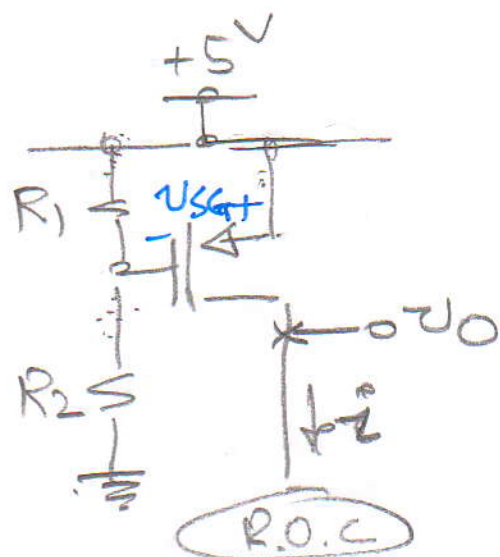
$$- \underline{+5 \text{ V}, 0 \text{ V}}$$



$$I_D = \frac{1}{2} K V_{OV}^2$$

$$0.125 = \frac{1}{2} \times 1.0 \times V_{OV}^2$$

$$\Rightarrow V_{OV} = 0.5 \text{ V}$$



$$\begin{aligned} V_{SG} &= V_{OV} + |V_t| \\ &= 0.5 + 0.8 \\ &= \underline{1.3 \text{ V}} \end{aligned}$$

$$V_{SG} = \frac{+5 \text{ V}}{R_1 + R_2} \times R_1 \Rightarrow 1 + \frac{R_2}{R_1} = \frac{5}{1.3}$$


$$\Rightarrow R_2/R_1 = 2.846$$

$$\Rightarrow \boxed{R_2 = 2.846 R_1}$$
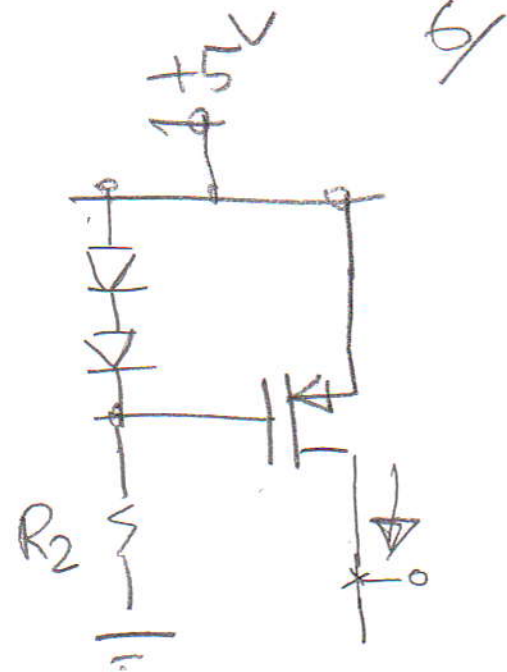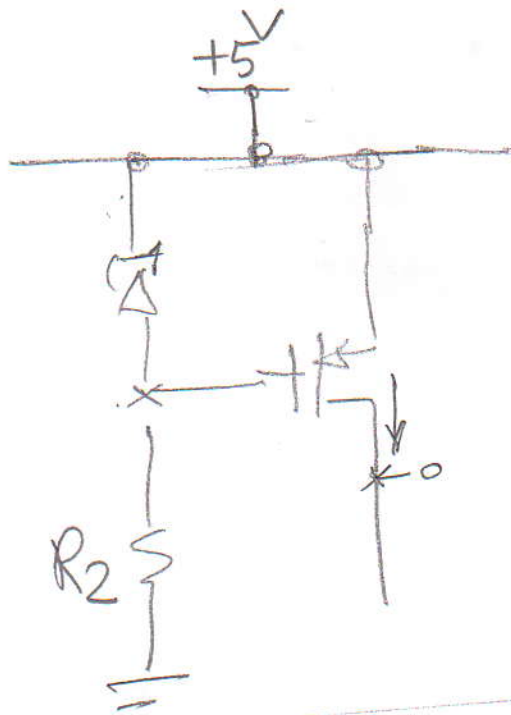
$$\begin{aligned} v_{SD} \geq V_{OV} &\Rightarrow 5 \text{ V} - v_O \geq 0.5 \text{ V} \\ &\Rightarrow \underline{v_O \leq 4.5 \text{ V}} \end{aligned}$$




Can we do better?

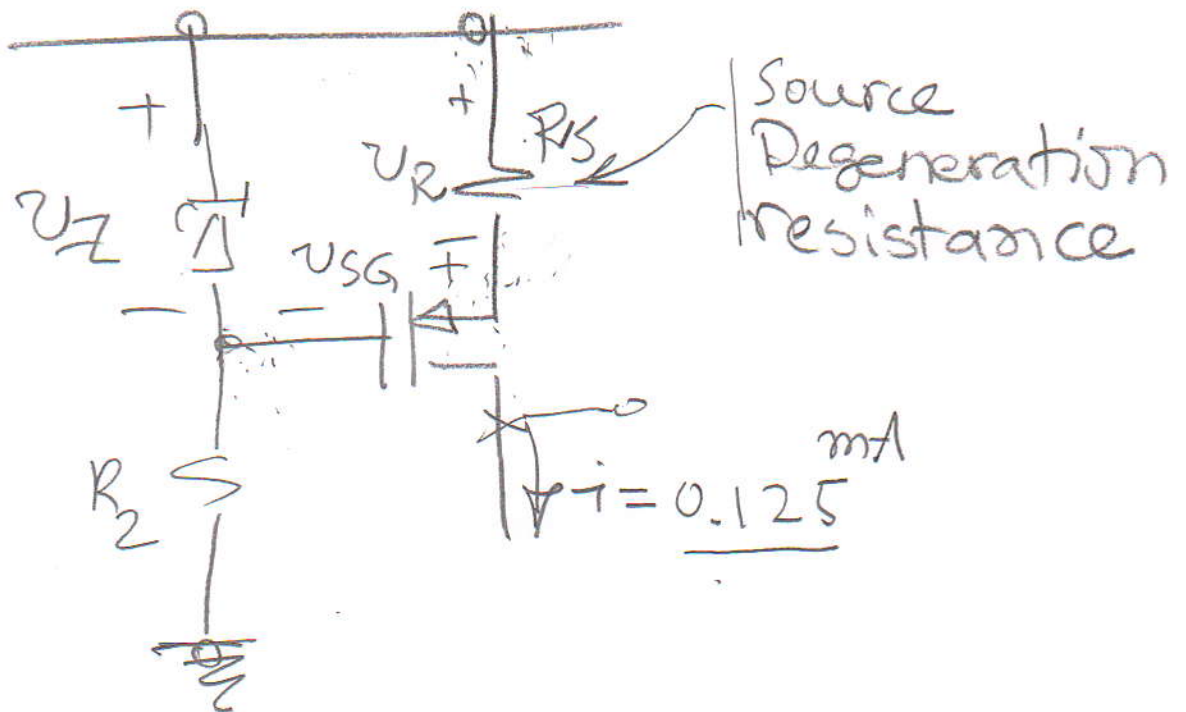

Previous Example

$$\tau = 0.125 \Rightarrow \underline{V_{SG} \approx 1.3V}$$

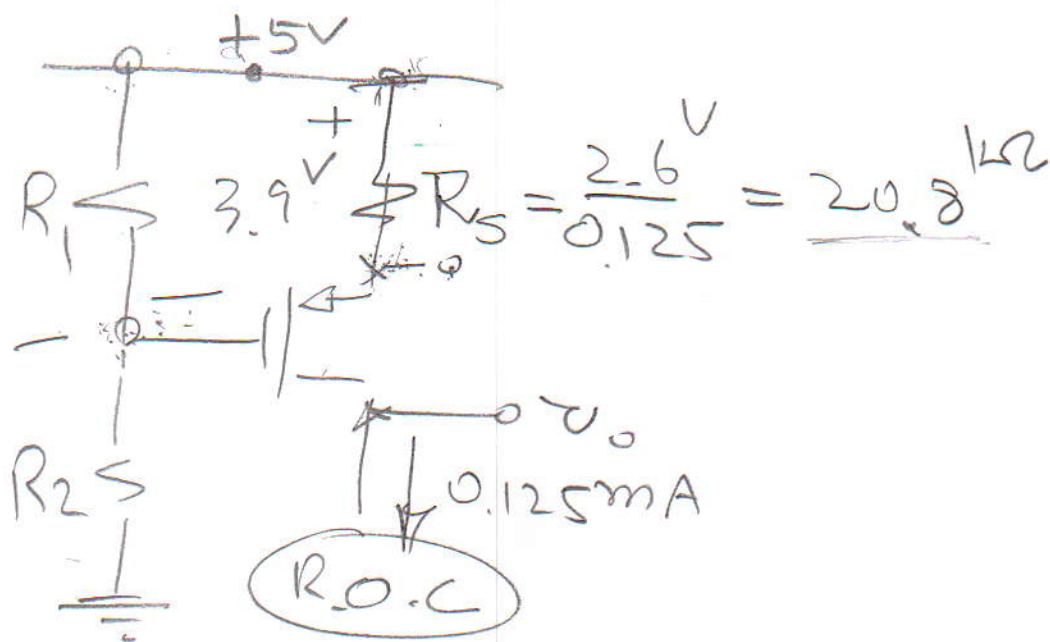let $V_R = \underbrace{2 V_{CE}}_{2.6V}$ (the larger the better)



$$3.9 = \frac{+5V}{R_1 + R_2} R_1 \Rightarrow$$

$$\frac{R_2}{R_1} = 0.282 \Rightarrow \underline{R_2 = 0.282 R_1}$$



$$V_{SD} \geq \underbrace{V_{SG} - |V_t|}_{V_{ov}} \Rightarrow \underbrace{(5 - 2.6)}_{V_S} - v_o \geq 0.5V$$

$$\Rightarrow \underline{v_o \leq 1.9V}$$

Sensitivity to k

- 8
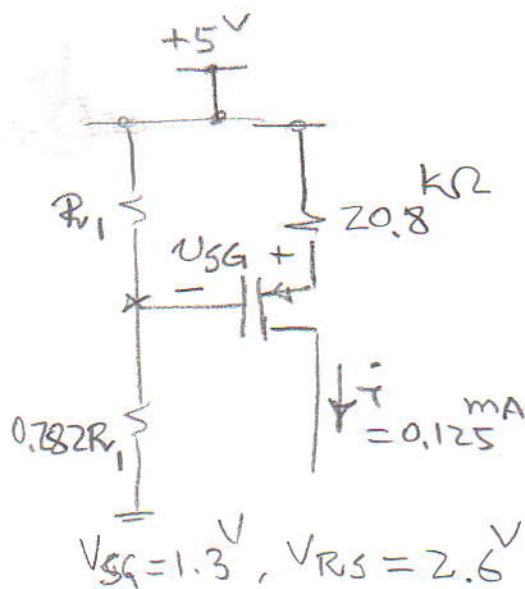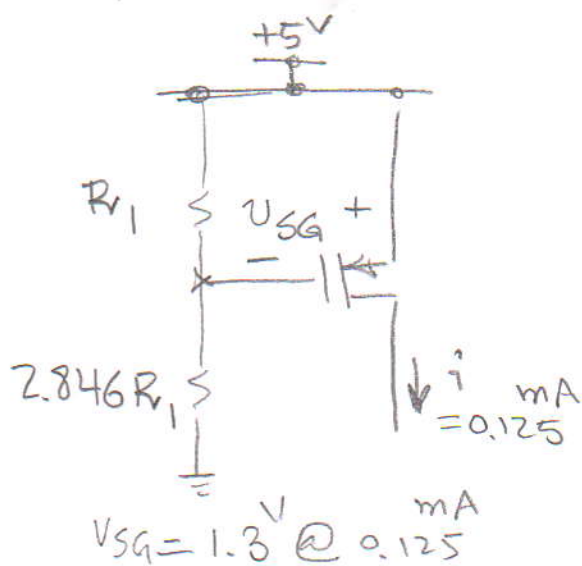
$$\left. \begin{array}{l} K = 1.0 \text{ mA/V}^2 \\ V_t = -0.8 \text{ V} \end{array} \right\} \text{ - nominal parameters}$$



Now, if $K = 1.1 \text{ mA/V}^2$

$$i = \frac{1}{2} \times 1.1 \times (1.3 - 0.8)^2 = 0.1375 \text{ mA}$$

without Source Degeneration.

The change in current, relative to the designed value of 0.125 mA is 10%

$$V_{SG} + 20.8i = 3.9 \text{ V}$$

$$V_{SG} + 20.8 \times \frac{1}{2} \times 1.1 (V_{SG} - 0.8)^2$$

$$V_{SG} + 11.44 (V_{SG}^2 - 1.6V_{SG} + 0.64) = 3.9$$

$$11.44V_{SG}^2 - 17.3V_{SG} + 3.42 = 0$$

$$V_{SG} = \frac{17.3 \pm \sqrt{(17.3)^2 - 4 \times 11.44 \times 3.42}}{2 \times 11.44}$$

$$= 1.278 \text{ V}$$



$$\Rightarrow i = \frac{1}{2} \times 1.1 \times (1.278 - 0.8)^2$$

$$= 0.1257 \text{ mA}$$

with Source Degeneration. The change in the current, relative to 0.125 mA is only 0.56%

Sensitivity to V_t

9

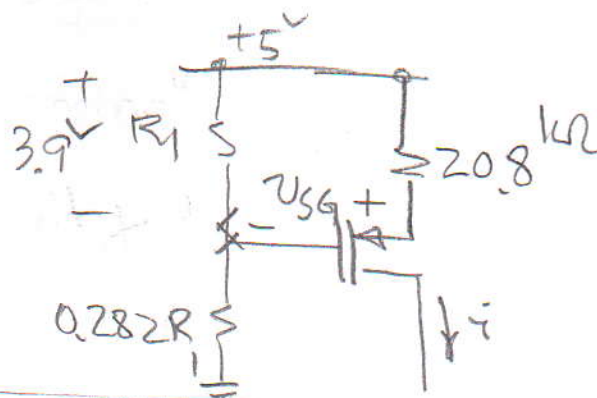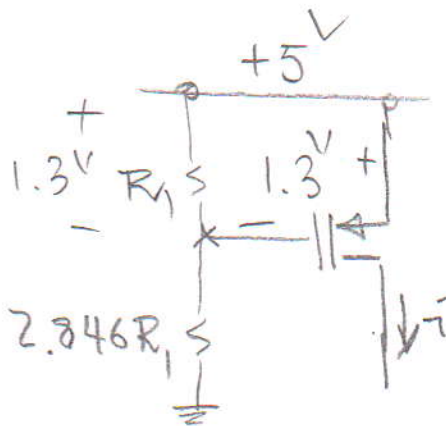

If $V_t = -0.85V$,

$$i = \frac{1}{2} \times 1.0 \times (1.3 - 0.85)^2$$

$$= \underline{0.101 \text{ mA}}$$

-19.2% change in the current due to the change in V_t from $-0.8V$ to $-0.85V$.

$$V_{SG} + 20.8i = 3.9$$

$$V_{SG} + 20.8 \times \frac{1}{2} \times 1.0 \times (V_{SG} - 0.85)^2 = 3.9$$

$$V_{SG} + 10.4(V_{SG}^2 - 1.7V_{SG} + 0.7225) = 3.9$$

$$10.4V_{SG}^2 - 16.68V_{SG} + 3.614 = 0$$


$$V_{SG} = \frac{16.68 \pm \sqrt{(16.68)^2 - 4 \times 10.4 \times 3.614}}{2 \times 10.4}$$

$$V_{SG} = 1.345V$$


$$i = \frac{1}{2} \times 1 \times (1.345 - 0.85)^2$$

$$= \underline{0.122 \text{ mA}}$$

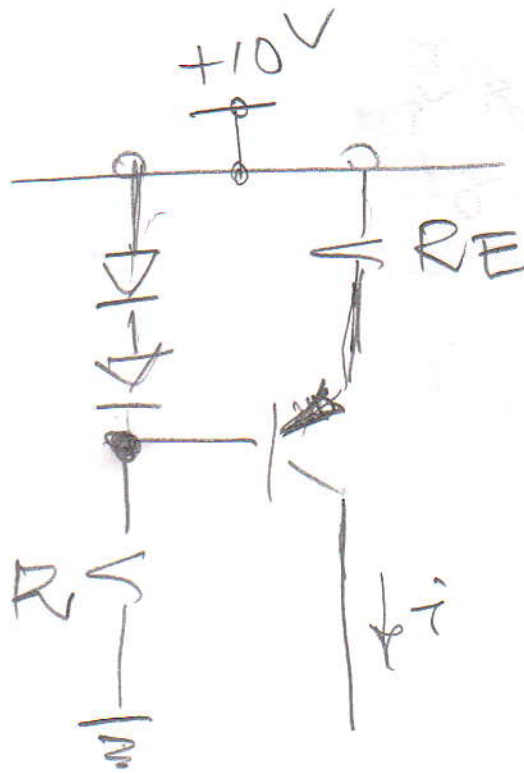-2.4% change in current due to the change ~~from~~ in V_t from $-0.8V$ to $-0.85V$.



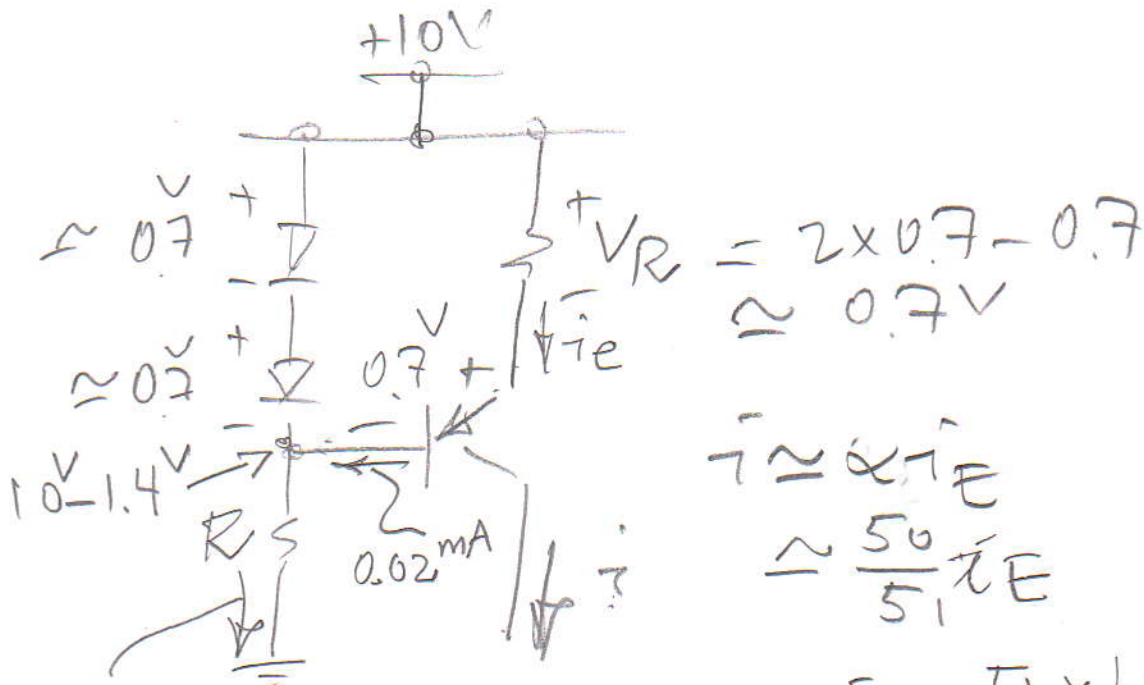$\beta = 50$
 $i \approx 1.0 \text{ mA}$
choose R_E & R



$$V_R = 2 \times 0.7 - 0.7 \approx 0.7 \text{ V}$$

$$i \approx \beta i_E \approx \frac{50}{51} i_E$$


$$\Rightarrow i_E = \frac{51 \times 1}{50} \text{ mA} = 1.02 \text{ mA}$$

$$R_E \approx \frac{0.7 \text{ V}}{1.02} = 0.686 \text{ k}\Omega \text{ or } \underline{680 \Omega}$$


$$i \approx 10 i_B = 0.2 \text{ mA}$$

$$R = \frac{10 \text{ V} - 1.4 \text{ V}}{0.2} = \underline{43 \text{ k}\Omega}$$

Internal Resistance

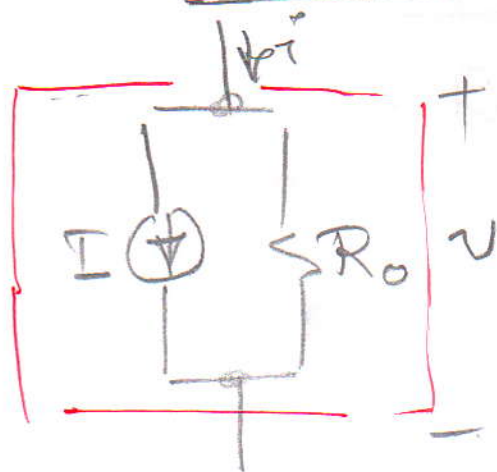


Physical nature of R_o :
Early effect

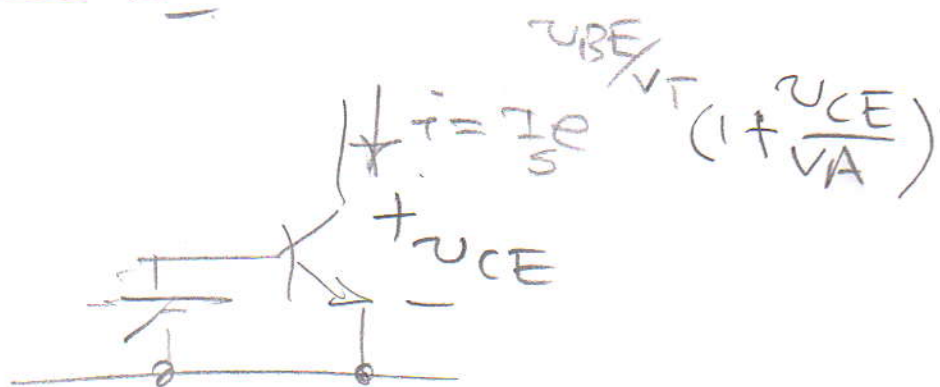


How to find R_o




Do small-signal (ac) analysis

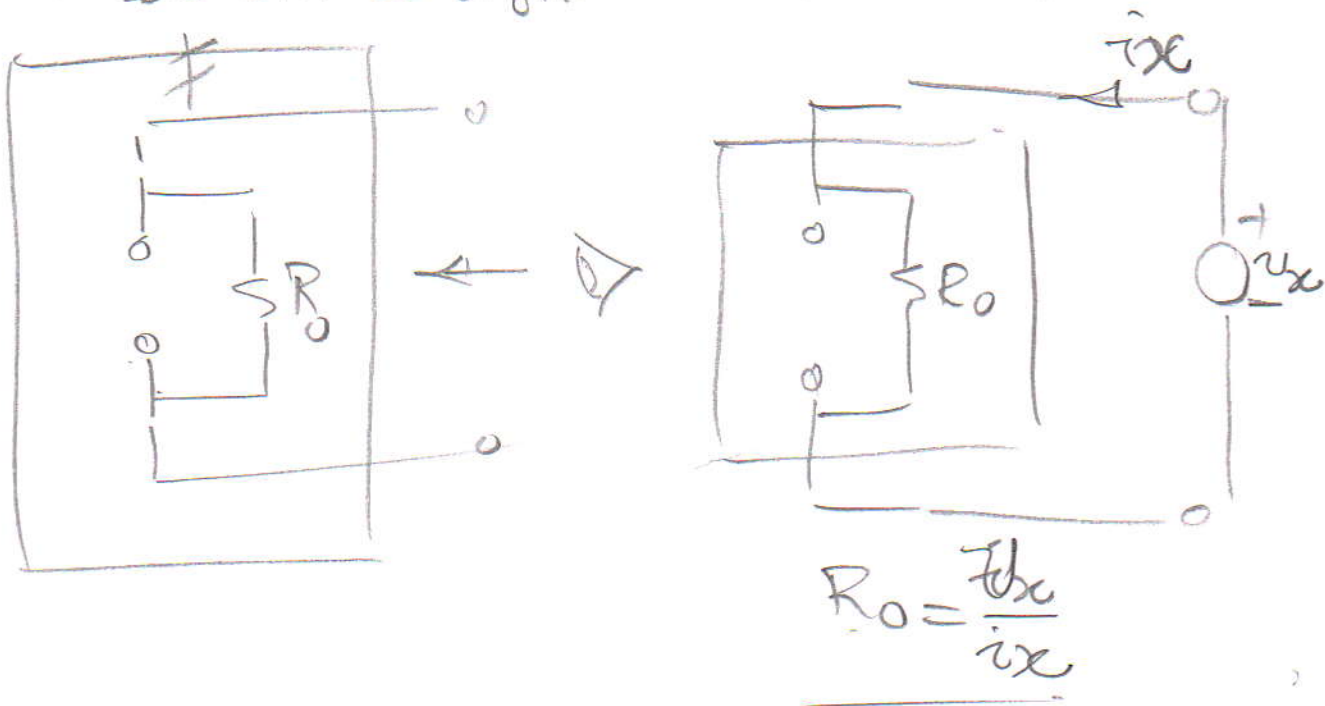


R.O.C

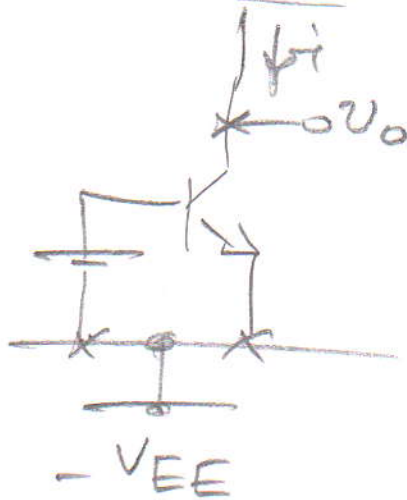Find R_o


ac analysis

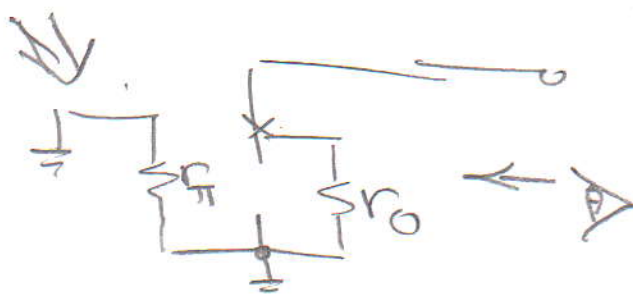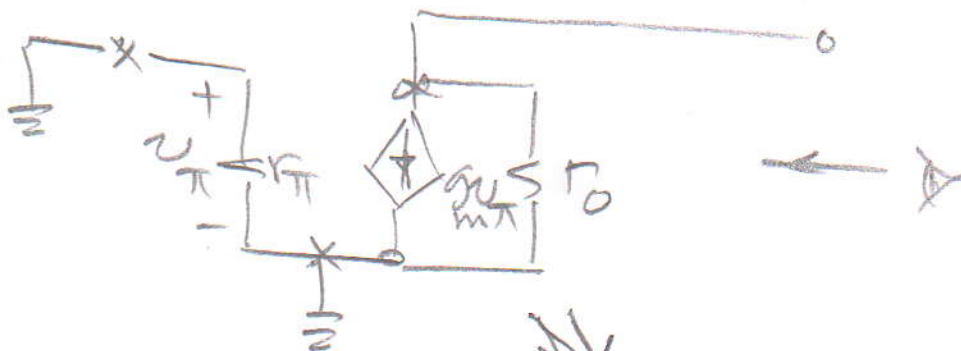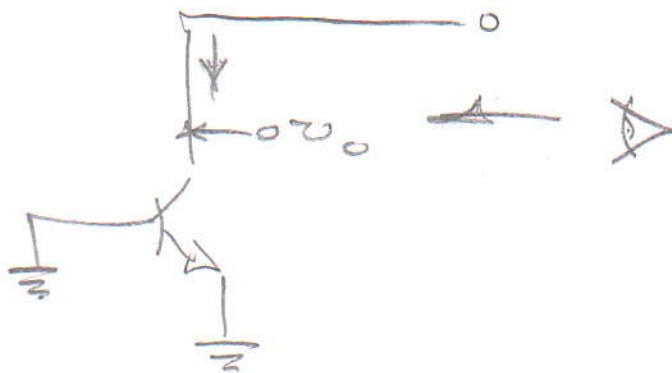

$$R_o = r_o$$

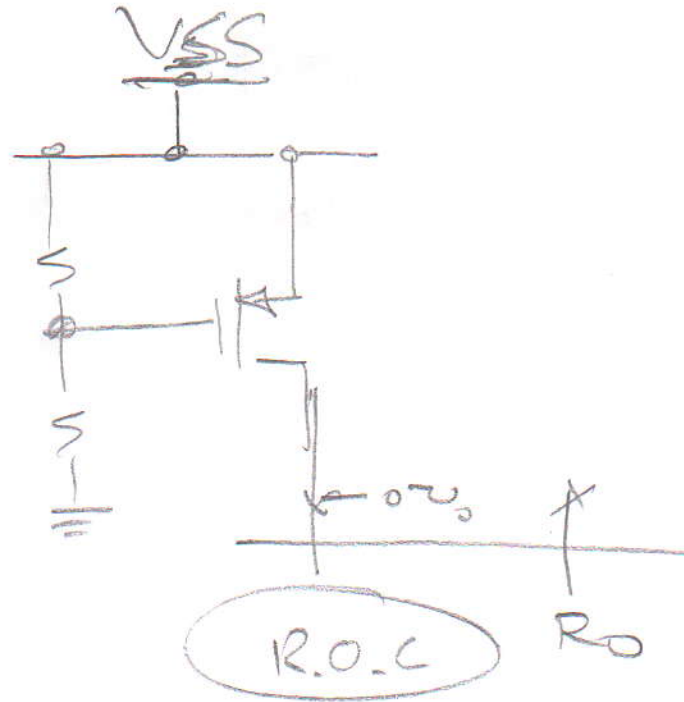


ac analysis.

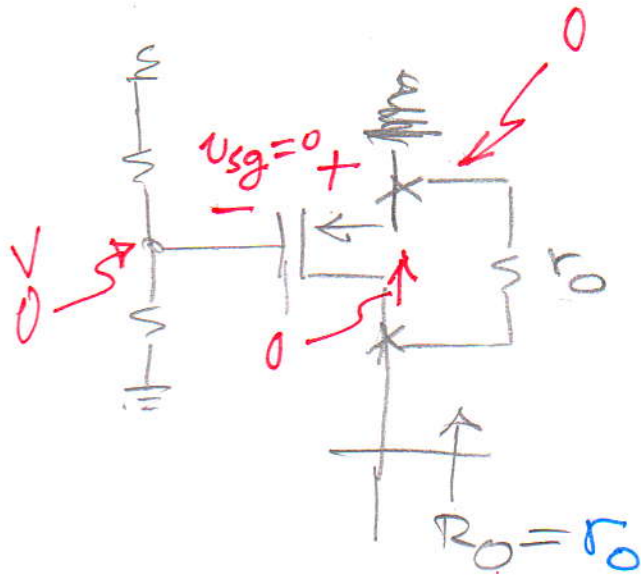


In general, $R_O = r_o$ if the emitter or source is grounded (ac wise).

Cases with Emitter Degeneration (Source Degeneration) Resistance


14

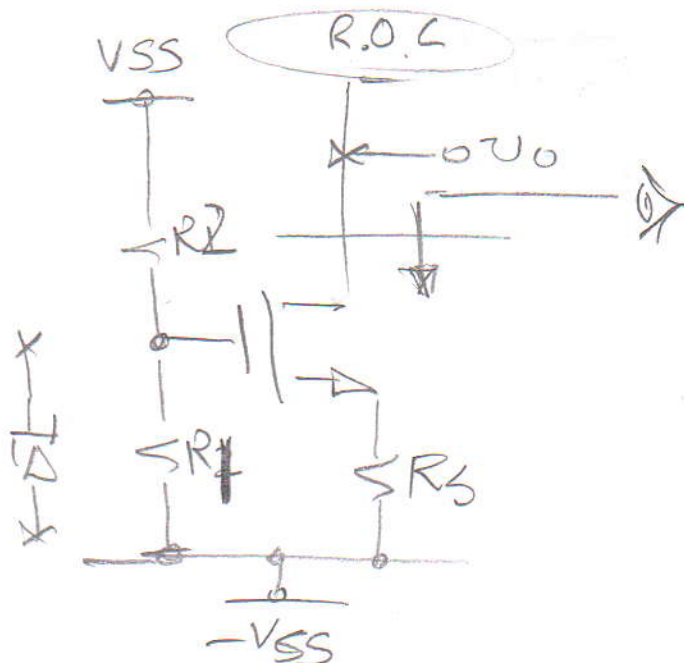

ac analysis

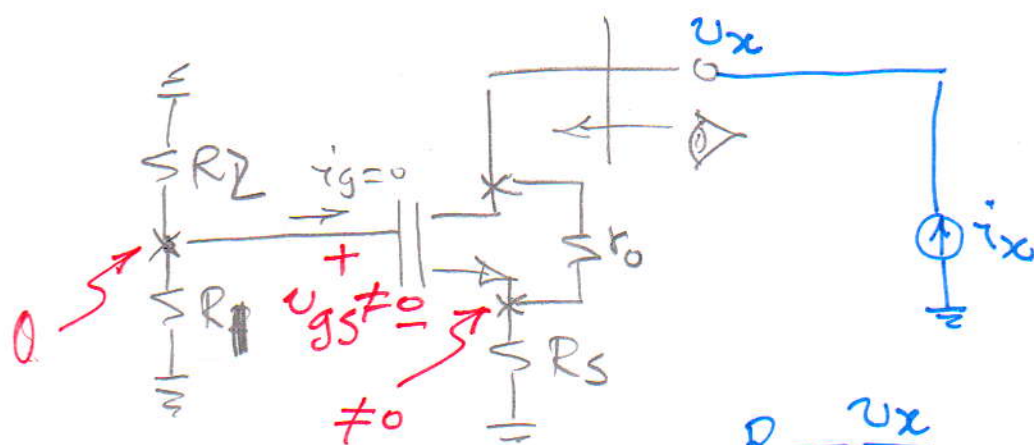

$$R_o = \frac{v_x}{i_x}$$

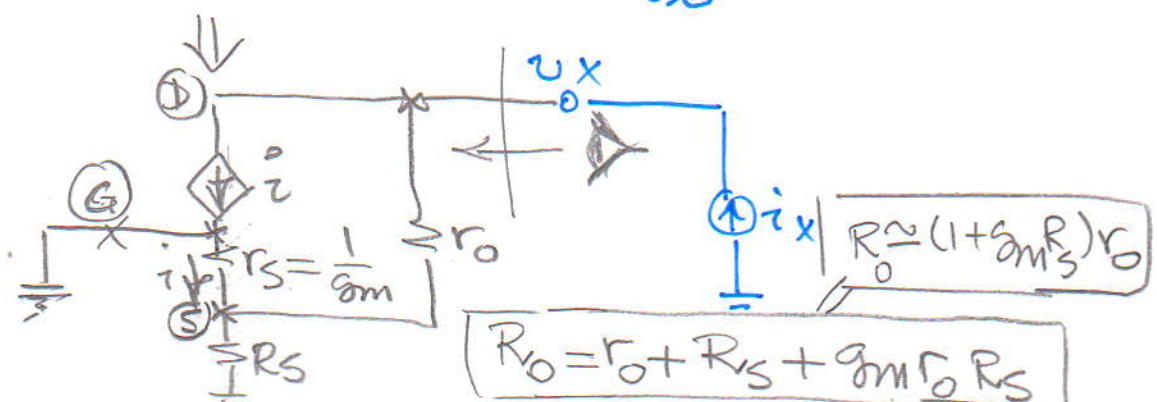

$$R_o = r_o + R_S + g_m r_o R_S$$


$$K = 1.0 \text{ mA/V}^2$$

$$I = 0.125 \text{ mA}$$

$$V_A = -20 \text{ V}$$


$$r_o = \frac{|V_A|}{I} = \frac{20}{0.125} = 160 \text{ k}\Omega$$
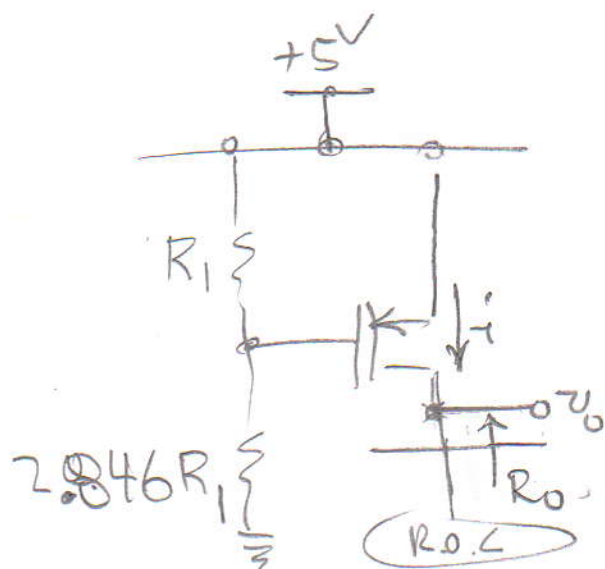
$$\Rightarrow g_m = \sqrt{2KI_D} = \sqrt{2 \times 1 \times 0.125} = \sqrt{0.25} = 0.5 \text{ mS}$$



$$R_o = r_o = 160 \text{ k}\Omega$$
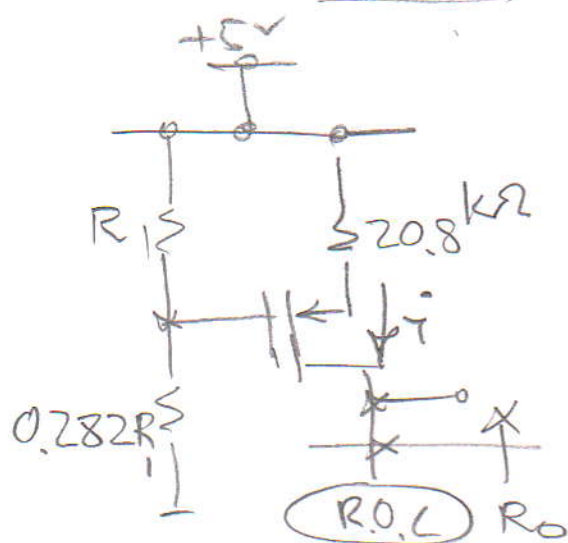
$$\frac{\Delta i}{\Delta v_o} = \frac{1}{R_o} = \frac{1}{160} = 6.25 \mu\text{A/V}$$



$$R_o = r_o + R_s + g_m r_o R_s = 160 + 20.8 + 0.5 \times 20.8 \times 160$$

$$= 18448 \text{ k}\Omega^{10.4}$$

$$= 1.84 \text{ M}\Omega$$


$$R_o \approx (1 + g_m R_s) r_o$$

$$= (1 + 10.4) \times 160$$


$$= 1824 \text{ k}\Omega$$

$$= 1.82 \text{ M}\Omega$$
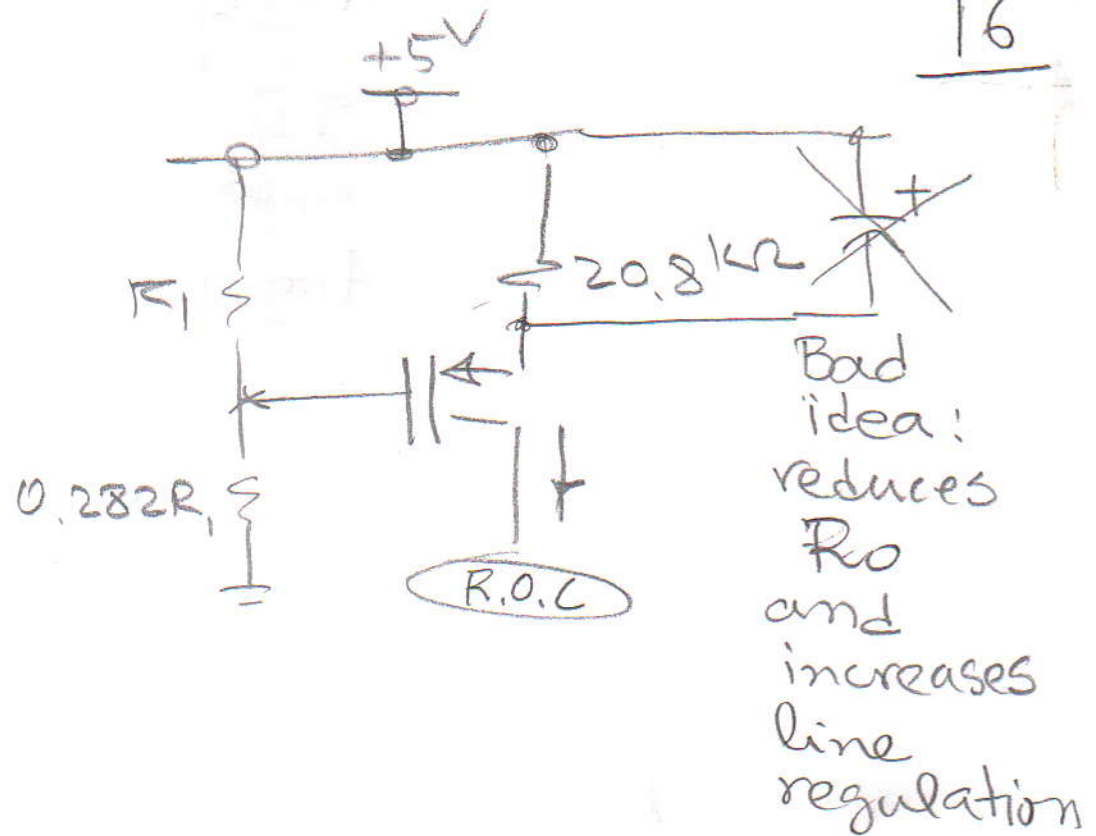
$$\frac{\Delta i}{\Delta v_o} = \frac{1}{R_o} = \frac{1}{1.84} = 0.54 \mu\text{A/V}$$



For BJT

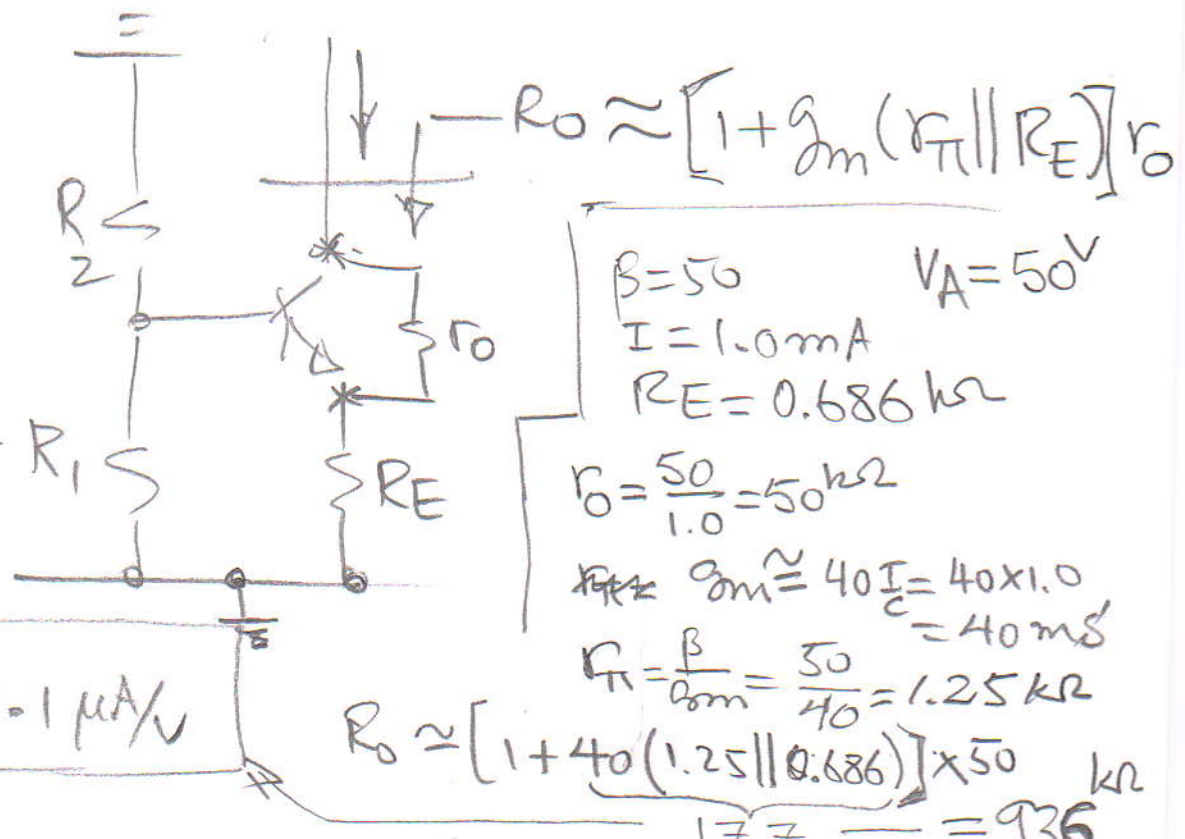

$$R_o \approx [1 + g_m(r_{\pi} \parallel R_E)] r_o$$

$$\beta = 50 \quad V_A = 50V$$

$$I = 1.0 \text{ mA}$$

$$R_E = 0.686 \text{ k}\Omega$$

$$r_o = \frac{50}{1.0} = 50 \text{ k}\Omega$$

$$g_m \approx 40 I_E = 40 \times 1.0 = 40 \text{ mS}$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{50}{40} = 1.25 \text{ k}\Omega$$

$$R_o \approx [1 + 40(1.25 \parallel 0.686)] \times 50 \text{ k}\Omega$$

$$\frac{\Delta i}{\Delta V_o} = \frac{1}{936} \approx 1.07 \mu\text{A/V}$$

Temperature Invariant Sources

17

