

Final Answers Only

Ryerson University
Department of Electrical and Computer Engineering
ELE404 (Electronic Circuits I)
Midterm Examination (P2014)
May 2014
Duration: 120 minutes
Examiner: Prof. A. Yazdani

Name:.....
[Print Last Name] [Print First Name]

Student No:..... Section No:....

NOTES

1. This is a closed-book examination. No aids other than basic calculators are permitted.
2. The examination paper is comprised of **FOUR QUESTIONS**, each question is worth as indicated in the following Table. The entire examination is worth 100 marks.

Question #	Maximum Mark	Mark Earned
1	25	
2	25	
3	25	
4	25	
Total	100	

3. Answer all questions in the booklet, within the blank spaces provided under each question in this booklet. **DO NOT USE THE REVERSE SIDE.**
4. *If in doubt about any question, clearly state your assumptions in answering the question.*
5. Part marks for an answer will only be given if the *correct methodology* is clearly shown.
6. **DO NOT DETACH** any pages from this booklet.

Q1: In the diode circuit of Fig. 1, $R_1 = 1.5\text{ k}\Omega$, $R_2 = 2.2\text{ k}\Omega$, $R_3 = 1.8\text{ k}\Omega$, $V_{CC} = 10\text{ V}$, $I_x = 5.1\text{ mA}$, and $V_x = -25\text{ V}$. Further, the diodes exhibit a forward voltage drop of 0.7 V . The diodes are assumed to have a large reverse breakdown voltage and, therefore, do not enter their breakdown regions.

Determine the state of conduction of the diodes and calculate the voltages V_1 through V_3 . Summarize your findings in Table 1. Show all the work.

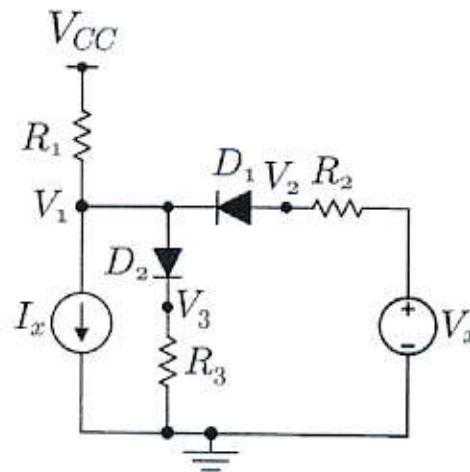


Fig. 1: Diode circuit of Q1.

Table 1: Results of the diode circuit of Q1.

State of D_1	State of D_2	V_1 [V]	V_2 [V]	V_3 [V]
OFF	ON	1.6	-25	0.9

Q2: A 2.4-V low-power electronic gadget is to be powered from a 12-V car outlet. A proposal is to use the circuit of **Fig. 2** in which three series-connected identical diodes are forward-biased by the car outlet voltage through a resistor. Consulting the datasheet, one finds that each diode exhibits a forward voltage drop of 0.65 V at 0.1 mA. Determine the resistance and power consumption of the resistor, R , such that $v_O = 2.4$ V. Show all the work.

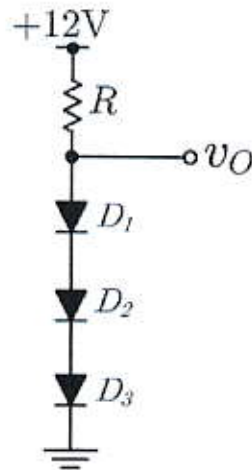


Fig. 2: Voltage regulator of Q2.

$$R = 238 \, \Omega$$

$$P_R = 387 \, \text{mW}$$

Q3: For the rectifier of Fig. 3a, $R_L = 80 \Omega$ and each diode may be assumed to exhibit a forward voltage drop of about 0.6 V . In the lab, a student has recorded the oscilloscope screenshot of Fig. 3b (in which each vertical axis division represents one volt). Determine the *reading of a DC voltmeter* of the voltage v_{rec} , the capacitance C , and the voltage ratio of the step-down transformer. Show all the work or explain. Complete Table 3.

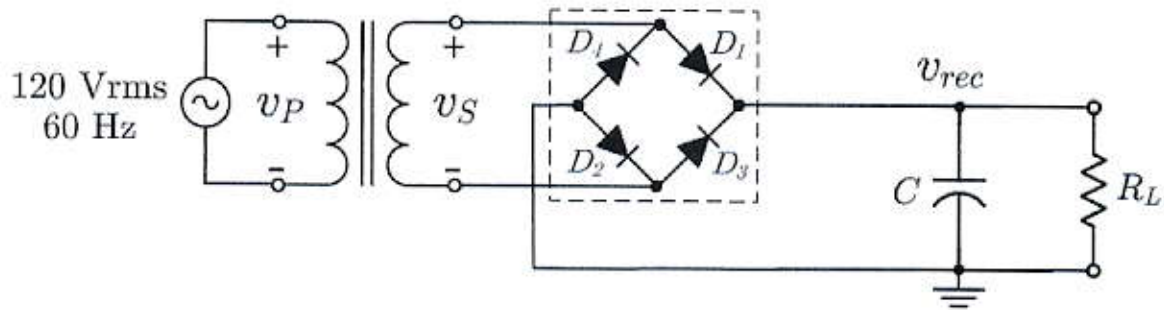


Fig. 3a: Rectifier of Q3.

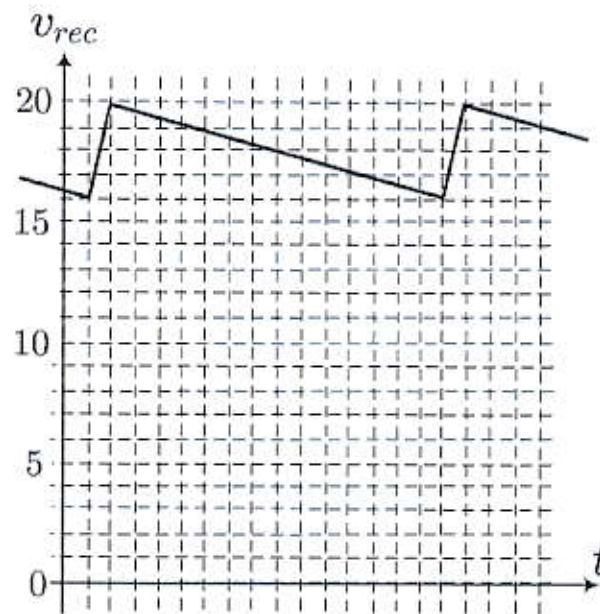


Fig. 3b: Rectifier's output voltage waveform.

Table 3: results of the rectifier of Q3.

Reading of DC voltmeter [V]	C [μF]	Voltage ratio of transformer [V_{rms}/V_{rms}]
18	470	120/15

Q4: In the shunt voltage regulator of Fig. 4, $R_L = 1.0 \text{ k}\Omega$ and $R = 820 \Omega$. According to the manufacturer, the Zener diode gives a voltage of $v_Z = V_{ZT} = 5.1 \text{ V}$ at a test current of $i_Z = I_{ZT} = 20 \text{ mA}$. Further, $r_Z = 10 \Omega$ and $I_{ZK} = 1.5 \text{ mA}$.

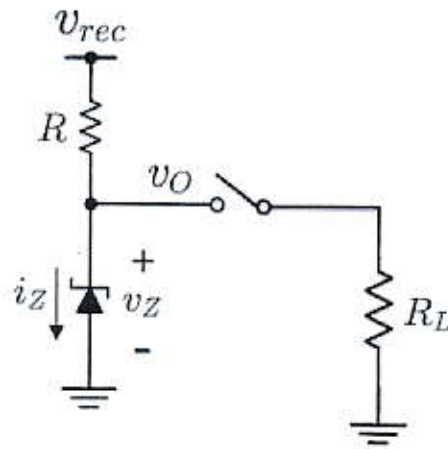


Fig. 4: Shunt regulator of Q4.

(4a) [10 marks] Assuming that the switch is open, determine the peak-to-peak ripple of the output voltage v_O if the unregulated voltage v_{rec} has a peak-to-peak ripple of 4.0 V . Show all the work.

$$\underline{48 \text{ mV}}$$

- (4b) [15 marks] Assuming that the switch is closed, calculate the minimum permissible value of the unregulated voltage v_{rec} , in order for the Zener diode to retain its effectiveness. Show all the work.

$$\underline{10.17 \text{ V}}$$