
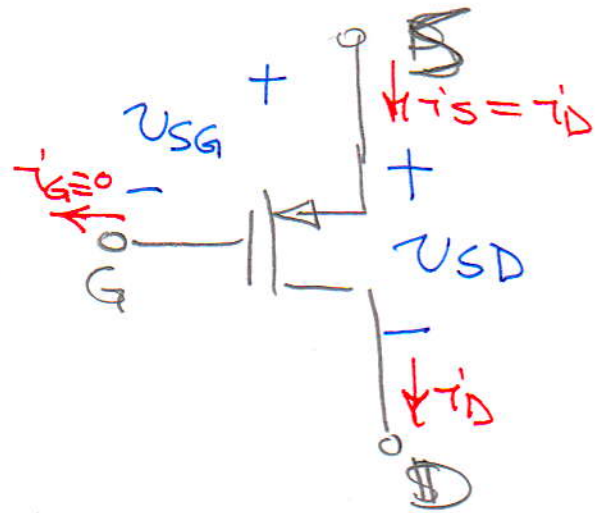
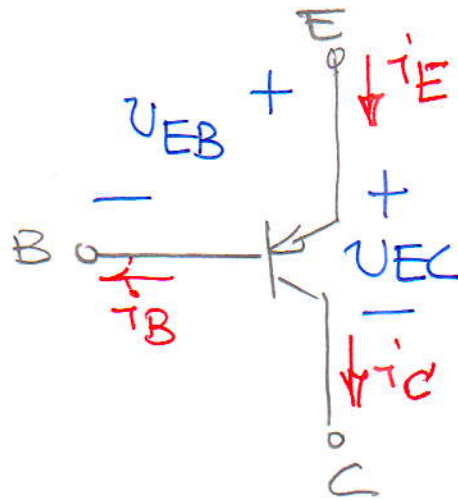
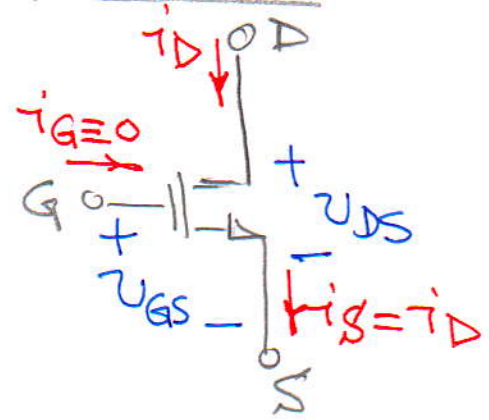


MOS and MOS Amplifiers

①

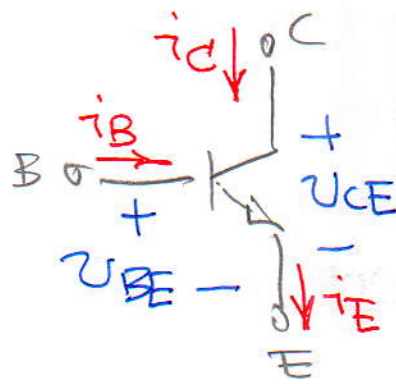


Modes of Operation

②

① Cut-off mode (corresponding to the cut-off mode in BJT)

Focus on NMOS Device:

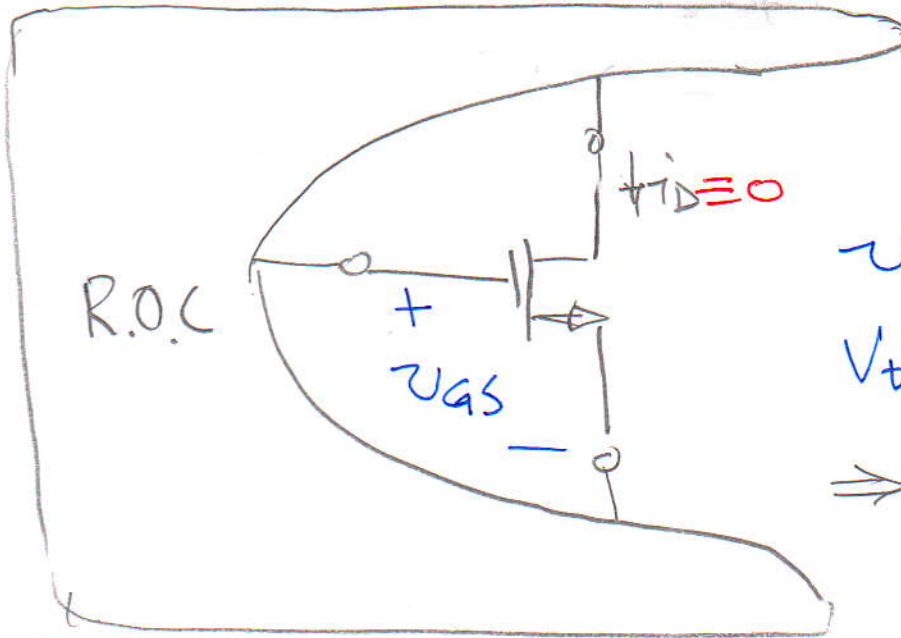

$$V_{GS} < V_{tn}$$


V_{tn} : Threshold voltage

\Rightarrow MOS is "off"

$$\Rightarrow i_D = 0$$

V_{tn} : from 0.5V — 1.5V

Example #1

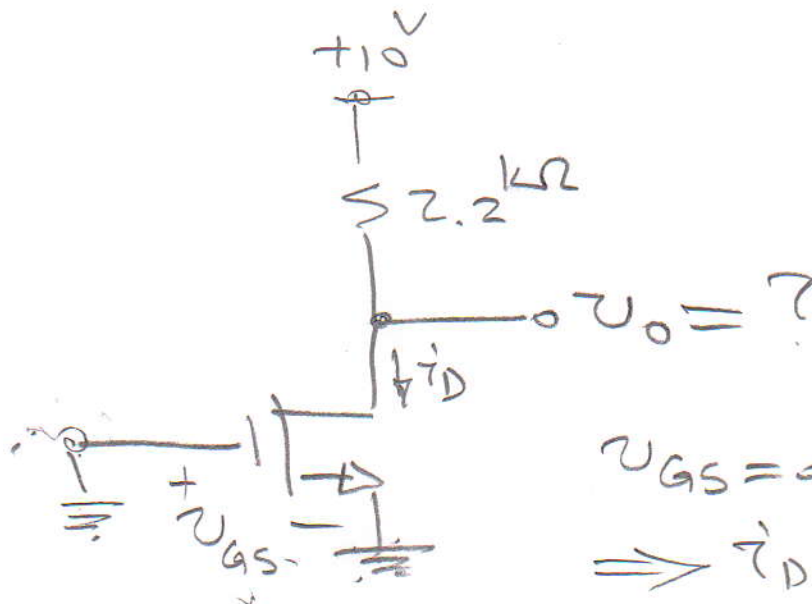

$$V_{GS} = 0 \Rightarrow V_{GS} < V_{tn}$$


$$\Rightarrow i_D = 0$$

$$\Rightarrow \boxed{V_O = 10V}$$


3

Example #2

$$V_{tp} = -1.1V$$

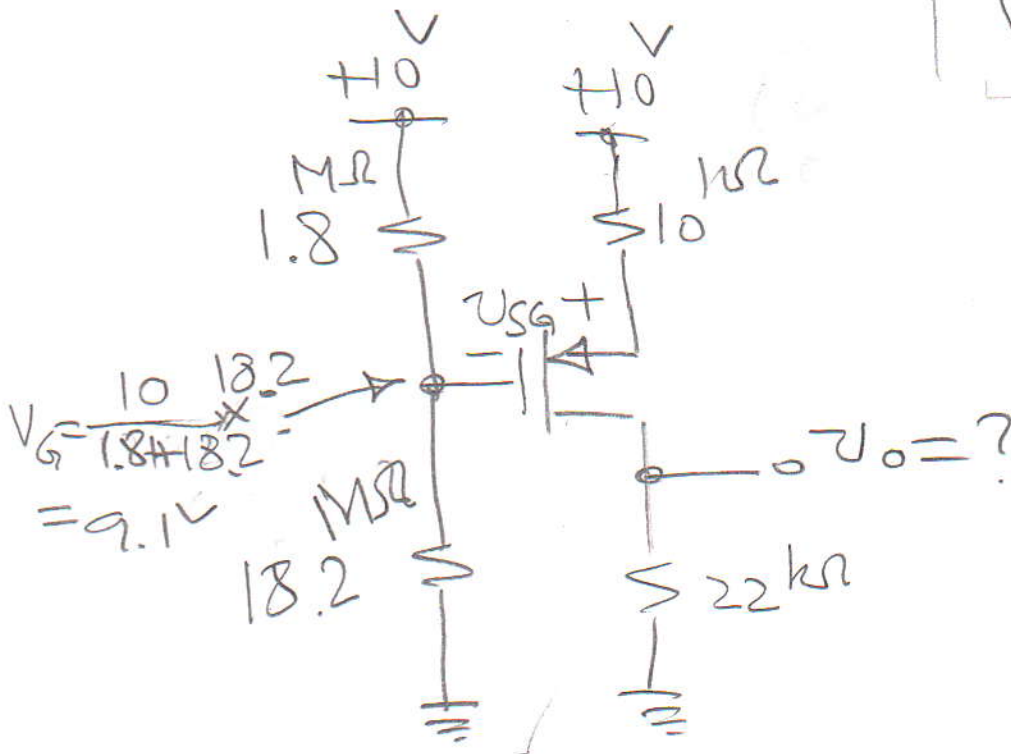

Assume off:

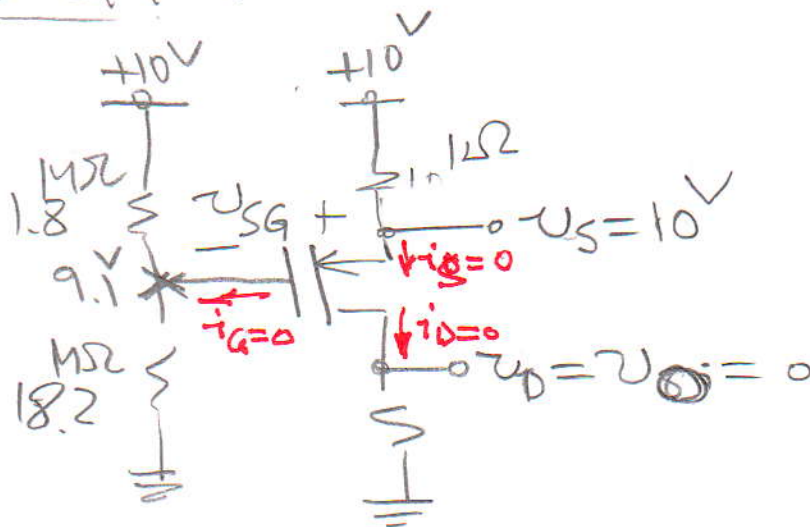


$$V_{SG} = V_S - V_G = 10 - 9.1 = 0.9V$$

$$V_{SG} \geq |V_{tp}| ?$$

$$\text{No! } V_{SG} = 0.9V, |V_{tp}| = 1.1V$$

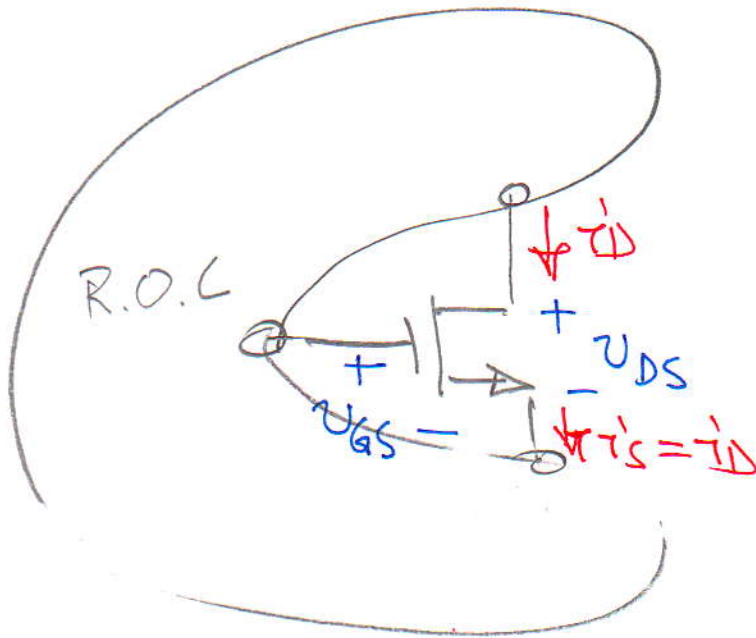(4)

② Triode mode of operation
(corresponding to Saturation mode in the BJT)



$$\begin{aligned}
 V_{GS} &> V_{tn} \\
 V_{DS} &\leq \underbrace{V_{GS} - V_{tn}}_{V_{ov}} \Rightarrow i_D = K_n \left[\underbrace{(V_{GS} - V_t)}_{V_{ov}} V_{DS} - \frac{V_{DS}^2}{2} \right] \\
 &= K_n \left[\underbrace{(V_{GS} - V_t)}_{V_{ov}} - \frac{V_{DS}}{2} \right] V_{DS}
 \end{aligned}$$


where K_n is called "transconductance parameter" in mA/V^2

$$V_{GS} - V_t \triangleq V_{ov} \Rightarrow V_{GS} = V_t + V_{ov}$$

V_{ov} : over-drive voltage
(typically $0.5\text{V} \dots$)

Example #3

5

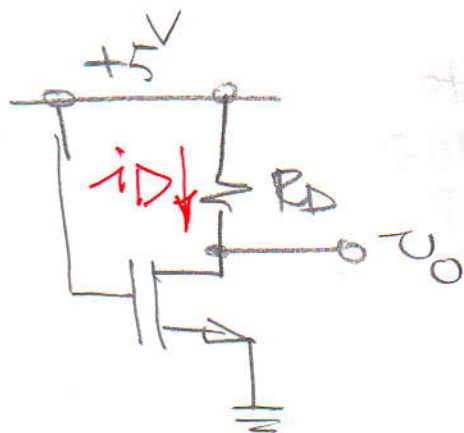

$$k_n = 1.0 \text{ mA/V}^2$$

$$V_{tn} = 1.0 \text{ V}$$

Find R_D if

$$v_O = 0.1 \text{ V}$$

$$v_G = 5 \text{ V}; v_S = 0 \text{ V} \Rightarrow v_{GS} = 5 \text{ V}$$

$$v_{GS} > V_{tn} ? \text{ ; Yes! } v_{GS} = 5 \text{ V}$$
$$V_{tn} = 1.0 \text{ V}$$

$$v_{DS} = v_D - v_S = 0.1 - 0 = 0.1 \text{ V}$$

$$v_{DS} < v_{GS} - V_{tn} ? \text{ ; Yes!}$$
$$0.1 \quad V_{ov} = 5 - 1 = 4 \text{ V}$$

Transistor is in triode mode.

$$i_D = k_n \left[(v_{GS} - V_{tn}) v_{DS} - \frac{1}{2} v_{DS}^2 \right]$$
$$= 1.0 \left[4 \times 0.1 - \frac{1}{2} \times (0.1)^2 \right]$$
$$= \underline{0.395 \text{ mA}}$$

$$R_D = \frac{5 \text{ V} - 0.1 \text{ V}}{0.395} = 12.40 \text{ k}\Omega$$

(6)


$$i_D = K_n \left[\underbrace{(v_{GS} - V_{th})}_{V_{OV}} v_{DS} - \frac{1}{2} v_{DS}^2 \right]$$

$$i_D = K_n \left[V_{OV} - \frac{1}{2} v_{DS} \right] v_{DS}$$

$$\Rightarrow \left(\frac{v_{DS}}{i_D} \right) = \frac{1}{K_n \left[V_{OV} - \frac{1}{2} v_{DS} \right]}$$

of resistance dimension
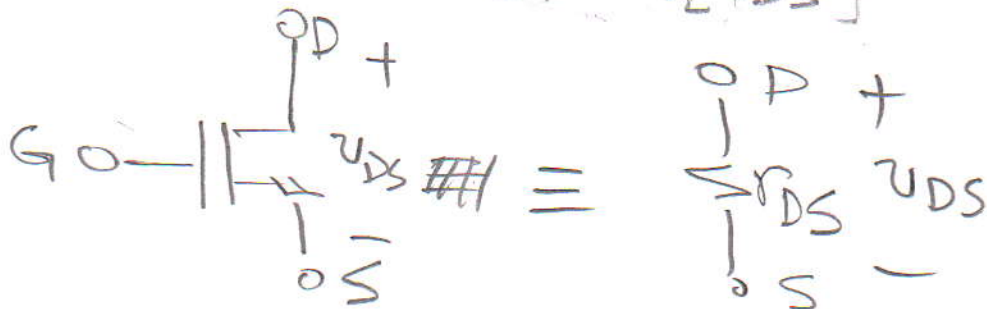
$$r_{DS} \triangleq \frac{1}{K_n \left[V_{OV} - \frac{1}{2} v_{DS} \right]}$$



If r_{DS} is nonlinear since its value depends on the voltage across it, i.e., v_{DS} .

$$\text{If } v_{DS} \ll 2V_{OV} \Rightarrow r_{DS} \approx \frac{1}{K_n \underbrace{V_{OV}}_{V_{GS} - V_{th}}}$$


A NOT GATE

⑦

$$k_n = 0.5 \text{ mA/V}^2$$

$$V_t = 1.0 \text{ V}$$

$$R_D = 10 \text{ k}\Omega$$

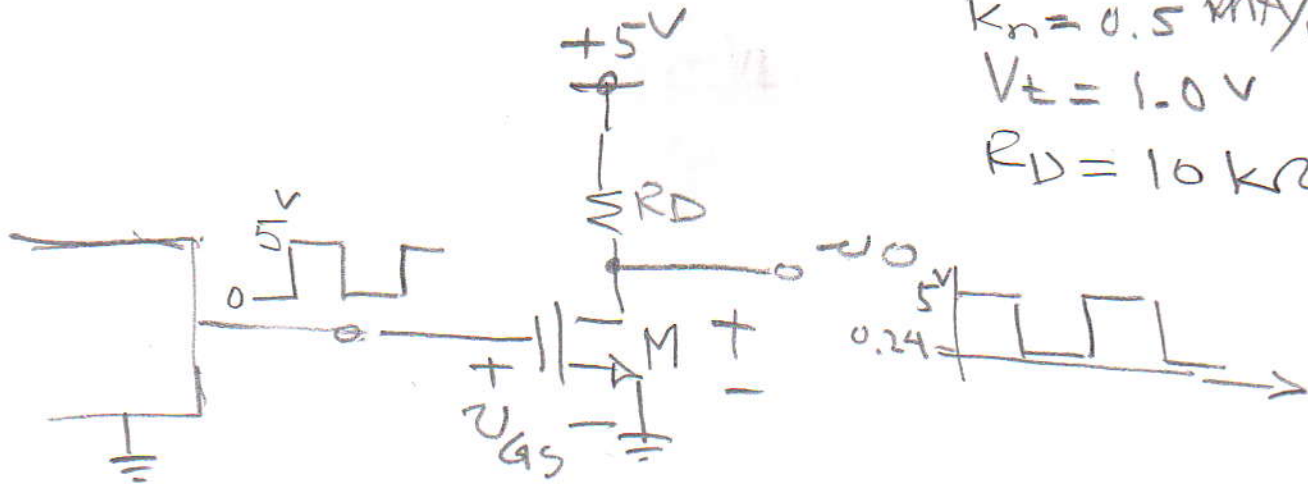

if $v_{GS} = 0 \rightarrow M: \text{off} \rightarrow i_D = 0 \rightarrow v_o = 5 \text{ V}$
High

if $v_{GS} = 5 \text{ V} \rightarrow M: \text{triode mode} \rightarrow$

$$i_D = k \left[V_{OV} - \frac{1}{2} V_{DS} \right] V_{DS}$$

But we know:


$$r_{DS} \approx \frac{1}{k V_{OV}} = \frac{1}{0.5 \times (5 - 1)} = 0.5 \text{ k}\Omega$$

$$v_o = \frac{5}{10.5} \times 0.5 = 0.24 \text{ V} \rightarrow \text{LOW}$$

$$v_{DS} = 0.24 \text{ V}, V_{OV} = 4 \text{ V}$$


$v_{DS} < V_{OV} \checkmark$ triode is correct

(8)

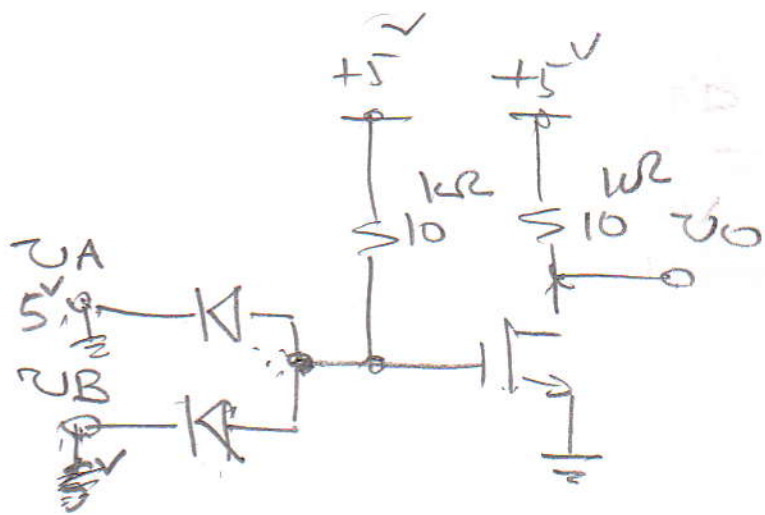


NAND Gate

v_A	v_B	v_O
0	0	5
0	1	5
1	0	5
1	1	0.24V


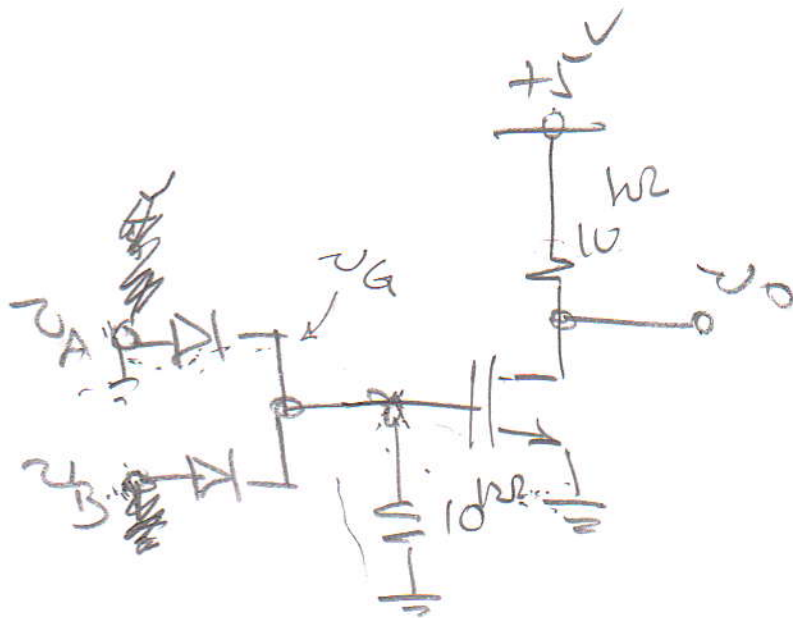


v_A	v_B	v_O
0	0	5V
0	1	0.29
1	0	0.29
1	1	0.29
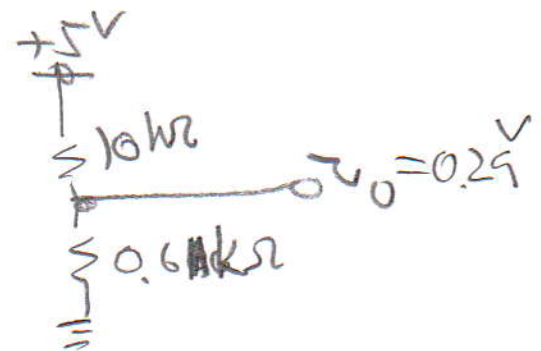
$$v_G = 4.3V \rightarrow r_{DS} = \frac{1}{0.5 \times (4.3 - 1)} = 0.61V$$



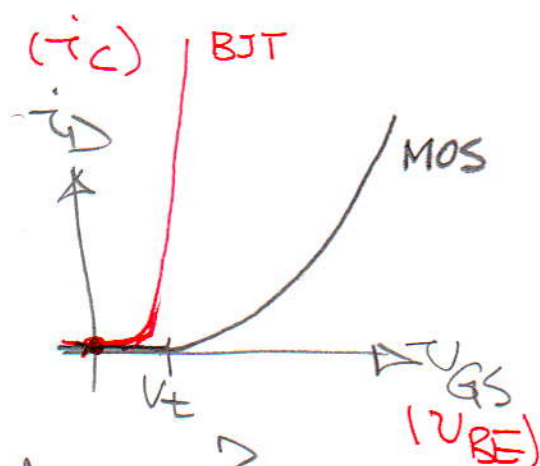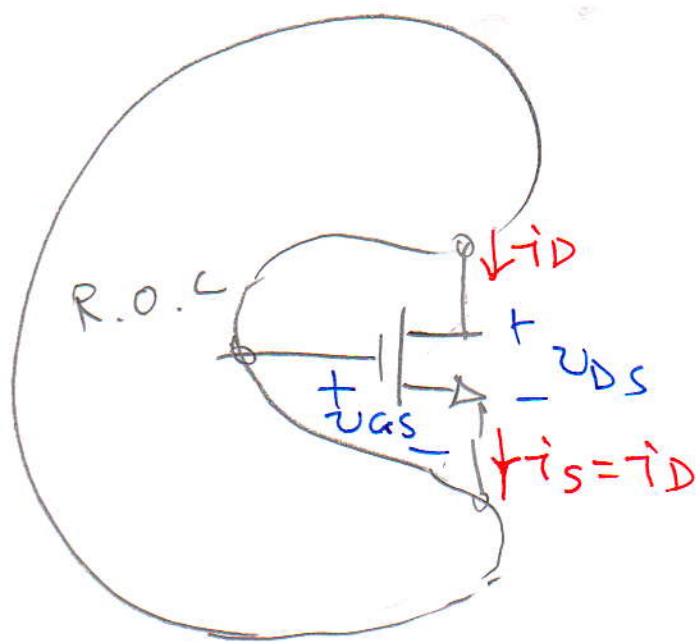- ③ Saturation mode of operation
(equivalent to the active mode in the BJT) \Rightarrow good for amplification.



$$V_{GS} > V_t$$

$$V_{DS} > \underbrace{V_{GS} - V_t}_{V_{OV}}$$

$$\rightarrow i_D = \frac{1}{2} K_n V_{OV}^2$$

ignoring Early effect.

$$i_D = \frac{1}{2} K_n V_{OV}^2 \left(1 + \frac{V_{DS}}{V_A} \right)$$

Where $V_{OV} = V_{GS} - V_t$



For the BJT:

$$i_C = I_S e^{V_{BE}/V_T} \quad \text{W.O.E.E}$$

$$i_C = I_S e^{V_{BE}/V_T} \left(1 + \frac{V_{CE}}{V_A} \right) \quad \text{W.E.E}$$

Example

$K_n = 1.0 \text{ mA/V}^2$, $V_t = 1.0 \text{ V}$, $\lambda = 0$ ($\lambda = \frac{1}{V_A} \Rightarrow V_A = \infty$)
 $V_{DD} = 5 \text{ V}$, $I_D = 0.5 \text{ mA}$; Find R_D .

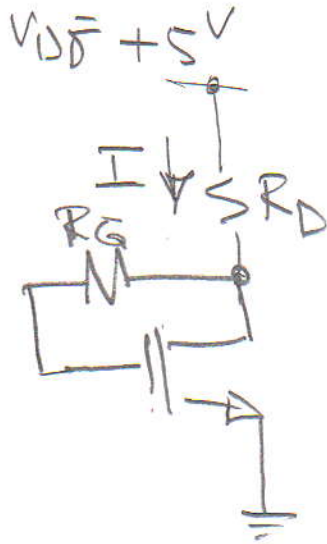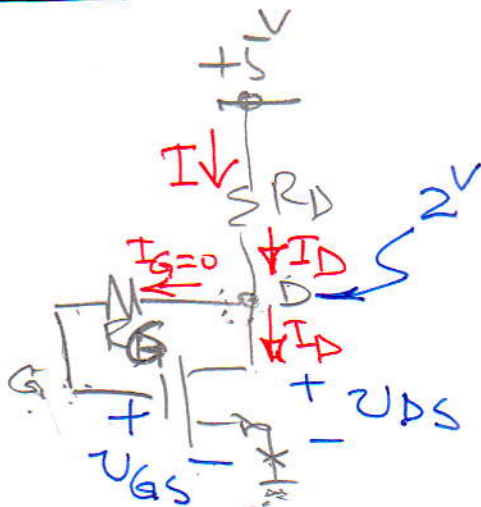Solution

Goes without saying that MOS is in the Saturation mode:

If $V_{GS} = V_{DS}$ (KVL)

$$\Rightarrow V_{DS} \geq V_{GS} - V_t$$

$$0.5 \text{ mA} = \frac{1}{2} \times 1.0 \times V_{OV}^2 \Rightarrow \underline{V_{OV} = 1 \text{ V}}$$

$$V_{GS} = V_{OV} + V_t = 1 + 1 = 2 \text{ V}$$

$$V_{DS} = V_{GS} \Rightarrow V_{DS} = 2 \text{ V} \Rightarrow V_D = 2.0 \text{ V}$$

$$R_D = \frac{5 - 2}{0.5} = 6.0 \text{ k}\Omega$$

E12

E24

1.0

1.2

1.5

1.8

2.2

2.7

3.3

3.9

4.7

5.6

6.8

8.2

There are 12
values in
every decade...

10


12

15

Small-Signal Model of the MOSFET

(12)

Test circuit

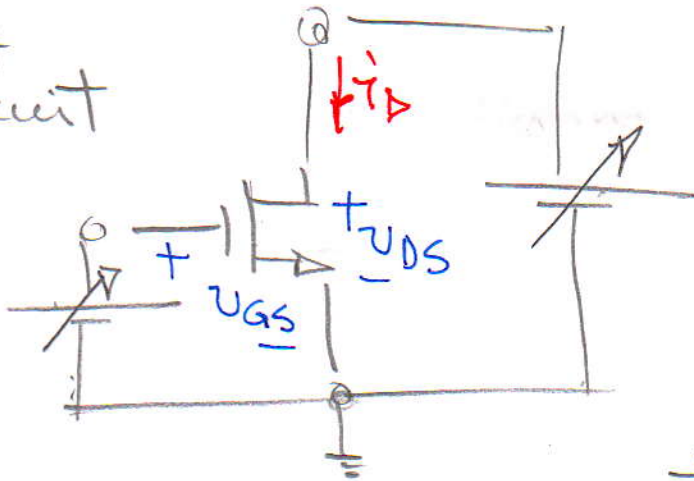

Device: in the Saturation mode (active mode in the BJT).

$$v_{DS} \gg v_{GS} - V_t$$

$$\Rightarrow i_D = \frac{1}{2} K v_{OV}^2$$

$$\Rightarrow i_D = \frac{1}{2} K (v_{GS} - V_t)^2$$



(ignoring Early effect)

Let $v_{GS} = \underbrace{V_{GS}}_{\text{large \& constant}} + \underbrace{v_{gs}}_{\text{small \& variable}}$



$$|v_{gs}| \ll V_{GS}$$

$$i_D = I_D + i_d$$

Question: How is i_d related to v_{gs} .

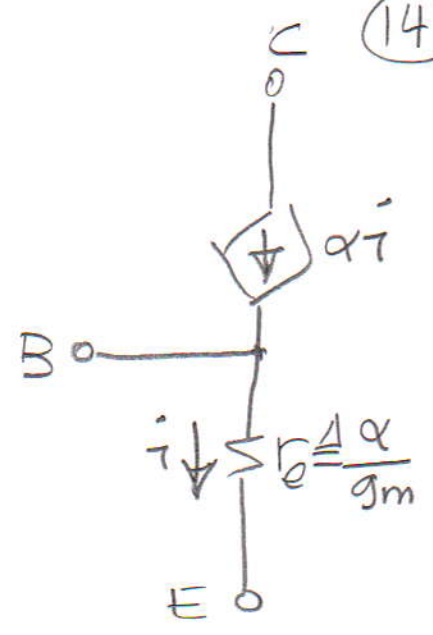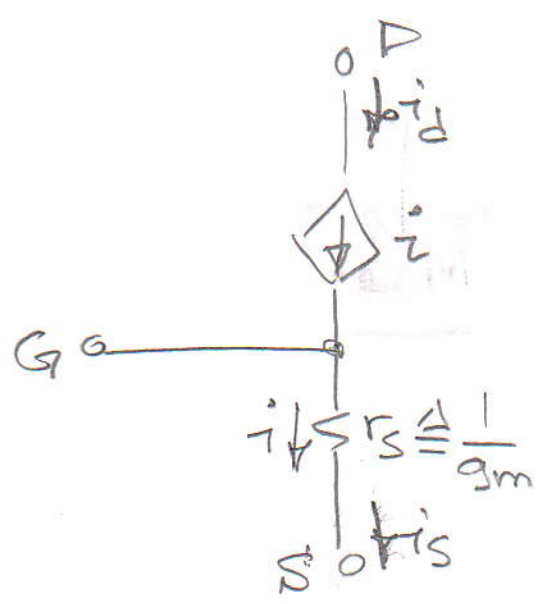

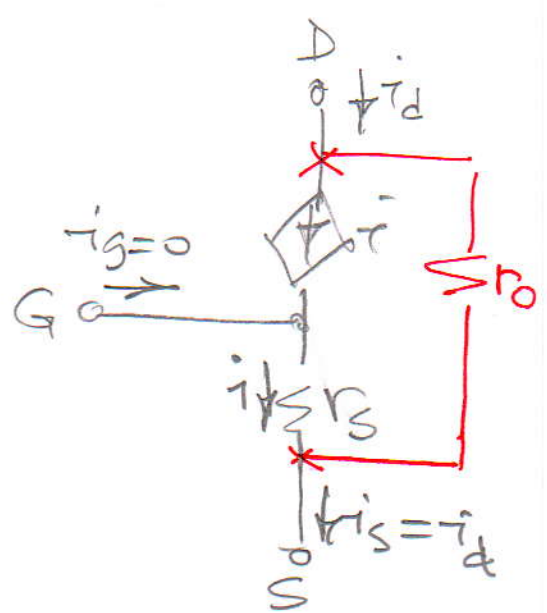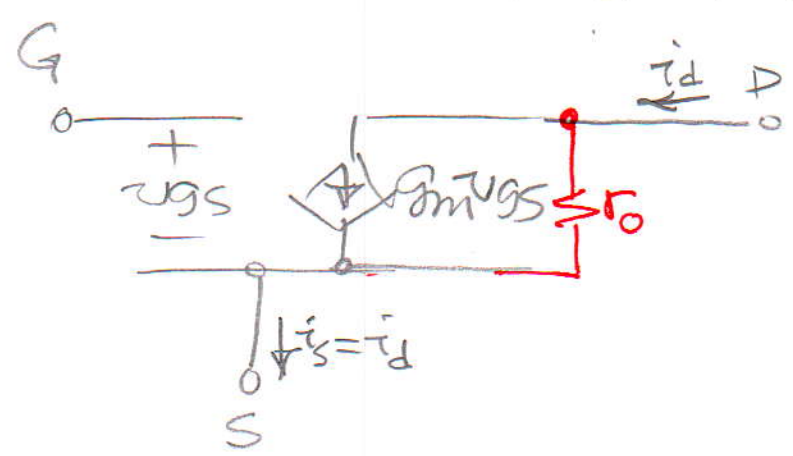Including "Channel-length modulation" effect or "Early effect".



$$r_o = \frac{|V_A|}{I_D'}$$

I_D' = Drain current ignoring Early eff.

$$I_D' = \frac{1}{2} k V_{ov}^2$$

$$g_m = K V_{ov}$$

But $I_D \approx \frac{1}{2} K V_{ov}^2 \Rightarrow V_{ov} = \sqrt{\frac{2I_D}{K}}$

$$\Rightarrow g_m \approx \sqrt{2KI_D}$$

Also,


$$K = \frac{2I_D}{V_{ov}^2}$$

$$\Rightarrow g_m \approx \frac{2I_D}{V_{ov}}$$

Amplifiers

BJT	CE	CC	CB
MOS	CS	CD	CG

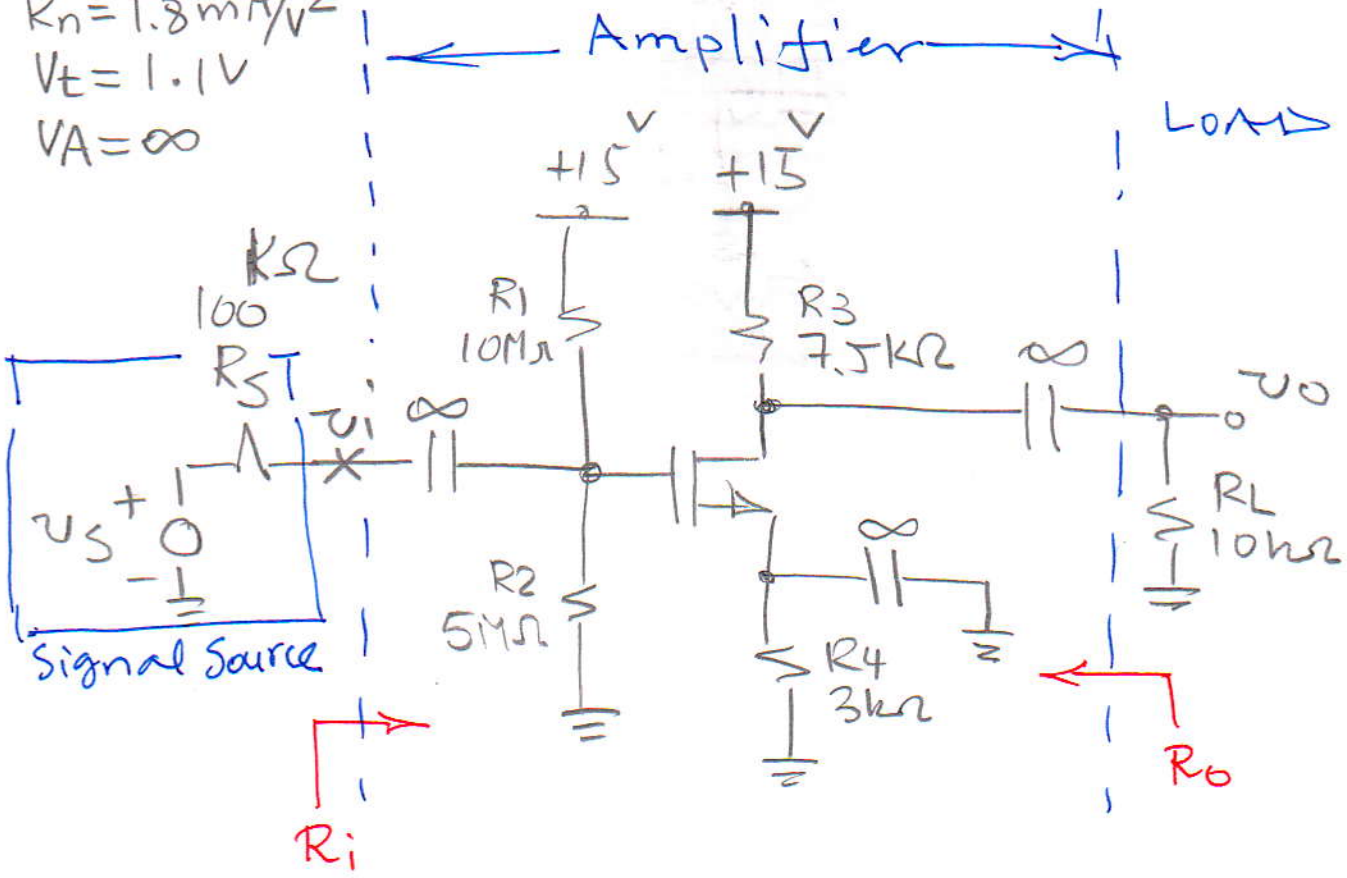$K_n = 1.8 \text{ mA/V}^2$
 $V_t = 1.1 \text{ V}$
 $V_A = \infty$



$$A_{v0} = \frac{v_o}{v_i} \bigg|_{R_L = \infty}$$

$$A_v = \frac{v_o}{v_i} \bigg|_{R_L \neq \infty}$$


$$A_{vS} = \frac{v_o}{v_S} \bigg|_{R_L \neq \infty}$$

$R_i :$

$R_o :$

DC Analysis

(17)

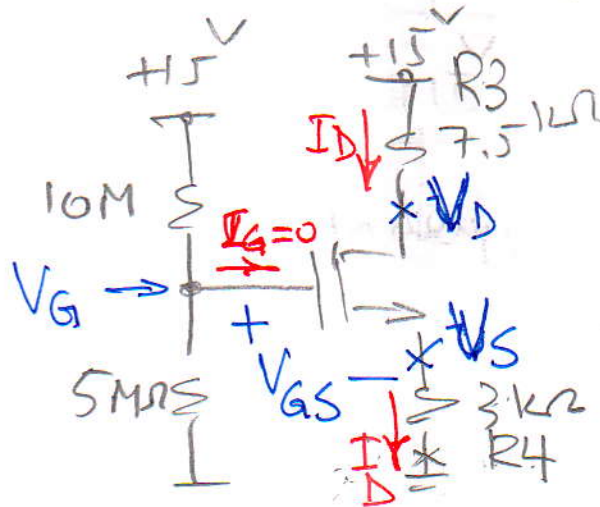

$$V_G = \frac{15}{10+5} \times 5 = 5V$$

$$\text{KVL: } V_G - V_{GS} - R_4 I_D = 0$$

$$5 - V_{GS} - 3I_D = 0 \quad (1)$$

Ass. sat. mode:

$$I_D = \frac{1}{2} K (V_{GS} - V_t)^2$$

$$I_D = \frac{1}{2} \times 1.8 (V_{GS} - 1.1)^2$$

$$= 0.9 (V_{GS} - 1.1)^2$$

$$= 0.9 (V_{GS}^2 - 2.2V_{GS} + 1.21)$$

(2)

Eliminate I_D between (1) & (2):

$$5 - V_{GS} - 3 \times 0.9 (V_{GS}^2 - 2.2V_{GS} + 1.21) = 0$$

$$\underline{2.7V_{GS}^2 - 4.94V_{GS} - 1.733 = 0} \Rightarrow V_{GS} < \begin{matrix} -3.01V \times \\ 2.13V \checkmark \end{matrix}$$

(18)

$$I_D = \frac{1}{2} \times$$

$$V_{OV} = V_{GS} - V_t =$$

$$= 2.13 - 1.1 = \underline{1.03V}$$

$$I_D = \frac{1}{2} K V_{OV}^2 = \frac{1}{2} \times 1.8 \times (1.03)^2$$

$$= 0.9 \times 1.06$$

$$= 0.954 \text{ mA}$$

$$V_D = +15V - R_3 I_D$$

$$= +15 - 7.5 \times 0.954 = 7.84V$$

$$V_S = R_4 I_D = 3 \times 0.954 = 2.86V$$

$$V_{DS} = V_D - V_S = 7.84 - 2.86 = 4.98V$$

$$V_{OV} = 1.03V$$


$\Rightarrow V_{DS} > V_{OV}$ ✓ sat. mode is the right mode.

$$g_m = K V_{OV} = 1.8 \times 1.03$$

$$= 1.854 \text{ mS}$$

Ac Analysis

19

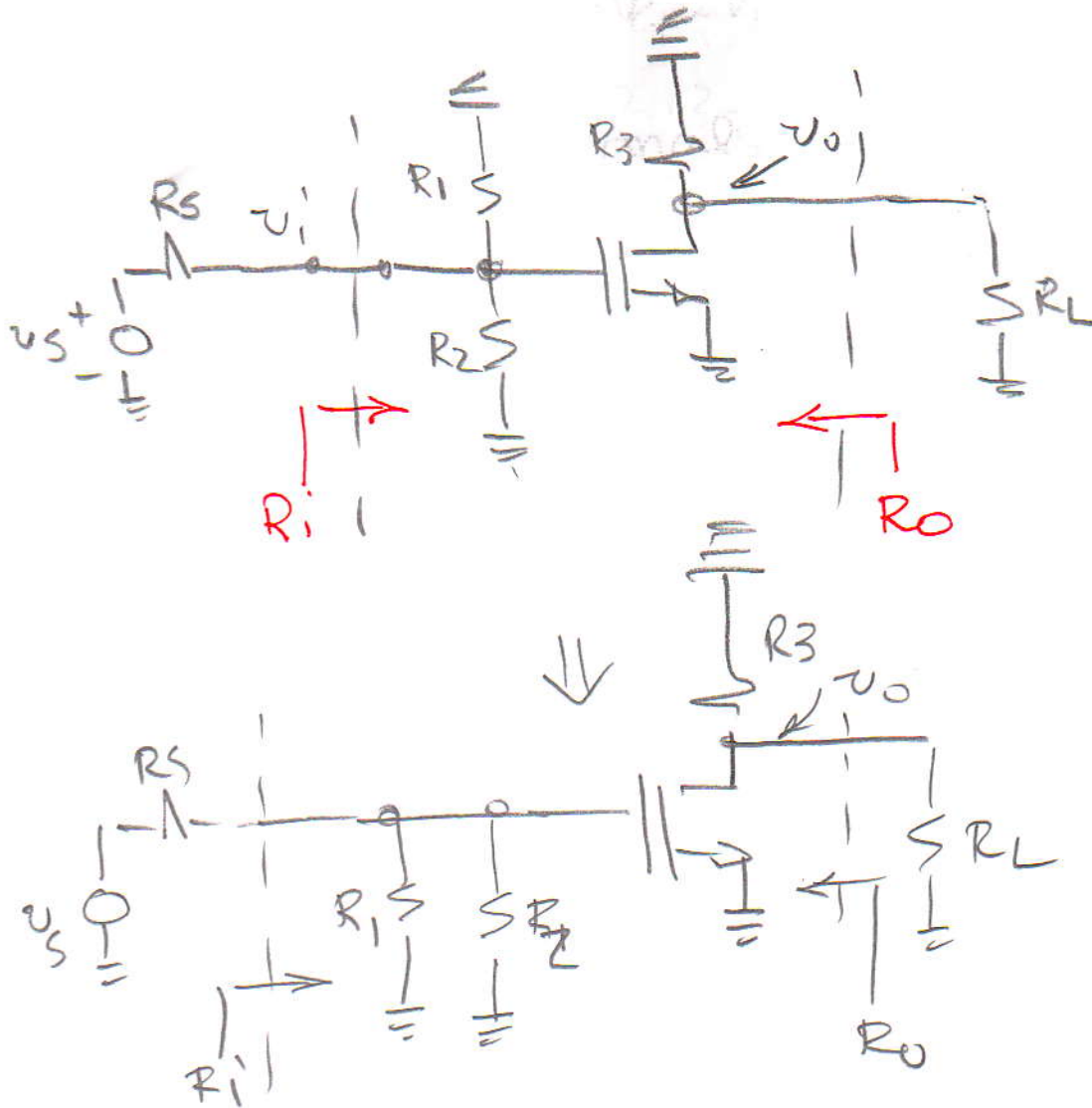

CS amp. (equivalent to CE).

BJT

$$\frac{v_o}{v_i} = \frac{-g_m R_C}{1 + g_m R_E}$$

MOS


$$\frac{v_o}{v_i} = \frac{-g_m R_D}{1 + g_m R_S}$$

$$A_{v_o} = \frac{v_o}{v_i} \Big|_{R_L = \infty} = \frac{-g_m R_3}{1 + g_m \times 0} = -g_m R_3$$

$$A_v = \frac{v_o}{v_i} \Big|_{R_L \neq \infty} = \frac{-g_m (R_3 \parallel R_L)}{1 + g_m \times 0} = -g_m (R_3 \parallel R_L)$$


Input Resis.

(20)

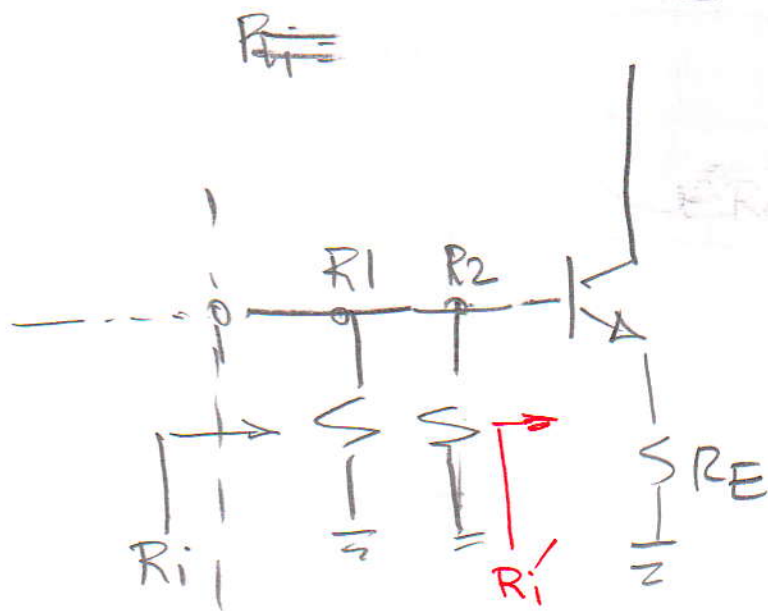

$$R_i' = r_{\pi} + (\beta + 1) R_E$$
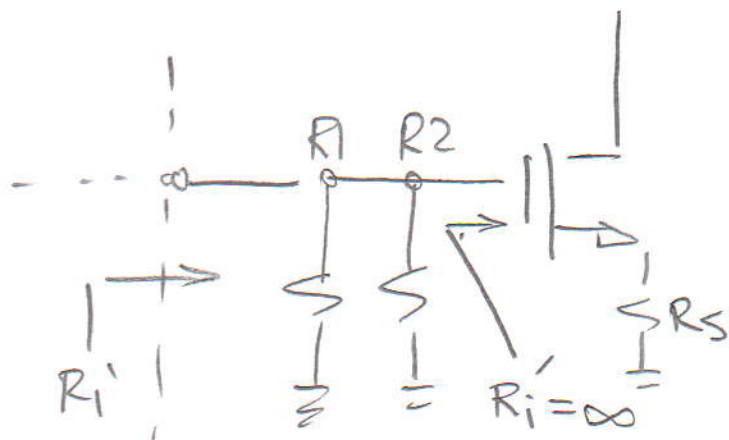
$$R_i = R_1 \parallel R_2 \parallel R_i'$$



$$R_i' = \infty$$


$$R_i = R_1 \parallel R_2 \parallel \infty$$

$$= \underline{R_1 \parallel R_2}$$


Finally

(21)


Output Resistance

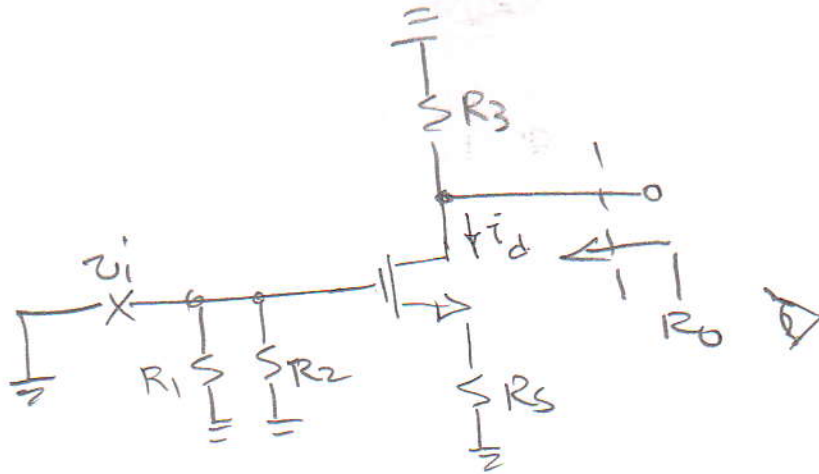

\Downarrow

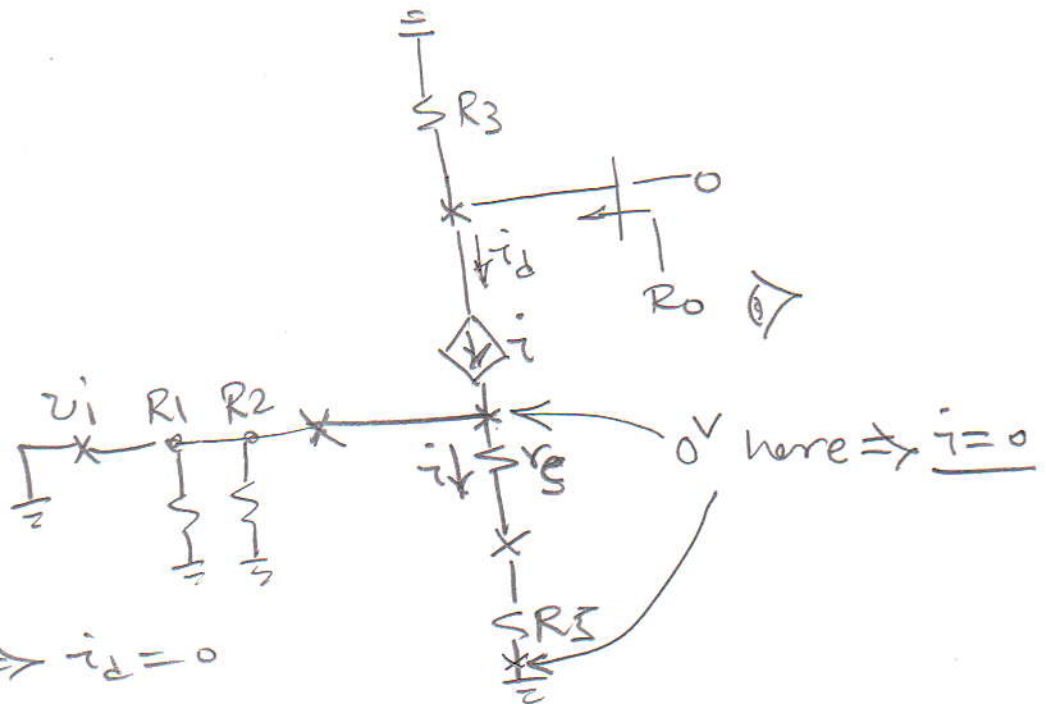


$$i = 0 \Rightarrow i_d = 0$$

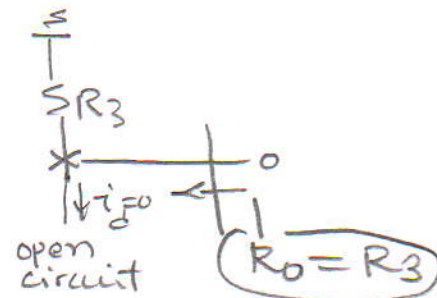


DESIGN Example


(22)

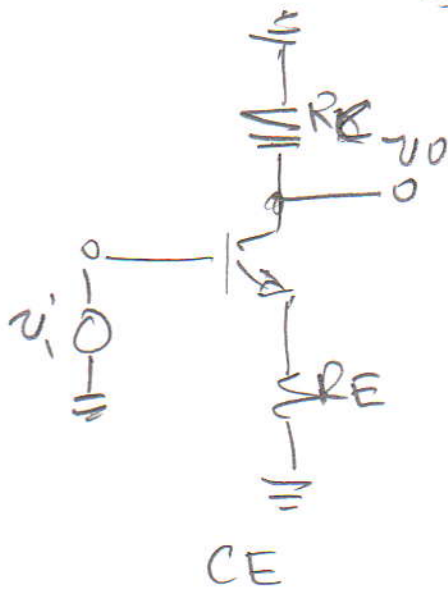

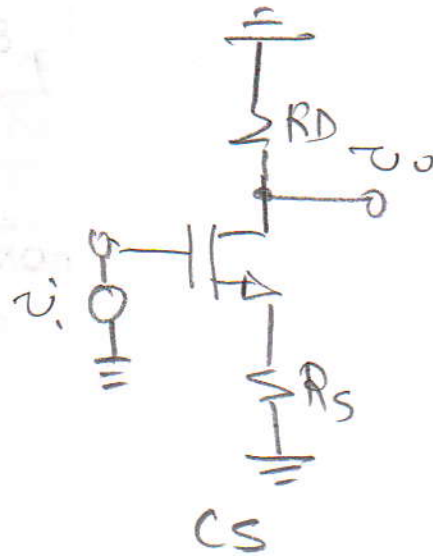
$$A_{v_o} \approx \frac{-g_m R_C}{1 + g_m R_E}$$


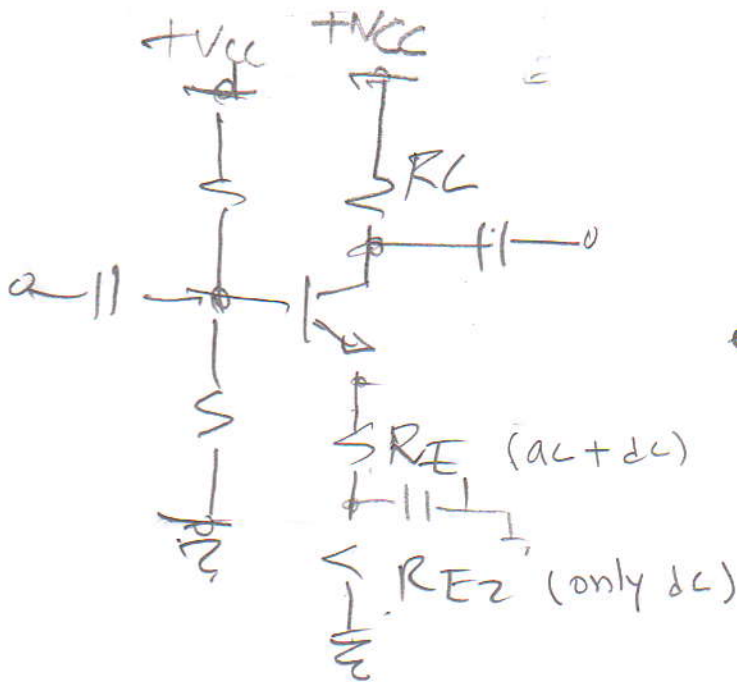
$$A_{v_o} = \frac{-g_m R_D}{1 + g_m R_S}$$



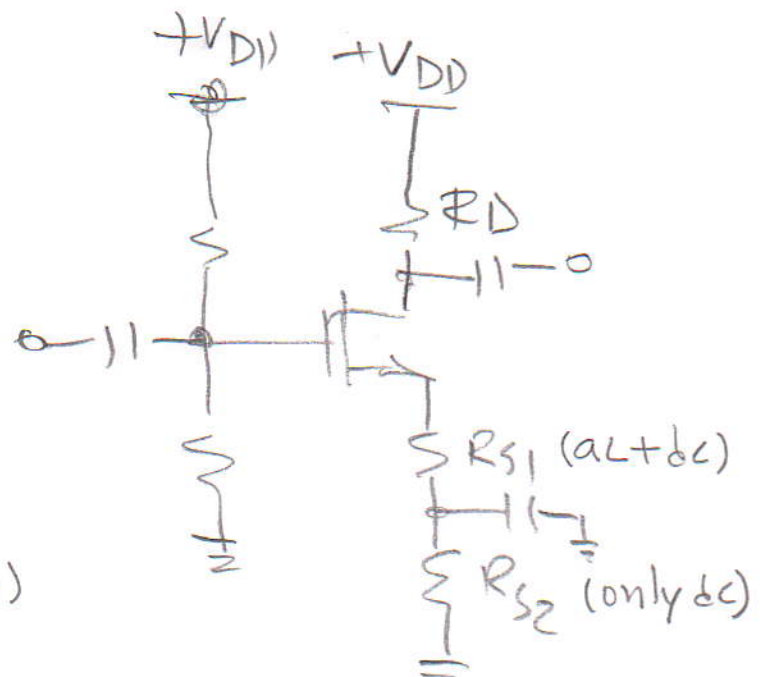
$$A_{v_o} = \frac{-g_m R_C}{1 + g_m R_{E1}}$$




$$A_{v_o} = \frac{-g_m R_D}{1 + g_m R_{S1}}$$


Design (using BJT, and may be other things ...) such that: (23)

- ① - $|A_{v0}| = 25$
 - ② - $R_{out} = 5\text{ k}\Omega$
 - ③ - $R_{in} \geq 15\text{ k}\Omega$
 - ④ - $V_{CC} = +12\text{ V}, 0$
 - ⑤ - Reasonable swing is achieved
- $\beta = 100$

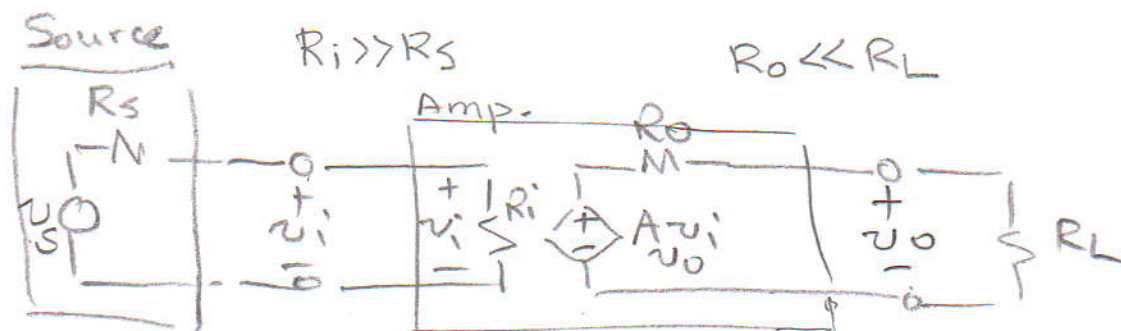

Candidate Designs: CE amp.

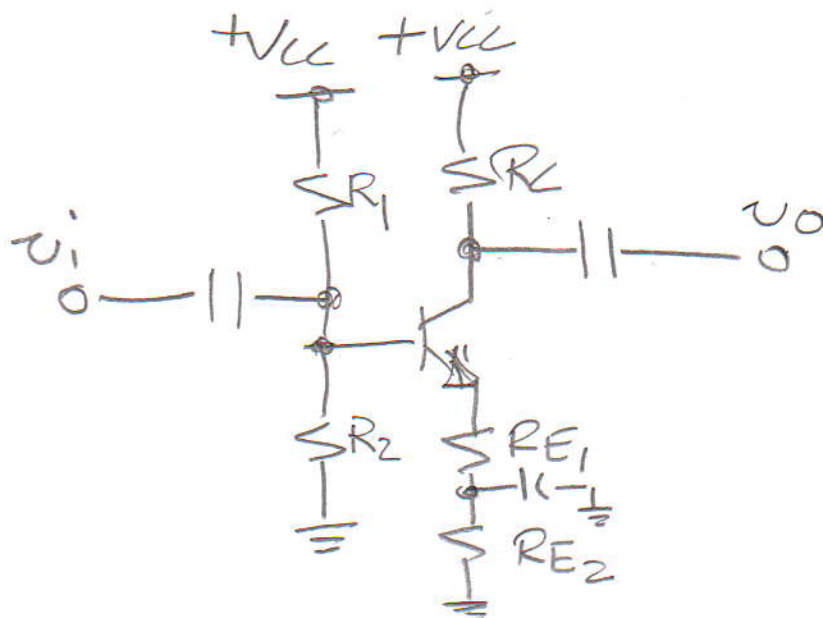

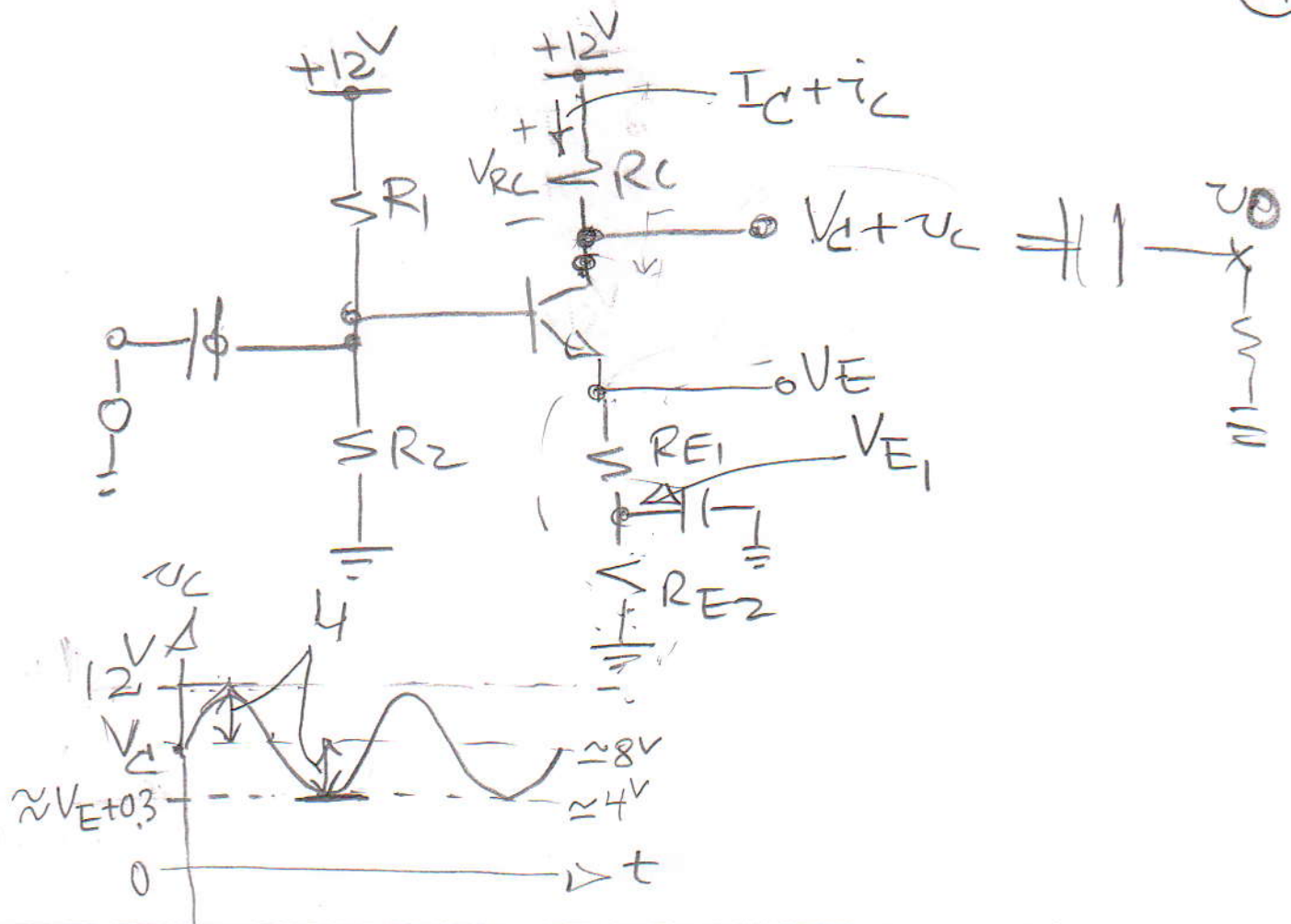

Rule of Thumb:

Try $V_{RC} = V_{CE} = V_E \approx \frac{V_{CC}}{3} = 4V$
for a reasonable swing!

On the other hand, we know that (in CE):

$$R_{out} = R_C \Rightarrow \underline{R_C = 5k\Omega}$$

$$I_C = \frac{V_{RC}}{R_C} = \frac{4}{5k\Omega} = \underline{0.8mA}$$

$$\Rightarrow g_m \approx 40 \times 0.8 = \underline{32mS}$$

$$\Rightarrow g_m R_L = 32 \times 5 = 160 \frac{V}{V}$$

$$|A_{v0}| = \frac{g_m R_L}{1 + g_m R_{E1}} = 25 \Rightarrow$$


$$g_m R_{E1} = \frac{160}{25} - 1$$

$$\Rightarrow R_{E1} = \underline{0.168 \text{ k}\Omega} \quad \text{or } \underline{168 \Omega}$$

$$V_E = 4 \text{ V}, \quad I_C = 0.8 \text{ mA} \Rightarrow I_E \approx I_C = 0.8 \text{ mA}$$

$$R_{E1} + R_{E2} = \frac{4 \text{ V}}{0.8 \text{ mA}} = 5 \text{ k}\Omega$$

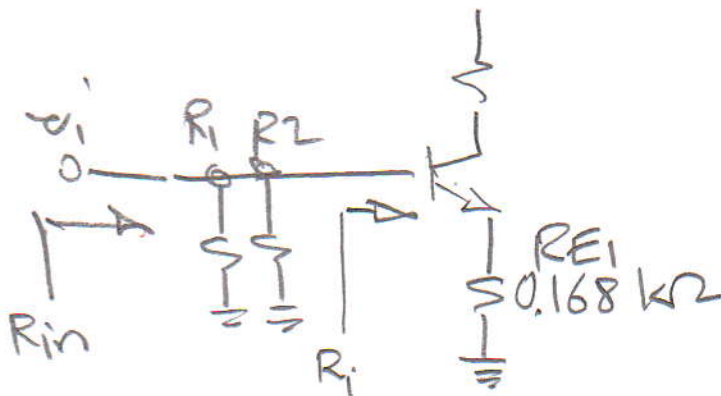
$$R_{E2} = 5 - 0.168 \approx \underline{4.83 \text{ k}\Omega}$$



$$\begin{aligned} R_i &= r_{\pi} + (\beta + 1) R_{E1} \\ &= \frac{100}{32} + 101 \times 0.168 \\ &\approx 20 \text{ k}\Omega \end{aligned}$$

$$\begin{aligned} R_{in} &= R_1 \parallel R_2 \parallel R_i \geq 15 \text{ k}\Omega \\ &\Rightarrow R_1 \parallel R_2 \geq 60 \text{ k}\Omega \end{aligned}$$

(26)

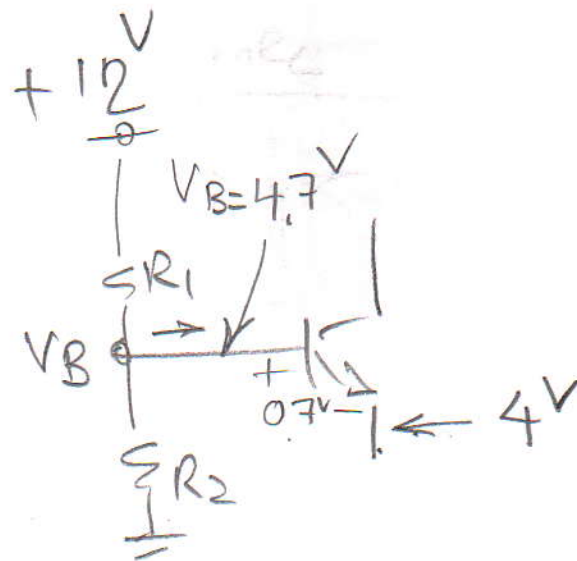

Ignore I_B (as an approx.)

$$V_B \approx \frac{+12}{R_1 + R_2} \times R_2$$

$$\Rightarrow 4.7 = \frac{12}{R_1 + R_2} R_2$$

$$\rightarrow \frac{R_1}{R_2} = \frac{12}{4.7} - 1 \Rightarrow \underline{R_1 \approx 1.55 R_2}$$


on the other hand,

$$\frac{R_1 R_2}{R_1 + R_2} \geq 60 \quad \text{let}$$

$$\text{let } \frac{R_1 R_2}{R_1 + R_2} = 60$$

$$\frac{1.55 R_2^2}{2.55 R_2} = 60 \Rightarrow R_2 = 98.7 \text{ k}\Omega$$
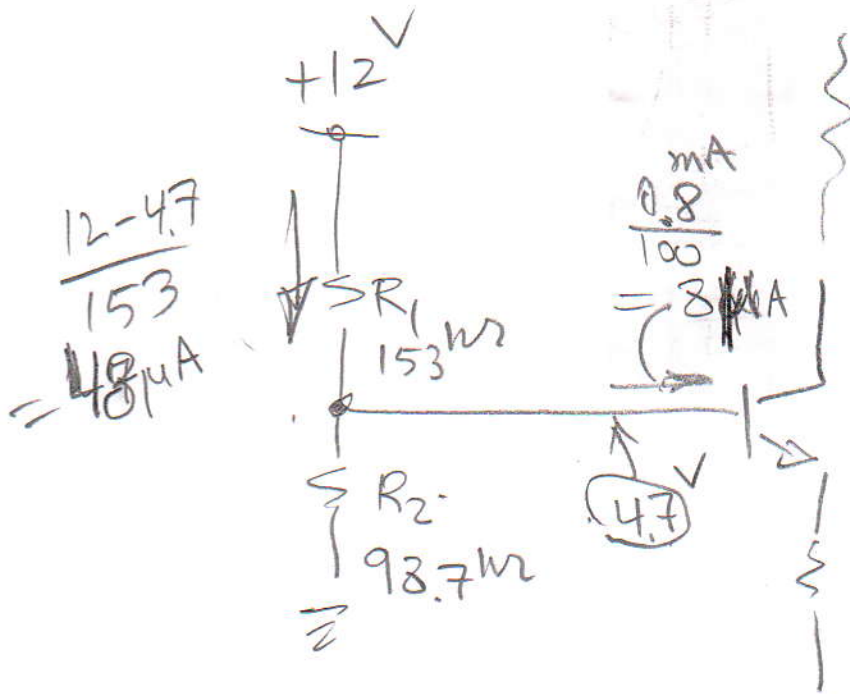
$$\Rightarrow \underline{R_1 = 153 \text{ k}\Omega}$$



If R_{in} was required to be
 (e.g. $\geq 40 \text{ k}\Omega$)
 So large that no value of
 R_1 or R_2 would be feasible, we
 would bring a CC stage as
 Buffer:

