

# Final Answers Only

**Ryerson University**  
Department of Electrical and Computer Engineering  
**ELE404 (Electronic Circuits I)**  
**Midterm Examination (W2015)**  
**February 2015**  
**Duration: 100 minutes**  
Examiner: Prof. A. Yazdani

Name: .....  
[Print Last Name] [Print First Name]

Student No: ..... Section: ....


## NOTES

1. This is a closed-book examination. No aids other than basic calculators are permitted.
2. Including this page, the **examination paper has 20 pages**. It is your responsibility to **check the integrity of your examination paper and immediately notify the invigilators of any missing pages**.
3. **DO NOT DETACH ANY PAGES** from the examination paper.
4. The examination consists of **FIVE QUESTIONS**, *each* question is worth as indicated in the following Table. The entire examination is worth *100* marks.

Question #	Maximum Mark	Mark Earned
1	<b>30</b>	
2	<b>10</b>	
3	<b>25</b>	
4	<b>15</b>	
5	<b>20</b>	
Total	<b>100</b>	

5. Answer all questions within the blank spaces provided under each question in this examination paper or on a page marked as "Blank Page" in the examination paper.  
**Do Not Use the Reverse as it will not be marked.**
6. *If in doubt about any question, clearly state your assumptions in answering the question.*
7. Part marks for an answer will only be given if the *correct methodology* is clearly shown.

Q1: In the circuit of **Fig. 1**,  $D_1$  and  $D_2$  are Light-Emitting Diodes (LED) that exhibit a constant voltage drop of  $2.5\text{ V}$  when they are *on*, while they require a minimum forward voltage of  $2.2\text{ V}$  (i.e., the cut-in voltage) to start to glow.  $R_1 = 1.5\text{ k}\Omega$ ,  $R_2 = 1.0\text{ k}\Omega$ ,  $V_{CC} = 10\text{ V}$ , and  $I = 4.0\text{ mA}$ . Assume that the reverse breakdown voltages of the diodes are large.

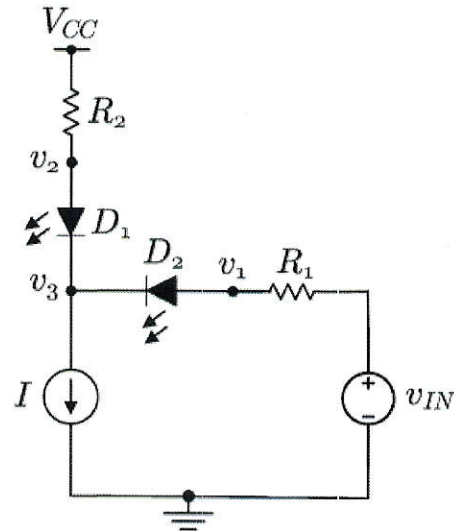

**Fig. 1:** Circuit of Q1.

- 1a) Determine the states of the two LEDs, i.e., *on* or *off*, if the input voltage  $v_{IN}$  is zero. Determine  $v_3$  in this condition. Complete **Table 1a**. Show all the work.

**Table 1a:** Results of the diode circuit of Q1.


State of $D_1$	State of $D_2$	$v_3$ [V]
ON	OFF	3.5

**1b)** Repeat Part (1a) for  $v_{IN} = 16.5\text{ V}$ . Complete **Table 1b**. Show all the work.

**Table 1b:** Results of the diode circuit of Q1.

State of $D_1$	State of $D_2$	$v_3$ [V]
OFF	ON	8

Q2: In the circuit of **Fig. 2**,  $V_s = -15\text{ V}$ . If  $V_o = -12\text{ V}$  at a temperature of  $20\text{ }^\circ\text{C}$ , what will it be the  $40\text{ Celsius}$ ? At  $0\text{ Celsius}$ ? Explain why and/or show the calculations. Summarize your results in **Table 2**.

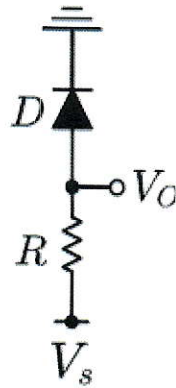


**Fig. 2:** Circuit of Q2.

**Table 2:** Results of the diode circuit of Q2.

$T\text{ }[^\circ\text{C}]$	20	40	0
$V_o[\text{V}]$	-12	-3	-14.25

Q3: In the rectifier of **Fig. 3**, the step-down center-tapped transformer has a voltage conversion ratio (i.e. the ratio  $v_S/v_I$ ) of 120V/15V. The source voltage  $v_S$  is a 60-Hz, 110-Vrms sinusoid. Each diode exhibits a relatively constant forward voltage drop of 1.0 V, and the smoothing capacitor is 1000  $\mu\text{F}$  in capacitance.

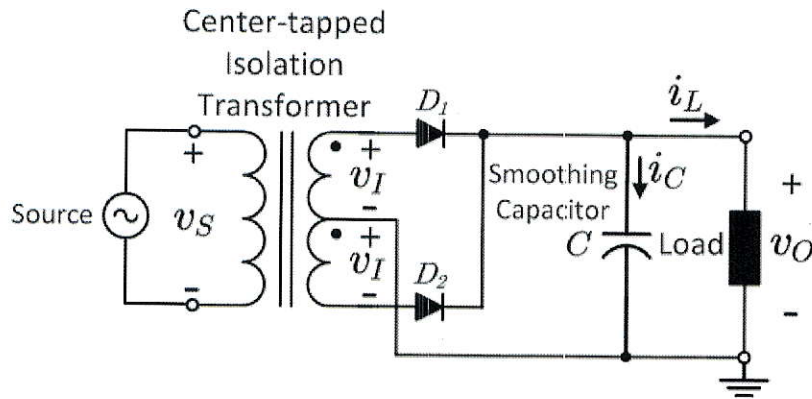

**Fig. 3:** Rectifier of Q3.

- (3a) Determine the *reading of a DC voltmeter* of the output voltage  $v_o$  and the peak-to-peak ripple of  $v_o$ , if the load draws a constant current of  $120\text{ mA}$ . Complete **Table 3a**. Show all the work.

**Table 3a:** results of the circuit of Q3.

DC meter reading of $v_o$ [V]	Peak-to-peak ripple of $v_o$ [V]
17.94	1.0

**(3b)** Repeat Part (3a) if the load is a **82  $\Omega$**  resistor. Complete **Table 3b**. Show all the work.

**Table 3b:** results of the circuit of Q3.

DC meter reading of $v_o$ [V]	Peak-to-peak ripple of $v_o$ [V]
17.50	1.88




(3c) Ignoring the output voltage ripple, determine the Peak Inverse Voltage (PIV) of each diode. Complete **Table 3c**. Show all the work.

**Table 3c:** results of the circuit of Q3.

PIV of each diode [V]
37.88

Q4: In the shunt voltage regulator of **Fig. 4**,  $R = 820\ \Omega$ . According to the manufacturer, the Zener diode gives a voltage of  $v_Z = V_{ZT} = 5.1\text{ V}$  at a test current of  $i_Z = I_{ZT} = 20\text{ mA}$ . Further,  $r_Z = 10\ \Omega$  and  $I_{ZK} = 1.5\text{ mA}$ .

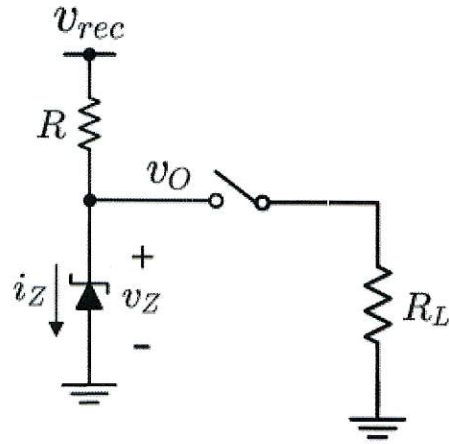

**Fig. 4:** Shunt regulator of Q4.

- (4a) Assuming that the switch is open, determine the peak-to-peak ripple of the output voltage  $v_o$  if the (unregulated) voltage  $v_{rec}$  has a peak-to-peak ripple of 2.0 V. Complete **Table 4a**. Show all the work.

**Table 4a:** results of the circuit of Q4.

Peak-to-peak ripple of $v_o$ [V]
0.024

(4b) Assuming that the switch is closed and  $R_L = 1.0\text{ k}\Omega$ , calculate the minimum permissible value of  $v_{rec}$ . Complete **Table 4b**. Show all the work.

**Table 4b:** results of the circuit of Q4.

Minimum of $v_{rec}$ [V]
10.18


- (4c) Assuming that the switch is closed and  $V_{CC} = 15\text{ V}$ , calculate the minimum permissible value of  $R_L$ . Complete **Table 4c**. Show all the work.

**Table 4c:** results of the circuit of Q4.

Minimum of $R_L$ [ $\Omega$ ]
455

Q5: In the transistor circuit of **Fig. 5**, determine the mode of operation of the transistor and the node voltages.  $V_{CC} = 10\text{ V}$ ,  $R_1 = R_2 = 1.0\text{ k}\Omega$ ,  $R_C = 100\text{ }\Omega$ , and  $R_E = 220\text{ }\Omega$ . Assume that  $V_{BEon} = 0.7\text{ V}$ ,  $V_{CEsat} = 0.3\text{ V}$ , and  $\beta = 50$ .

Complete **Table 5**. Show all the work.

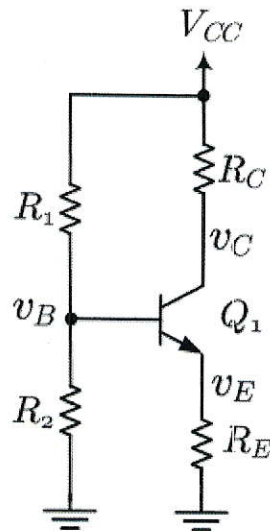

**Fig. 5:** Transistor circuit of Q5.

**Table 5:** transistor's mode of operation and the node voltages in the circuit of Q5.

Mode of Q1	$v_B[V]$	$v_C[V]$	$v_E[V]$
active	4.82	8.17	4.12